# Transformerless Ethernet Operation

DP83848 PHYTER®

### 1.0 Introduction

PHYTER products are designed for robust operation to meet the needs of a variety of end user applications. Non-typical applications which are sensitive to cost, utilize short distance PCB connections, or even extreme environmental conditions may benefit from operation without the use of a transformer. Examples of such applications include extreme environment short distance cable applications, and backplane applications

This application note describes a method for using National's PHYTER products without transformer magnetics. This includes a list of recommendations for configuring transformerless systems. A description of a typical network configuration is provided, followed by descriptions of non-typical transformerless configurations. Finally, this application note presents PHYTER product performance data recorded from a transformerless configuration.

This Application note is applicable to the following products:

DP83848C DP83848I

DP83848YB

DP83848M

DP83848T

DP83848H

DP83848J

DP83848K

# 2.0 Recommendations

In general, it is recommended that transformerless configurations utilize non-polarized blocking capacitors with DC voltage tolerance ratings that meet the needs of specific applications. See *Figure 5*. It is also recommended that blocking capacitors have a minimum capacitance of 33 nF to meet IEEE 802.3 impedance specifications, and a maximum capacitance constrained by application specific DC blocking specifications. It is also recommended that forced 100 Mb/s operation be utilized.

In general, network connections configured using non-typical topologies can raise application specific concerns, especially when node connection lengths exceed 1 meter. Therefore, it is recommended that network designs utilizing non-typical topologies be verified at the specific application level.

# 3.0 Typical Network Configuration Using Transformer Isolation

To understand non-typical transformerless application development constraints, it is first necessary to understand physical network services and signaling, and the functions that transformers provide in typical applications.

A typical network configuration consists of a point to point connection, through a cable, between two physical layer devices. *Figure 4* shows a schematic for a typical trans-

National Semiconductor Application Note 1519 David Miller, Devin Seely, Tung Ngo October 2006



former interface. The transmitter and the receiver of each node are DC isolated from the network cable by 1:1 transformers.

A typical network configuration provides the services of autonegotiation, Auto-MDIX, 10 Mb/s operation, and 100 Mb/s operation. Autonegotiation is a feature which automatically determines the optimal network operating speed. Auto-MDIX is a feature allowing either straight-through or cross-over cables to be used.

Autonegotiation uses link pulses to determine the operating mode. Link pulses appear as differential 2.5V signals when ideal 50 ohm balanced loading is provided. 100 Mb/s data appears as +1V, 0V, and -1V differential signals, and 10 Mb/s data appears as +2.5V and -2.5V differential signals across ideal loading. See *Figure 1*, *Figure 2*, and *Figure 3*.

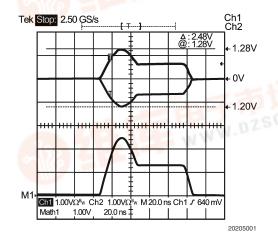


FIGURE 1. Sample Link Pulse waveform

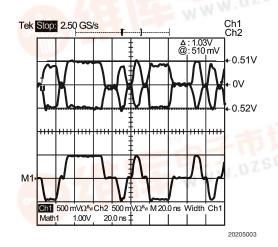


FIGURE 2. Sample 100 Mb/s Waveform (MLT-3)

AN-1519

www.national.com

PHYTER® is a registered trademark of National Semiconductor

# 3.0 Typical Network Configuration DUSing中面ansformer Isolation

(Continued)

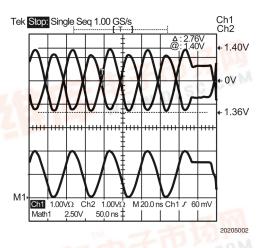


FIGURE 3. Sample 10 Mb/s Waveform

Transformers provide the functions of DC isolation from the cable, and DC biasing at the physical layer device.

Isolation is necessary to meet IEEE 802.3 AC and DC isolation specifications for cabled configurations. IEEE 802.3 isolation requirements are described in section 14.3.1.1 of the specification, and include the ability to sustain cable faults to 1500V 50 or 60 Hz or 2250Vdc voltage levels for 60 seconds.

PHYTER product transmitters and receivers are DC biased internally, from the transformer centertap, and through 50 ohm load resistors used in typical applications.

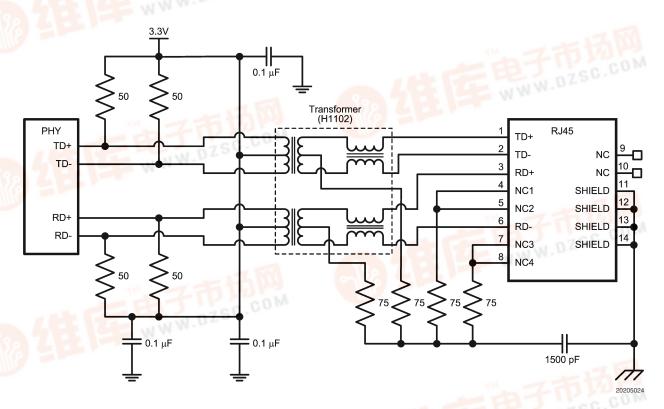


FIGURE 4. Typical 10/100 Mb/s Twisted Pair Interface

# 4.0 Transformerless Configuration

In order to meet the operational requirements of non-typical transformerless network applications, several requirements must be met. Physical layer component transmit and receive separation and biasing requirements must be met, as well as

high voltage DC isolation to meet the specific safety requirements of the application.

For non-typical applications, the isolation that the transformer provides in typical configurations can be realized using non-polarized capacitors. See *Figure 5*.



www.national.com 2

# 4.0 Transformerless Configuration (Continued)

查询DP83848供应商

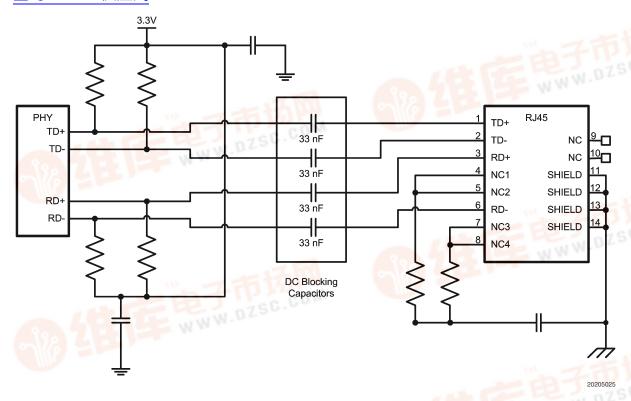


FIGURE 5. Transformerless Configuration

#### **4.1 TRANSMIT REQUIREMENTS**

A typical transformer based application includes a centertap connection to Vdd. 100 Mb/s signaling which is local to the component driver appears as 2.8V to 3.8V signaling across the transformer, with the polarity reversing to create +1V and -1V signaling at the transformer secondary. Refer to Figure 6. 10 Mb/s signaling appears as 2.05V to 4.55V signaling local to the component driver, with polarity reversing to create +2.5V and -2.5V signaling at the secondary of the transformer. Link pulses appear similar to 10 Mb/s signaling, without polarity switching. Refer to Figure 7.

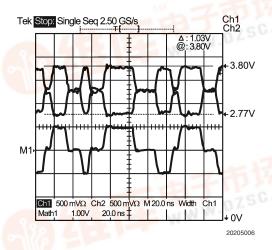


FIGURE 6. Sample 100 Mb/s Waveform

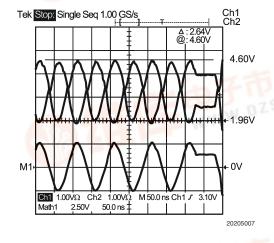


FIGURE 7. Sample 10 Mb/s Waveform



# 4.0 Transformerless Configuration

#### 间DP**83%4%/**轉应商

In 100 Mb/s mode configured with blocking capacitors, the transmit DC bias voltage shifts. A "zero" state in 100 Mb/s operation corresponds to a DC bias voltage near 2.3V. Data signals appear as 1.8V to 2.8V signaling across the differential pair, which is within the operating range of the 100 Mb/s transmit drivers. Polarity reversing creates +1V and -1V signaling on the cable side of the capacitors. Refer to Figure 8.

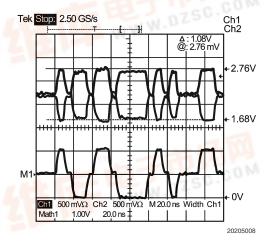


FIGURE 8. Sample 100 Mb/s Waveform With No Transformer

In 10 Mb/s mode, the differential driver is biased to Vdd. When configured with blocking capacitors, each side of the differential pair operates separately, each dropping 2.5V across the differential load while the opposite signal remains fixed at Vdd. Thus, each signal switches between 3.3V and 0.8V, and 10 Mb/s signaling is asymmetrical (not balanced). On the cable side of the capacitors, the signal appears as +2.5V and -2.5V differential pulses. Link pulses appear as 2.5V pulses which do not switch polarity. Refer to Figure 9.

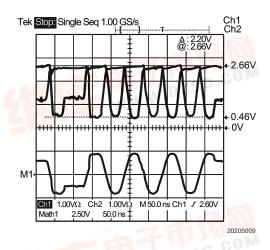


FIGURE 9. Sample 10 Mb/s Waveform With No Transformer

While 10 Mb/s signaling is operational within these signal voltage ranges, it is not guaranteed. Specifically, the 0.8V operating point is not guaranteed to function normally under all conditions. Also, differential signaling in 10 Mb/s transformerless operation is not symmetrical as it is when a transformer is used, so there is added EMI radiation risk. Therefore, it is recommended that transformerless operation be restricted to forced 100 Mb/s modes, with autonegotiation disabled.

#### **4.2 RECEIVE REQUIREMENTS**

PHYTER component 100 Mb/s and 10 Mb/s receivers are self biased to Vdd, so the signals which appear at the receive side of the blocking caps are identical to the signals seen using a transformer.

Because the automatic MDIX switching feature is based on receive signal detection, MDIX functionality is not adversely affected by the use of blocking capacitors.

### 5.0 Capacitor Selection

Capacitors used for transformerless applications must be non-polarized, and meet application specific AC and DC isolation requirements. High voltage multi-layer ceramic capacitors are readily available for this purpose. With regard to choosing the value of the blocking capacitors, ANSI INCITS 263-1995 TP-PMD specifies that the physical layer must meet return loss standards for both magnitude and phase. For an unshielded twisted pair, the return loss must be greater than 16 dB, with an impedance range of 100  $\pm$  15 ohms, nominally resistive with a phase angle less than 3° over the frequency range of 2 to 80 Mhz.

Since the impedance of a series capacitor is greatest at low frequencies, the 2 MHz operating point is of special interest. The minimum calculated capacitance value which meets this standard at 2 MHz is 30.42 nF. 33 nF is recommended because it represents the nearest standard value available, and is proven acceptable based on validation testing. The derivation for determining this value is attached as an appendix.

While there is no theoretical upper limit to the capacitance value, DC isolation specifications for non-polarized capacitors tend to decrease as capacitance increases.



www.national.com 4


# 6.0 Topology Considerations

Type and the work configurations consist of two physical layer nodes connected through a cable with transformers at each node.

It is possible to connect a capacitive isolated node, to a capacitive coupled, transformer coupled node or a node with no isolation. The latter implies there will be only one set of blocking caps between two nodes. Refer to *Figure 10*. Connections can be made using 100 ohm twisted CAT5 cables or directly on PCB boards using 50 ohm traces (as in backplane applications).

While any of these possible topologies work well when connection distances are shorter than 1 meter, each topology may present application specific risks as connection distances increase.

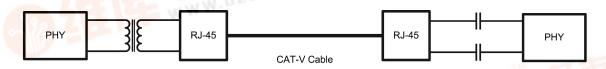
Therefore, network connections configured using non-typical topologies need to be verified at the specific application level.



A: Cable Cap to Transformer Topology



B: Cable Cap to Cap Topology

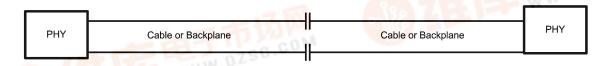

C: Single Cap Isolation Topology

20205020

FIGURE 10. Non-typical Network Connection Topologies

#### 7.0 Validation Results

To validate the performance of the transformerless implementation, a DP83848 device was configured as represented schematically in *Figure 5* using both 0.1 uF and 33 nF capacitors. Standard IEEE compliance testing as well as bit error rate testing was performed. Bit error testing was performed with a traditional link partner, which utilized magnetics, and with a transformerless link partner.

IEEE compliance testing was performed on the transformerless interface with both straight and crossover cables. The results showed compliance for critical 100 Mb/s mode parameters (jitter, tx/rx return loss, Vod). Other IEEE tests, which are designed to simulate worst-case cable loading, did not pass, thus supporting the recommendation to use short distance configurations in non-typical transformerless appli-

In 10 Mb/s mode, as predicted, many of the tests resulted in non-compliance results. For the bit error rate tests con-

ducted, error free operation of the transformerless circuit was obtained up to 100 meters in 10 Mb/s mode and in 100 Mb/s mode.

In each test, the link partners were configured to operate in both 10 Mb/s and 100 Mb/s modes, and the circuit under test was allowed to auto-negotiate with its link partner.

The following bit error rate test parameters were used:

- Packet lengths: 1514 bytes (+CRC)
- Minimum Interframe Gap (960 ns for 100 Mb/s, 9.6 us for 10 Mb/s)
- 10 million packets sent (100 Mb/s mode)
- 1 million packets sent (10 Mb/s mode)
- Full-duplex
- Auto-MDIX
- · Cable lengths: up to 100 m
- Energy Detect Disabled (default state)



## 7.0 Validation Results (Continued)

nF capacitors were similar. The following figures represent the 100 Mb/s passing results using 33 nF capacitors. In each diagram, the bold vertical lines represent passing limits.

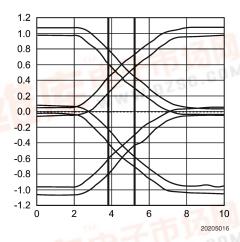


FIGURE 11. 100 Mb/s Jitter with 33 nf Blocking Capacitors

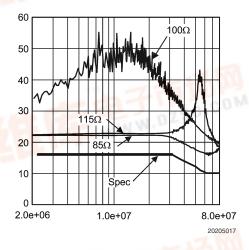


FIGURE 12. 100 Mb/s Receive Return Loss with 33 nf
Blocking Capacitors

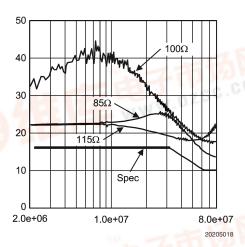


FIGURE 13. 100 Mb/s Transmit Return Loss with 33 nf
Blocking Capacitors

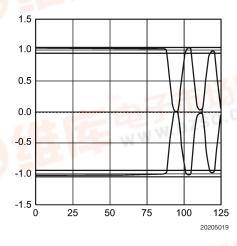


FIGURE 14. 100 Mb/s Vod with 33 nf Blocking Capacitors

# 8.0 Summary

In summary, this paper presents recommendations for configuring PHYTER products in non-typical transformerless network applications. Recommendations include the use of 33 nF or larger non-polarized capacitors for DC isolation from a network cable, with a minimum DC isolation rating which suits the individual application. Because transformerless configuration results in non-symmetrical 10 MB/s signaling which exceeds the recommended operating range of the 10 Mb/s transmission drivers, it is recommended that forced 100 Mb/s operation be utilized.

In support of these recommendations, operating conditions required by PHYTER product component transmit and receive functions, were presented. Test results were presented which validate PHYTER bit error and IEEE standard compliance performance.

www.national.com 6

# 9.0 Appendix A: Calculating the Minimum Recommended Capacitance

The hand wing sories that the calculated using the following equation for return loss,

Return Loss = -20 Log |(Zload - Zo)| / |(Zload + Zo)|

Where:

Return Loss = 16 dB Zo = 100 ohms

Zload =  $100 + 1/j\omega C + 1/j\omega C$  ohms (from circuit in *Figure 5*).

Substituting the above values into Equation 1 and solving, results in:

$$\omega C = 0.0622$$

At 2 MHz, the minimum series blocking capacitor value, C, would be 4.95 nF based on the return loss requirement.

The ANSI standard also specifies a limitation on the phase angle of the load (+/-3° maximum). For the phase calculation, a 100 ohm load at -3° phase angle produces a worst case capacitance.

(2)

$$2 * 1/\omega C = 100 \sin(-3^\circ) = -5.233$$
 (3

Solving Equation 3 for C at 2 MHz gives 30.42 nF, which represents minimum capacitor value required to meet the phase specification. The recommendation of 33 nF is the nearest standard value generally available, and proved acceptable based on validation testing.





National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

#### LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- 1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- 2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

#### **BANNED SUBSTANCE COMPLIANCE**

National Semiconductor follows the provisions of the Product Stewardship Guide for Customers (CSP-9-111C2) and Banned Substances and Materials of Interest Specification (CSP-9-111S2) for regulatory environmental compliance. Details may be found at: www.national.com/quality/green.

Lead free products are RoHS compliant.



National Semiconductor Americas Customer Support Center

Email: new.feedback@nsc.com Tel: 1-800-272-9959

www.national.com

**National Semiconductor** Europe Customer Support Center Fax: +49 (0) 180-530 85 86

Email: europe.support@nsc.com Deutsch Tel: +49 (0) 69 9508 6208 English Tel: +44 (0) 870 24 0 2171 Français Tel: +33 (0) 1 41 91 8790

**National Semiconductor** Asia Pacific Customer Support Center Email: ap.support@nsc.com **National Semiconductor** Japan Customer Support Cente Fax: 81-3-5639-7507 Email: jpn.feedback@nsc.com Tel: 81-3-5639-7560

