LM25088 Evaluation Board

National Semiconductor Application Note 1931 Ajay Hari December 8, 2008



M25088 Evaluation Board

AN-193

com

www.national.com

Introduction

The LM25088 evaluation board is designed to provide the design engineer with a fully functional power converter based on Emulated Current Mode Control to evaluate the LM25088 controller IC. The LM25088 evaluation board is available in two versions (like the LM25088 controller): the LM25088-1

evaluation board provides $\pm 5\%$ oscillator frequency dithering to reduce EMI and the LM25088-2 evaluation board provides hiccup mode restart to reduce over load stress. Both the evaluation boards share the same layout except for silkscreen. The printed circuit board consists of 2 layers, 2 ounce of copper top and bottom and the board size is 2.55x1.5x0.5 inches.

| Specification | LM25088-1 | LM25088-2 |
|---------------------------|------------------------------------|---------------------|
| Input Voltage Range | 5.5V to 36V | 5.5V to 36V |
| Output Voltage | 5.0V | 5.0V |
| Max. Average Load Current | 7A | 7A |
| Load Regulation | 2% | 2% |
| Current Limit Type | Cycle-by-cycle current limit | Hiccup Mode Restart |
| Frequency | 250 kHz (±5% Oscillator Dithering) | 250 kHz |

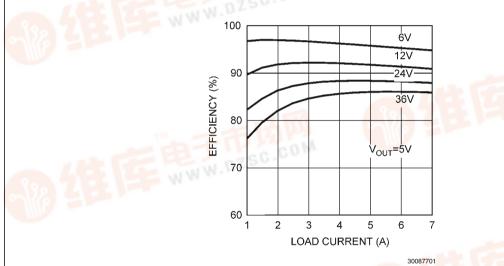


FIGURE 1. Typical Efficiency Curves of LM25088-1 and LM25088-2 Evaluation Boards

Powering and Loading 间LM25088供应商 Considerations

Read this entire page prior to attempting to power the evaluation board.

QUICK SETUP PROCEDURE

Step 1: Set the power supply current limit to 10A. Turn off the power supply. Connect the power supply to the VIN terminals. **Step 2:** Connect the load, with a 7A capability, to the VOUT terminals.

Step 3: Slowly increase the load while monitoring the output, VOUT should be in regulation with a nominal 5V output.

Step 4: Slowly sweep the input voltage from 5.5V to 36V, VOUT should remain in regulation with a nominal 5V output.

Step 5: Temporarily short the EN pin to check the shutdown function, Also, EN pin can be set between 0.4V and 1.2V, for example, by shorting EN pin to ground with a diode, to check the standby function.

Step 6: Increase the load beyond the rated current to check the current limiting. The output current should limit at approximately 10A. The LM25088-1 board will enter cycle-by-cycle current limiting, while LM25088-2 is configured for a hiccup mode restart. Cooling is critical in this step.

AIR FLOW

Prolonged operation with high input voltage (>24V) at full load will cause the LM25088 and MOSFETs to overheat and could potentially result in thermal shutdown. A fan with a minimum of 100LFM should always be used to cool the LM25088 evaluation board.

POWERING UP

It is suggested that the load be kept low during the first power up. Set the current limit of the source supply to provide about 1.5 times the anticipated wattage of the load. A quick efficiency check is the best way to confirm that everything is operating properly. If something is amiss one can be reasonably sure that it will affect the efficiency adversely. Few parameters can be correct in a switching power supply without creating losses and potentially damaging heat.

OVER CURRENT PROTECTION


The LM25088-1 and LM25088-2 evaluation boards are both configured with over-current protection schemes. The LM25088-1 employs a cycle-by-cycle current limiting, while the LM25088-2 is configured for a hiccup mode restart. Please refer the LM25088 datasheet for more information on RES pin.

SYNCHRONIZATION

A Sync pin has been provided on the evaluation board. This pin can be used to synchronize the LM25088 to an external clock. It is recommended not to exceed 500 kHz while synchronizing. Refer the LM25088 datasheet for complete information.

ACTIVE LOADS

When using electronic load, it is strongly recommended to power up the evaluation board at light load and then slowly increase the load. This is necessary as most of the electronic loads do not draw any current till the output reaches an internally set point; this can result in soft-start function to not work as desired and can trip the current sense comparator. Electronic loads, in general, are best suited for monitoring steady state waveforms. If it is desired to power up the evaluation board at maximum load, resistor banks can be used. This will ensure a soft-start and evaluation board will perform as desired. Ensure that there is sufficient cooling for both the resistor banks and the LM25088 evaluation board, while running at full load.

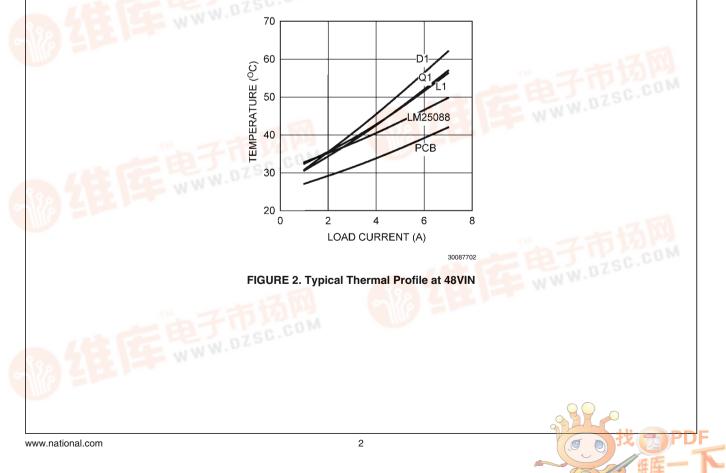

Typical Performance Waveforms of LM2508844 W25088425088-2

Evaluation Boards


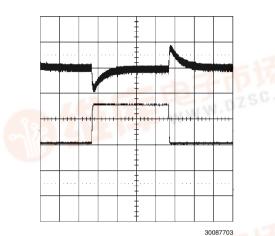


FIGURE 3. Transient Response

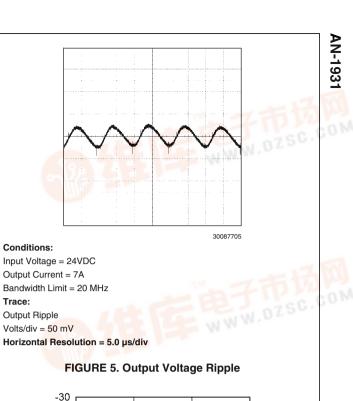

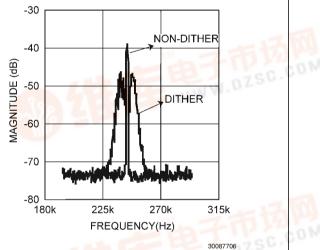


FIGURE 6. Conducted Emissions Measured at the Input of a LM25088-1 Evaluation Board

Conditions: Input Voltage = 24VDC Output Current = 7A Trace: Output Voltage Volts/div = 1V

Conditions:

Traces:

Amps/div = 2A

Volts/div = 100 mV

Input Voltage = 24VDC Output Current = 4A to 7A Bandwidth Limit = 20 MHz

Bottom Trace: Output Current

Top Trace: Output Voltage response


Horizontal Resolution = 500 µs/div

FIGURE 4. Soft-Start


30087704

3

PDF #F pdf.dzsc.com

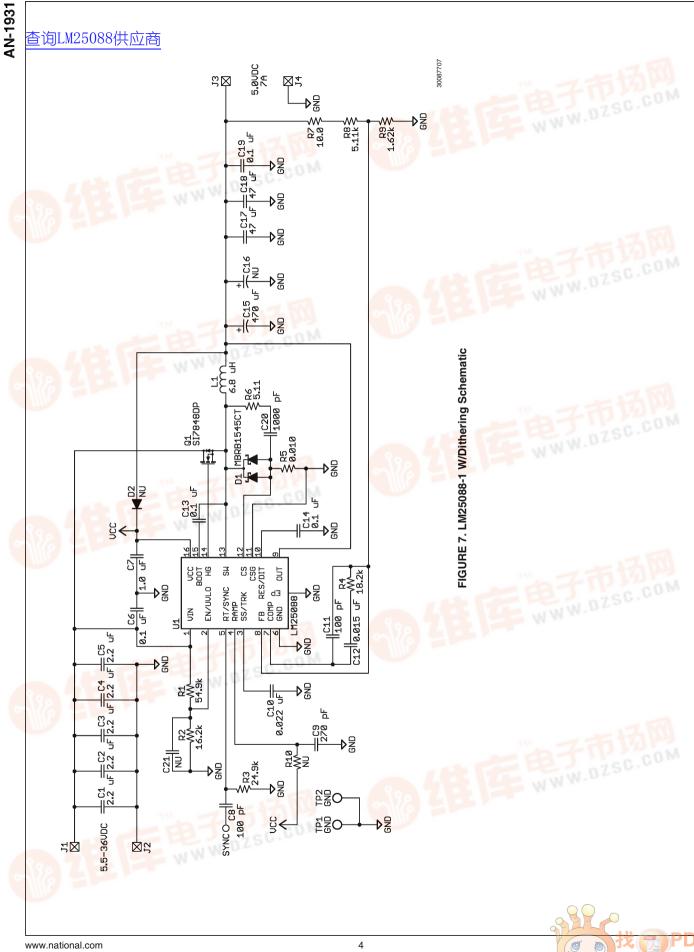



df.dzsc.com

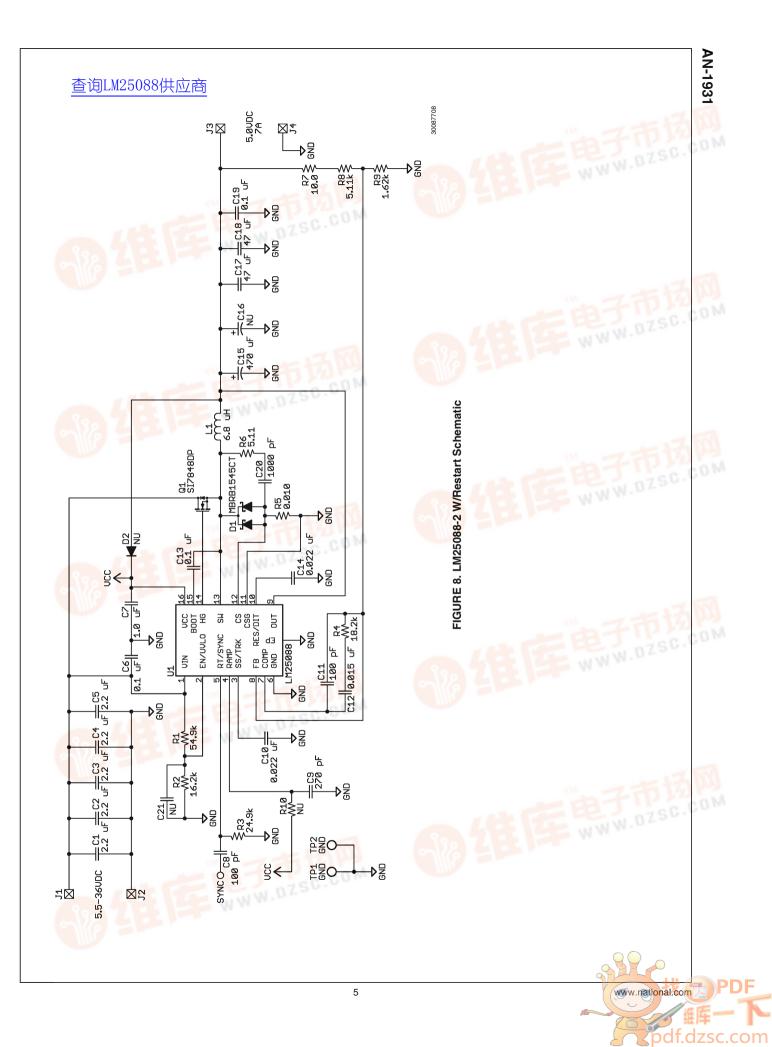

Bill of Materials for LM25088-1 and LM25088-2 Evaluation Boards 查询LM25088供应商

| Part | Value | Package | Manufacturer | Manufacturer Part Number | Description |
|--------------------|---------------------|-----------------------|-----------------|-----------------------------|----------------------------------|
| C1,C2,C3, C4,C5 | 2.2 µF | C1210 | Murata | GRM32ER72A225KA35L | CAP CER 2.2 µF 100V X7R 1210 |
| C6,C19 | 0.1 µF | C0805 | TDK Corporation | C2012X7R2A104K | CAP CER .10 µF 100V X7R 10% 080 |
| C7 | 1μF | C0603 | Murata | GRM188R71C105KA12D | CAP CER 1 µF 16V X7R 0603 |
| C8,C11 | 100 pF | C0603 | AVX Corporation | 06031A101FAT2A | CAP CERM 100 pF 1% 100V NP0 060 |
| C9 | 270 pF | C0603 | Murata | GRM1885C2A271JA01D | CAP CER 270 pF 100V 5% C0G 060 |
| C13 | 0.1 µF | C0603 | Murata | GRM188R72A104KA35D | CAP CER .1 µF 100V X7R 0603 |
| C10 | 0.022 µF | C0603 | Murata | GRM188R71C223KA01D | CAP CER 22000 pF 16V 10% X7R 060 |
| C12 | 0.015 µF | C0603 | Murata | GRM188R71H153KA01D | CAP CER 15000 pF 50V 10% X7R 060 |
| C15 | 470 μF | 0.327x0.327x0.3 03 | Nippon-Chemicon | APXF6R3ARA471MH80G | CAP 470 µF 6.3V ELECT POLY SME |
| C17,C18 | 47 µF | C1210 | Murata | GRM32ER61A476KE20L | CAP CER 47 µF 10V X5R 1210 |
| C20 | 1000 pF | C0805 | Murata | GRM2195C2A102JA01D | CAP CER 1000 pF 100V 5% COG 080 |
| C16 | NU | 0.327x0.327x0.3 03 | NU | NU | NU |
| C21 | NU | C0603 | NU | NU | NU |
| C14 LM25088-1 | 0.1 µF | C0603 | Murata | GRM188R72A104KA35D | CAP CER .1 µF 100V X7R 0603 |
| C14 LM25088-2 | 0.022 μF | C0603 | Murata | GRM188R71C223KA01D | CAP CER 22000 pF 16V 10% X7R 060 |
| D1 | Schottky Diode | D2PAK | On Semi | MBRB1545CT | Schottky Rectifiers 15A 45V |
| D2 | NU | SOD123 | NU | NU | NU |
| L1 | 6.8 µH | HC9 series | Coiltronics | HC9-6R8-R | INDUCTOR HIGH CURRENT 6.8 µH |
| Q1 | MOSFET | SO-8 | Vishay IR | SI7848DP | MOSFET N-CH 40V PWR PAK SO8 |
| R1 | 54.9 kΩ | R0805 | Rohm | MCR10EZHF5492 | RES 54.9 kΩ 1/8W 1% 0805 SMD |
| R2 | 16.2 kΩ | R0603 | Rohm | MCR03EZPFX1622 | RES 16.2 kΩ 1/10W 1% 0603 SMD |
| R3 | 24.9 kΩ | R0603 | Rohm | MCR03EZPFX2492 | RES 24.9 kΩ 1/10W 1% 0603 SMD |
| R4 | 18.2 kΩ | R0603 | Rohm | MCR03EZPFX1822 | RES 18.2 kΩ 1/10W 1% 0603 SMD |
| R5 | 10 mΩ | R0815 | Susumu Co Ltd | RL3720WT-R010-F | RES .01Ω 1W 1% 0815 SMD |
| R6 | 5.1Ω | R2512 | Panasonic - ECG | ERJ-1TRQF5R1U | RES 5.1Ω 1W 1% 2512 SMD |
| R7 | 10Ω | R0805 | Rohm | MCR10EZHF10R0 | RES 10.0Ω 1/8W 1% 0805 SMD |
| R8 | 5.11 kΩ | R0603 | Rohm | MCR03EZPFX5111 | RES 5.11 kΩ 1/10W 1% 0603 SMD |
| R9 | 1.62 kΩ | R0603 | Rohm | MCR03EZPFX1621 | RES 1.62 kΩ 1/10W 1% 0603 SMD |
| R10 | NU | R0603 | NU | NU | NU |
| J1,J2,J3, J4 | Terminal_ Turret | 10003 | Keystone | 1509 | Terminal, Turret |
| TP1,TP2 | Slotted test point | | Keystone | 1040 | Terminal test point slotted |
| U1 | PWM IC | TSSOP16_EP | National | LM25088-1/LM25088-2 | ECM Buck Controller |

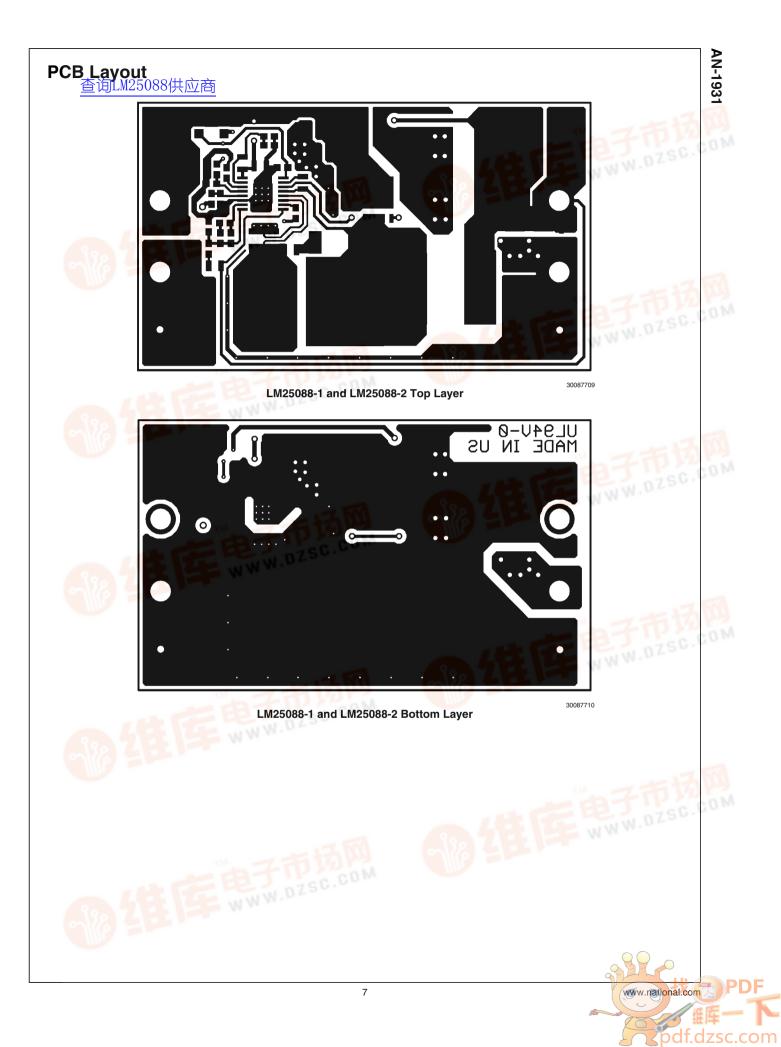

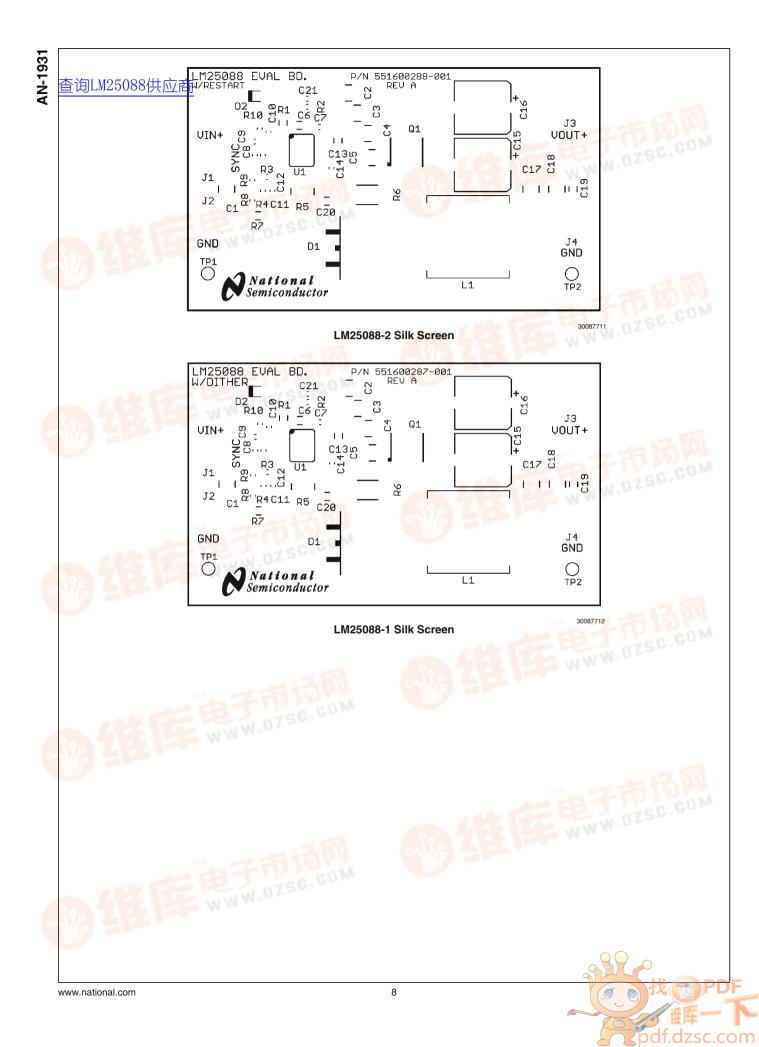



查询LM25088供应商

Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

| Pi | roducts | Design Support | |
|--------------------------------|------------------------------|-------------------------|--------------------------------|
| Amplifiers | www.national.com/amplifiers | WEBENCH® Tools | www.national.com/webench |
| Audio | www.national.com/audio | App Notes | www.national.com/appnotes |
| Clock and Timing | www.national.com/timing | Reference Designs | www.national.com/refdesigns |
| Data Converters | www.national.com/adc | Samples | www.national.com/samples |
| Interface | www.national.com/interface | Eval Boards | www.national.com/evalboards |
| LVDS | www.national.com/lvds | Packaging | www.national.com/packaging |
| Power Management | www.national.com/power | Green Compliance | www.national.com/quality/green |
| Switching Regulators | www.national.com/switchers | Distributors | www.national.com/contacts |
| LDOs 📫 | www.national.com/ldo | Quality and Reliability | www.national.com/quality |
| LED Lighting | www.national.com/led | Feedback/Support | www.national.com/feedback |
| Voltage Reference | www.national.com/vref | Design Made Easy | www.national.com/easy |
| PowerWise® Solutions | www.national.com/powerwise | Solutions | www.national.com/solutions |
| Serial Digital Interface (SDI) | www.national.com/sdi | Mil/Aero | www.national.com/milaero |
| Temperature Sensors | www.national.com/tempsensors | Solar Magic® | www.national.com/solarmagic |
| Wireless (PLL/VCO) | www.national.com/wireless | Analog University® | www.national.com/AU |

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2008 National Semiconductor Corporation

For the most current product information visit us at www.national.com

AN-193

National Semiconductor Americas Technical Support Center Email: support@nsc.com Tel: 1-800-272-9959 National Semiconductor Europe Technical Support Center Email: europe.support@nsc.com German Tel: +49 (0) 180 5010 771 English Tel: +44 (0) 870 850 4288 National Semiconductor Asia Pacific Technical Support Center Email: ap.support@nsc.com National Semiconductor Japan Technical Support Center Email: jpn.feedback@nsc.com