

Small, Wide Input Voltage Range LM2842 Keeps LEDs Cool

National Semiconductor
Application Note 1982
Clinton Jensen
July 15, 2009



Introduction

The world seems to be poised to make the leap to LED lighting. Incandescent has been deemed too inefficient, which it is, and fluorescent lighting often does not achieve the lifetime it claims. Fluorescent also has another set of baggage, dangerous chemicals. So the logical choice that most people believe can take the crown is HB (high brightness) LEDs. HBLEDs are becoming more attractive as the manufacturers of such devices are making great strides in increasing the lumens per watt that they can produce which improves the efficiency. It will not be long before LEDs produce significantly more lumens per watt than current fluorescent lamps.

Two of the main initial areas of focus for replacement with LED lighting are low voltage down lighting and track lighting. These would include replacements for standard sizes such as MR16, PAR20, PAR25, PAR30, and PAR38. National already offers a variety of solutions for driving multiple LEDs beautifully for such applications including the LM342x and LM340x series of LED drivers. But regardless of how the LEDs are driven they have one issue: They produce heat. In these small enclosures a heatsink with free flowing air is often not enough. This forces the designer of the fixture into a situation where some forced air is required. The most practical solutions for a fixture of such size are either a DC fan or a more elegant and rugged solution provided by the Nuventix, Inc. Synjet®. A fan is generally a more cost effective solution and can run off either 5VDC or 12VDC rail but it can be difficult to fit into these enclosures and has a lifetime measuring in the tens of thousands of hours at best. On the other hand the Synjet is designed specifically to fit into each of these enclosures, runs off of 5VDC, and has a lifespan on the order of 100k hours.

The standard inputs for these systems can be either a DC system or an AC system. 12VAC and 24VAC systems have been common for some time for low voltage lighting, but 12VDC and 24VDC systems are making a push and are becoming more common. Since there are many 12V systems it makes for an easier design to drive a 5V cooling mechanism. But since there are multiple systems that could provide a very wide input voltage range, particularly in the case of the AC inputs, it would be nice to have one solution that could take the wide input range and provide the 5V rail while taking up very little space and could easily fit into such enclosures. Fortunately the LM2842 does this quite nicely as does the LM2841 for the smaller fixtures.

The DC input systems offer the easiest and most simple solution as a regulator with a wide input voltage range can take this voltage directly and convert it to a 5V rail. Typical solutions including both the fan and the Synjet require between 100 mA and 600 mA to power them. The LM2841 can supply up to 300 mA for the smaller cooling systems while the LM2842 can supply up to 600 mA for the larger, more powerful cooling systems. Figure 1 shows the LM2842 designed to take either a 12VDC or 24VDC input and provide the 5V rail necessary. The entire solution for driving up to 600 mA only takes about 1/4 square inch of PCB real estate making it easy to fit into any of the retrofit fixtures. The LM2841 would be an identical design for the lower current applications but would allow for a physically smaller inductor and would take up less space.

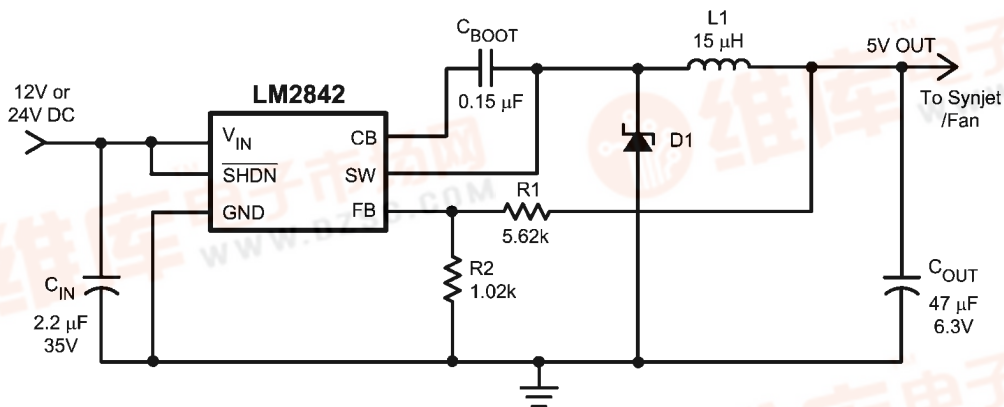


FIGURE 1. DC Input 5VDC Output

However, as mentioned, many 12VAC and 24VAC systems are still in place throughout the world and it is most often desirable to be able to retrofit and use these systems rather than replacing them with a more modern DC system. This means that a design with a wide input voltage range must be used. This can be done rather simply by using a bridge rectifier and a larger amount of input capacitance to form a crude AC-DC

converter. Given line tolerances, a 24VAC system could provide peaks nearing 40V. But you would also like to be able to minimize the input capacitance which would allow the input to fall as low as 10V to 12V. The LM2841 and LM2842 can accommodate such a wide input voltage range with sufficient power supply rejection to keep the output perfectly steady at



5V. Figure 2 and Figure 3 show the circuits for a 12VAC system and a 24VAC system respectively.

It is important to note, the 24VAC input has a higher RMS voltage and therefore the LM2842 draws less current. It also has a higher peak. Due to these facts a lower value input capacitor can be used to maintain an acceptable operating input voltage to the LM2842. Also important to note is that the circuits in Figure 2 and Figure 3 are designed for the full output current of 600 mA. It becomes apparent that if the cooling system uses less current, then less input capacitance could

be used further reducing the circuit size. For example, if the LM2842 were to be substituted with the LM2841 running a maximum of 300 mA of output current then the input capacitance could be cut in half.

This article does not focus on the LED drive circuitry itself since that is a subject for another article. But it does show that thermal management of the LEDs does not have to be a difficult issue if you have the right drive tools available. Visit national.com/LED for more information on National's LED drivers and to use WEBENCH® LED Designer.

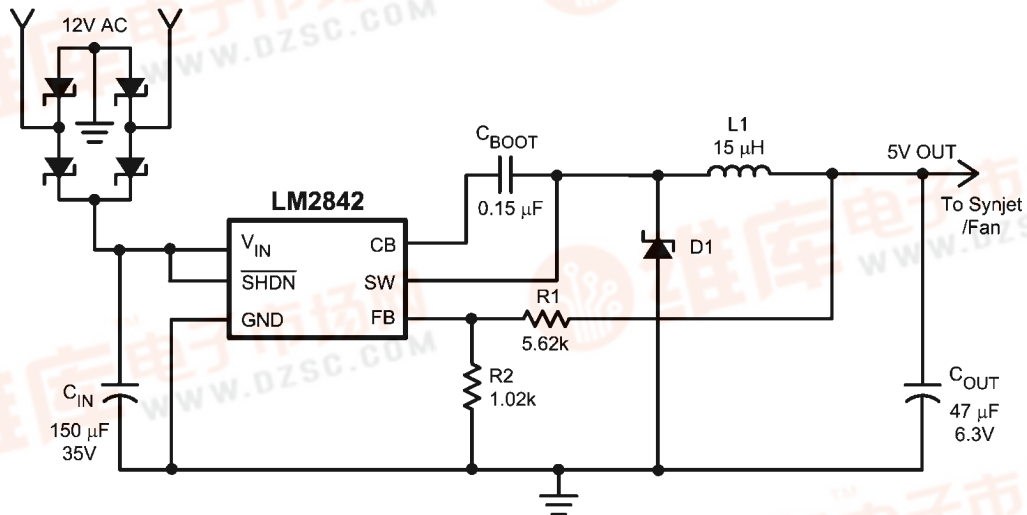


FIGURE 2. 12VAC Input to 5VDC Output


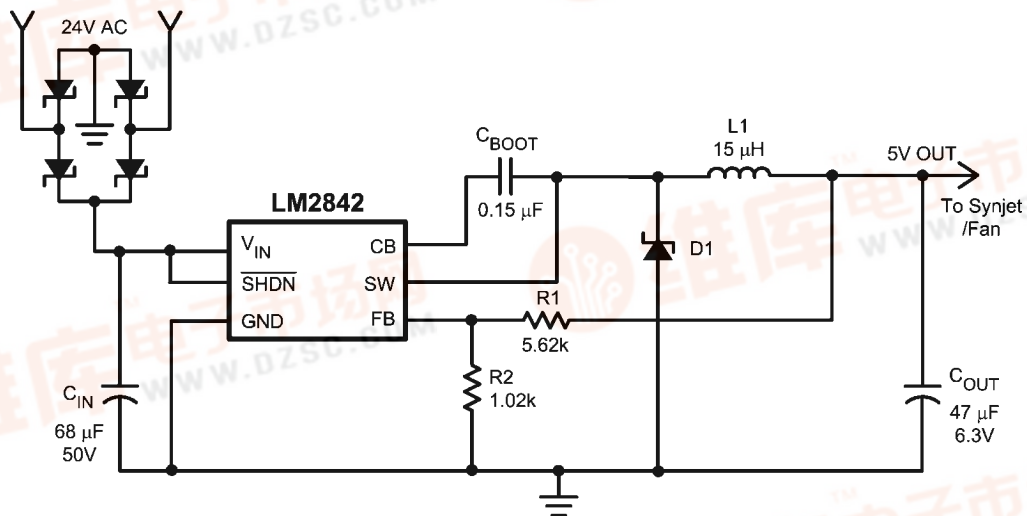


FIGURE 3. 24VAC Input to 5VDC Output

[查询LM2842供应商](#)

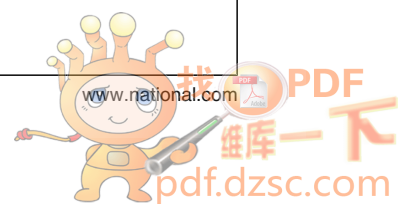

[查询LM2842供应商](#)

Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

| Products | | Design Support | |
|--------------------------------|--|------------------------------|--|
| Amplifiers | www.national.com/amplifiers | WEBENCH® Tools | www.national.com/webench |
| Audio | www.national.com/audio | App Notes | www.national.com/appnotes |
| Clock and Timing | www.national.com/timing | Reference Designs | www.national.com/refdesigns |
| Data Converters | www.national.com/adc | Samples | www.national.com/samples |
| Interface | www.national.com/interface | Eval Boards | www.national.com/evalboards |
| LVDS | www.national.com/lvds | Packaging | www.national.com/packaging |
| Power Management | www.national.com/power | Green Compliance | www.national.com/quality/green |
| Switching Regulators | www.national.com/switchers | Distributors | www.national.com/contacts |
| LDOs | www.national.com/ldo | Quality and Reliability | www.national.com/quality |
| LED Lighting | www.national.com/led | Feedback/Support | www.national.com/feedback |
| Voltage Reference | www.national.com/vref | Design Made Easy | www.national.com/easy |
| PowerWise® Solutions | www.national.com/powerwise | Solutions | www.national.com/solutions |
| Serial Digital Interface (SDI) | www.national.com/sdi | Mil/Aero | www.national.com/milaero |
| Temperature Sensors | www.national.com/tempensors | SolarMagic™ | www.national.com/solarmagic |
| Wireless (PLL/VCO) | www.national.com/wireless | PowerWise® Design University | www.national.com/training |

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2009 National Semiconductor Corporation

For the most current product information visit us at www.national.com



National Semiconductor Americas Technical Support Center
Email: support@nsc.com
Tel: 1-800-272-9959

National Semiconductor Europe Technical Support Center
Email: europe.support@nsc.com

National Semiconductor Asia Pacific Technical Support Center
Email: ap.support@nsc.com

National Semiconductor Japan Technical Support Center
Email: jpn.feedback@nsc.com

