

# LM3406 Evaluation Board

[查询LM3406供应商](#)

National Semiconductor  
Application Note 1750  
Chris Richardson  
September 9, 2008



## Introduction

The LM3406 is a buck regulator controlled current source designed to drive a series string of high power, high brightness

LEDs (HBLEDs) such as the Luxeon™ K2 Emitter at forward currents of up to 1.5A. The converter's output voltage adjusts as needed to maintain a constant current through the LED array.

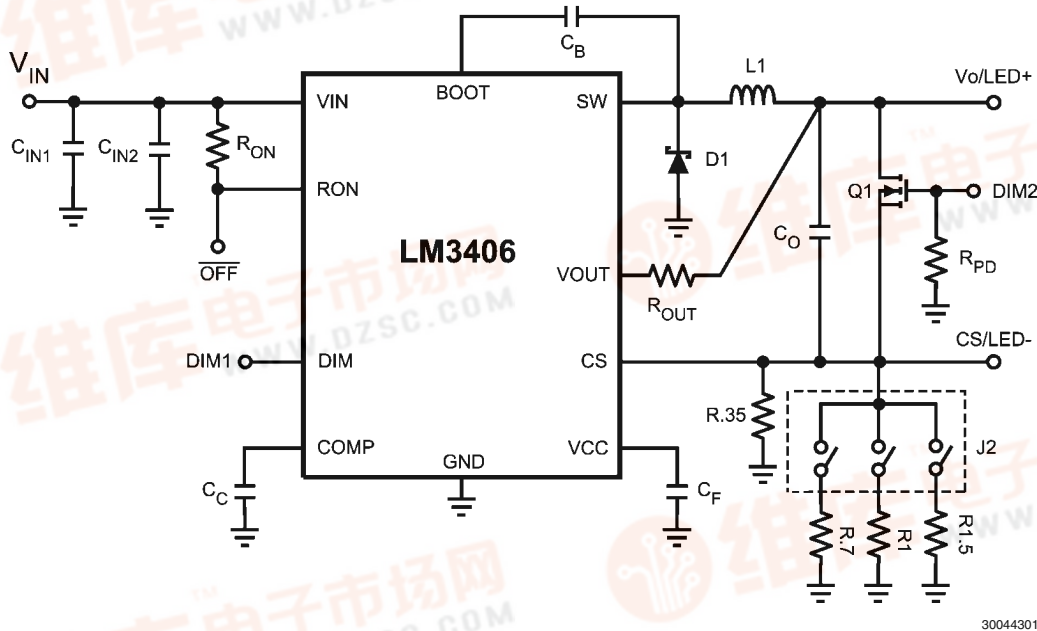


FIGURE 1. Complete Circuit Schematic

## Circuit Performance

The LM3406 circuit and BOM that come pre-installed on the evaluation board are optimized to run from an input voltage of 24V, but the circuit can operate from a wide input voltage range of 6.0V to 42V. The current output ranges from 0.35A to 1.5A. Figure 2 shows the program jumper settings used to program currents of 0.35A, 0.7A, 1A, and 1.5A.

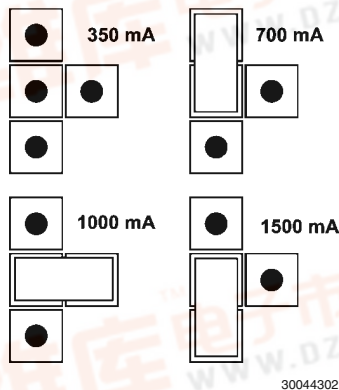


FIGURE 2. Setting Output Current, J2

The LM3406 is a step-down regulator with an output voltage range extending from a  $V_{O-MIN}$  of 200 mV (the reference voltage) to a  $V_{O-MAX}$  determined by the ratio of the minimum off time (typically 230 ns) to the switching frequency. The regulator can maintain the output current through any number of LEDs as long as the combined forward voltage of the array does not exceed  $V_{O-MAX}$ .  $V_{O-MAX}$  can be calculated with the following formula:

$$V_{O-MAX} = V_{IN-MIN} \times (1 - f_{SW} \times t_{OFF-MIN})$$

For example, if  $V_{IN}$  is  $24V \pm 10\%$ , then  $V_{IN-MIN}$  is 21.6V. For a switching frequency of 500 kHz the maximum output voltage for the converter is  $21.6 \times [1 - (5 \times 10^5) \times (230 \times 10^{-9})] = 19.1V$ . Output voltage is calculated with the following formula:

$$V_O = n \times V_F + 0.2V$$

Where 'n' is the number of series-connected LEDs,  $V_F$  is the forward voltage of each LED, and 0.2V represents the voltage across the current sense resistor. For InGaN LEDs (white, blue, blue-green)  $V_F$  is typically 3.5V, and with a limit of  $(19.1 - 0.2) = 18.9V$  the LM3406 could drive as many as five in series. For AlInGaP LEDs (red, orange, amber)  $V_F$  is typically

2.5V, so a  $V_{O-MAX}$  of 18.9V would allow as many as seven to be driven in series.

查询LM3406供应商

## Connecting the LED Array

The LM3406 Evaluation Board includes a female 6-pin SIP connector, **J1**, as well as two standard 94mil turrets for the cathode and anode connections of the LED array. *Figure 3* shows the pinout of **J1**. Solid 18 or 20 gauge wire with about 1 cm of insulation stripped away makes a convenient, solderless connection to **J1**.

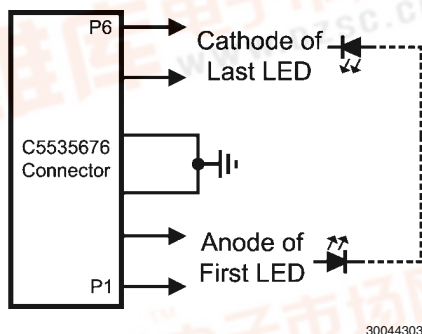


FIGURE 3. 6-Pin LED Connector, J1

## Setting the LED Current

The default forward current  $I_F$  delivered to the LED array when no program jumper is installed on **J2** is 0.35A, set by resistor **R.35**. The higher LED currents are set when the program jumper puts resistors **R.7**, **R1** or **R1.5** in parallel with **R.35**. For users that wish to program a current other than one of the four default levels, or for users who want the best accuracy at

a given current, the program jumper **J2** should be removed, and **R.35** changed according to the following equation:

$$R.35 = 0.2 / I_F$$

This resistor should be rated to handle the power dissipation of the LED current. For example, the closest 5% tolerance resistor to set an LED current of 0.35A is 0.56Ω. In steady state this resistor will dissipate  $(0.35^2 \times 0.56) = 69$  mW, indicating that a resistor with a 1/8W rating is more than capable of dissipating the power.

## Pulse Width Modulation (PWM) Dimming

The **DIM1** terminal on the PCB provides an input for a logic-level pulse width modulation signal for dimming of the LED array. In order to fully enable and disable the LM3406 the PWM signal should have a maximum logic low level of 0.8V and a minimum logic high level of 2.2V. Graphical representations of minimum and maximum PWM duty cycle are illustrated in *Figure 4*. The interval  $t_D$  represents the delay from a logic high at the DIM pin to the rise in output current. The quantities  $t_{SU}$  and  $t_{SD}$  represent the time needed for the output current to slew up to steady state and slew down to zero, respectively. It is important to note that  $t_D$  is a property of the LM3406 and remains fixed in all applications. The slew rates  $t_{SU}$  and  $t_{SD}$  are a function of the external circuit parameters  $V_{IN}$ ,  $V_O$ ,  $I_F$ , inductance (L) and the LM3406 parameter  $t_{OFF-MIN}$ . Response times for a circuit driving three white LEDs at 1A from 24V are shown in the Typical Performance Characteristics section, but the user should test every new circuit to determine the actual PWM dimming response.

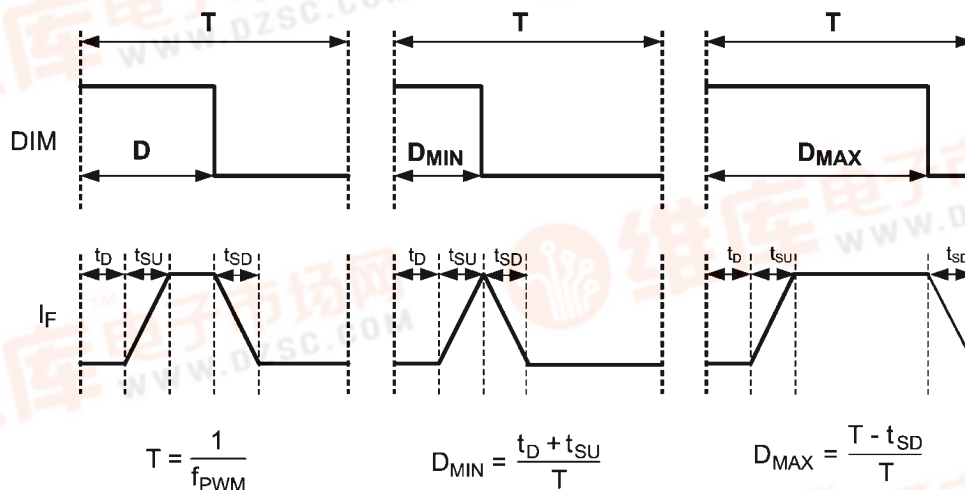


FIGURE 4. PWM Dimming Limits

The logic of **DIM1** is active low, hence the LM3406 will deliver regulated output current when the voltage at **DIM1** is high, and the current output is disabled when the voltage at **DIM1** is low. Connecting a constant logic low will disable the output. Note that an internal pullup ensures that the LM3406 is enabled if the DIM pin is open-circuited. The **DIM1** function disables only the power MOSFET, leaving all other circuit

blocks functioning to minimize the converter response time,  $t_D$ .

The **DIM2** terminal provides a second method for PWM dimming by connecting to the gate of MOSFET **Q1**. **Q1** provides a parallel path for the LED current. Shunting the output current through a parallel MOSFET reduces the PWM dimming delays because the inductor current remains continuous, providing faster response time for higher frequency and/or

greater resolution in the PWM dimming signal. The trade-off in this method is that the full current flows through **Q1** while the LED is off, resulting in lower efficiency. The standard BOM of the LM3406 evaluation board includes an output capacitor to reduce output current ripple, but the drawback of this output capacitor is that it causes significant delays when using parallel MOSFET dimming. The output capacitor should be removed to take full advantage of parallel MOSFET dimming.

The logic of **DIM2** is active high, hence the regulated output current flows through the LED array when the voltage at **DIM2** is low, and the current flows through the shunt FET when the voltage at **DIM2** is high. Connecting a constant logic high to the **DIM2** will turn off the LED but will not shut down the LM3406.

## Low Power Shutdown

The LM3406 can be placed into a low power shutdown (typically 240  $\mu$ A) by grounding the **OFF\*** terminal. During normal operation this terminal should be left open-circuit.

## Output Open Circuit

The LM3406 will begin to operate as soon as  $V_{IN}$  is greater than 6V and the DIM and RON pins are not grounded. If the regulator is powered and enabled but no LED array is connected, the output voltage will rise to  $V_{IN}$ . The output of the circuit is rated to 50V (beyond the maximum input voltage) and will not suffer damage, however care should be taken not to connect an LED array if the output voltage is higher than the target forward voltage of the LED array in steady state.

If the LEDs are disconnected or one of the LEDs fails open-circuit while the LM3406 is operating, the output voltage will

experience a surge as the current in the output inductor seeks a discharge path. The output capacitor (if present) can absorb some of this energy, however circuits with little or no output capacitance can experience a voltage spike that exceeds the rating of the VOUT pin. The evaluation board uses a 10 k $\Omega$  resistor in series with the VOUT pin to limit current flowing into the pin. Alternatively, a diode connected from  $V_{IN}$  to  $V_O$  as shown in Figure 5 will clamp the spike to  $V_{IN}$  plus a diode drop.

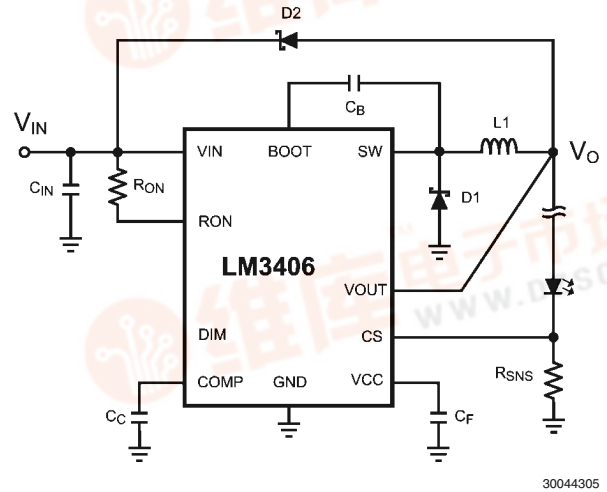


FIGURE 5. Schottky Diode Protection for Open-Circuit

## Bill of Materials

ID	Part Number	Type	Size	Parameters	Qty	Vendor
U1	LM3406	Buck LED Driver	eTSSOP-14	42V, 1.5A	1	NSC
Q1	Si3458DV	N-MOSFET	SOT23-6	60V, 2.8A	1	Vishay
D1	CMSH2-60M	Schottky Diode	SMA	60V, 2A	1	Central Semi
L1	VLF10045T-330M2R3	Inductor	10 x 10 x 4.5mm	33 $\mu$ H, 2.3A, 70 m $\Omega$	1	TDK
Cin1 Cin2	C4532X7R1H685M	Capacitor	1812	6.8 $\mu$ F, 50V	2	TDK
Co	C3216X7R1H474M	Capacitor	1206	470 nF, 50V	1	TDK
Cf ,Cc	VJ0603Y104KXXAT	Capacitor	0603	100 nF 10%	2	Vishay
Cb	VJ0603Y223KXXAT	Capacitor	0603	22 nF 10%	1	Vishay
R3.5	ERJ6RQFR56V	Resistor	0805	0.56 $\Omega$ 1%	1	Panasonic
R.7	ERJ6RQFR62V	Resistor	0805	0.62 $\Omega$ 1%	1	Panasonic
R1	ERJ6RQFR30V	Resistor	0805	0.3 $\Omega$ 1%	1	Panasonic
R1.5	ERJ6RQFR16V	Resistor	0805	0.16 $\Omega$ 1%	1	Panasonic
Ron	CRCW08051433F	Resistor	0805	143k $\Omega$ 1%	1	Vishay
Rpd Rout	CRCW06031002F	Resistor	0603	10 k $\Omega$ 1%	2	Vishay
OFF* DIM1 DIM2	160-1512	Terminal	0.062"		3	Cambion
VIN GND CS/LED- Vo/LED+	160-1026	Terminal	0.094"		2	Cambion




## Typical Performance Characteristics

查询LM3406供应商


$V_{IN} = 24V$ ,  $I_F = 1A$ ,  $T_A = 25^\circ C$ , and the load consists of three InGaN LEDs in series unless otherwise noted.

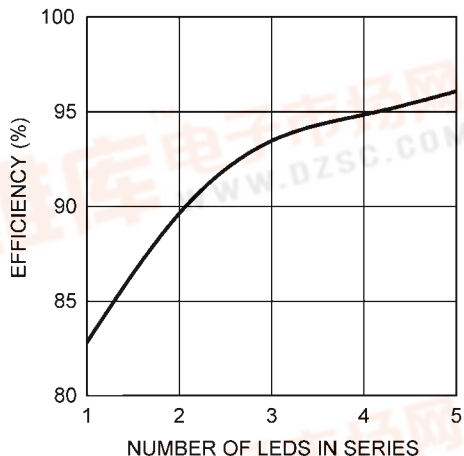Efficiency Vs. Number of InGaN LEDs in Series




30044308

Efficiency Vs. Output Current

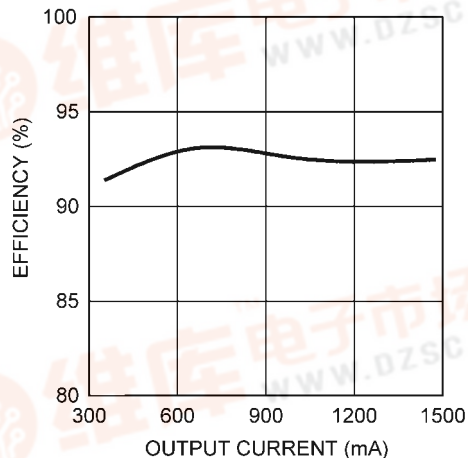


30044309

$I_F$  vs  $V_{IN}$

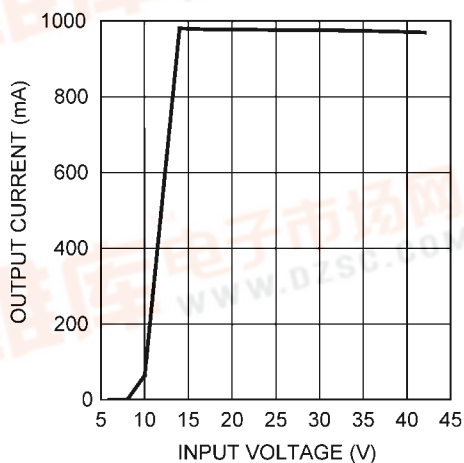


30044310

$I_F$  vs  $T_A$

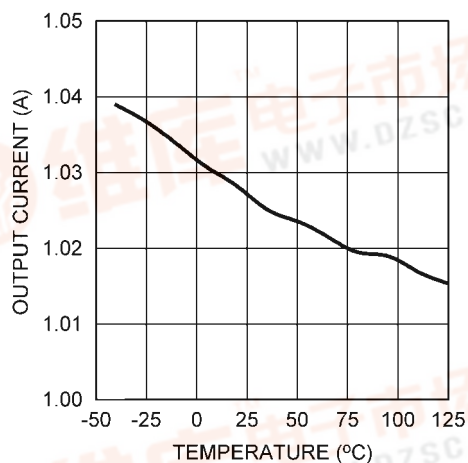


30044311

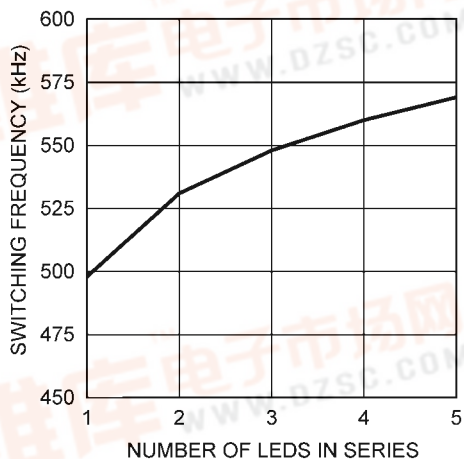Switching Frequency vs Number of InGaN LEDs in Series




30044312

Switching Frequency vs  $V_{IN}$

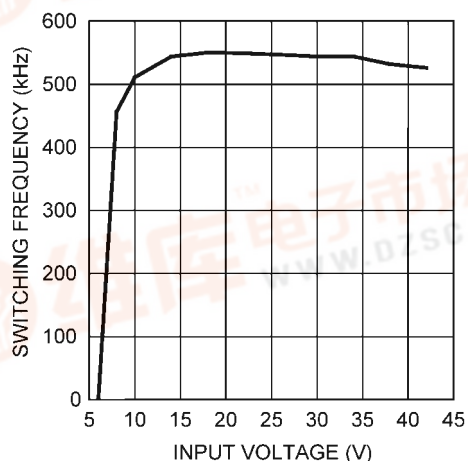


30044313

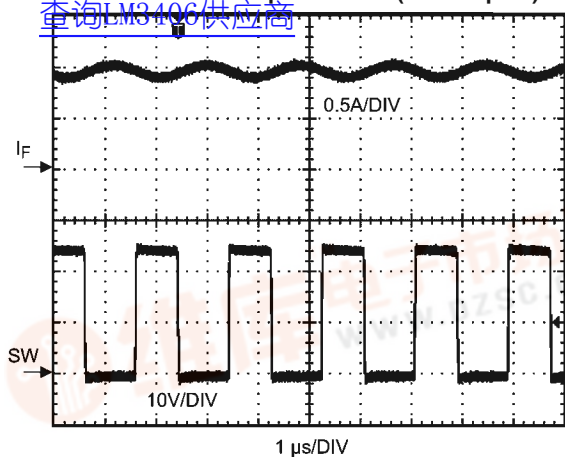Switch Node and Output Current (DC Coupled)




30044314

Output Current (AC Coupled)

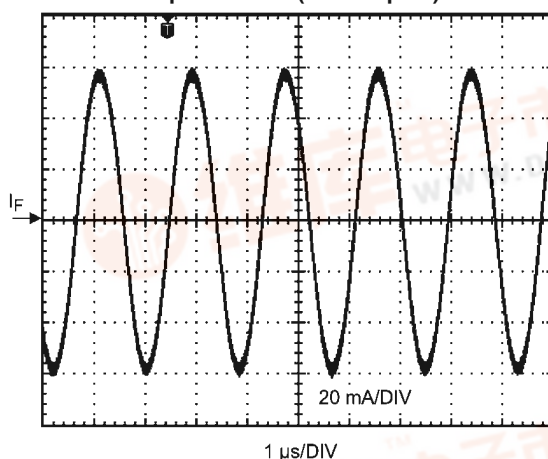


30044315

DIM1 Response (Rising)

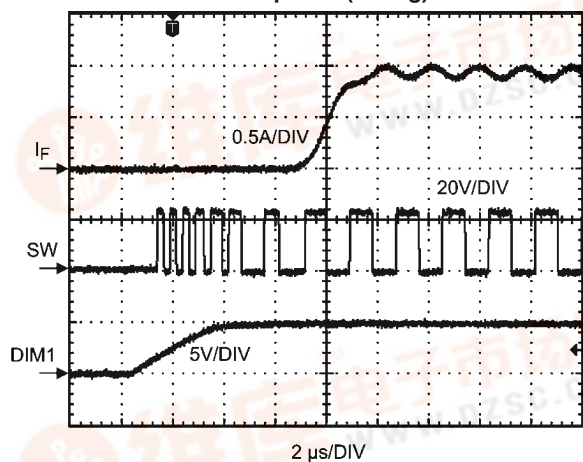


30044316

DIM1 Response (Falling)

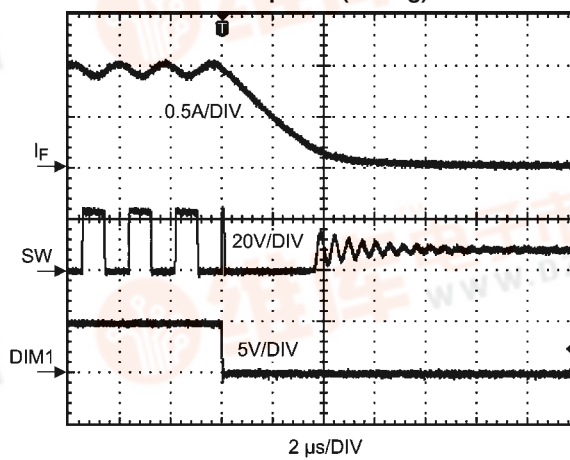


30044317

Start Up using OFF Terminal

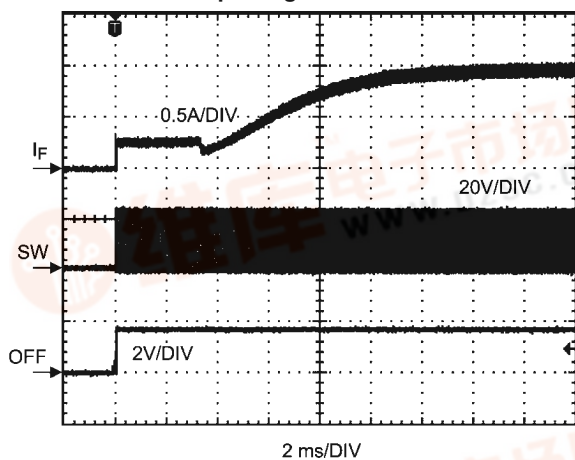

30044318


Shutdown using OFF Terminal

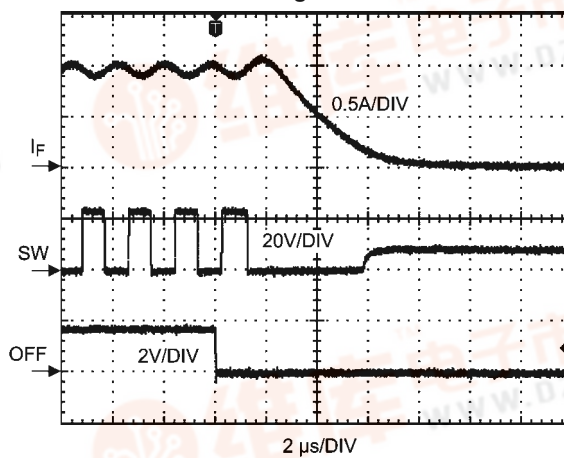

30044319


# Layout

[查询LM3406供应商](#)

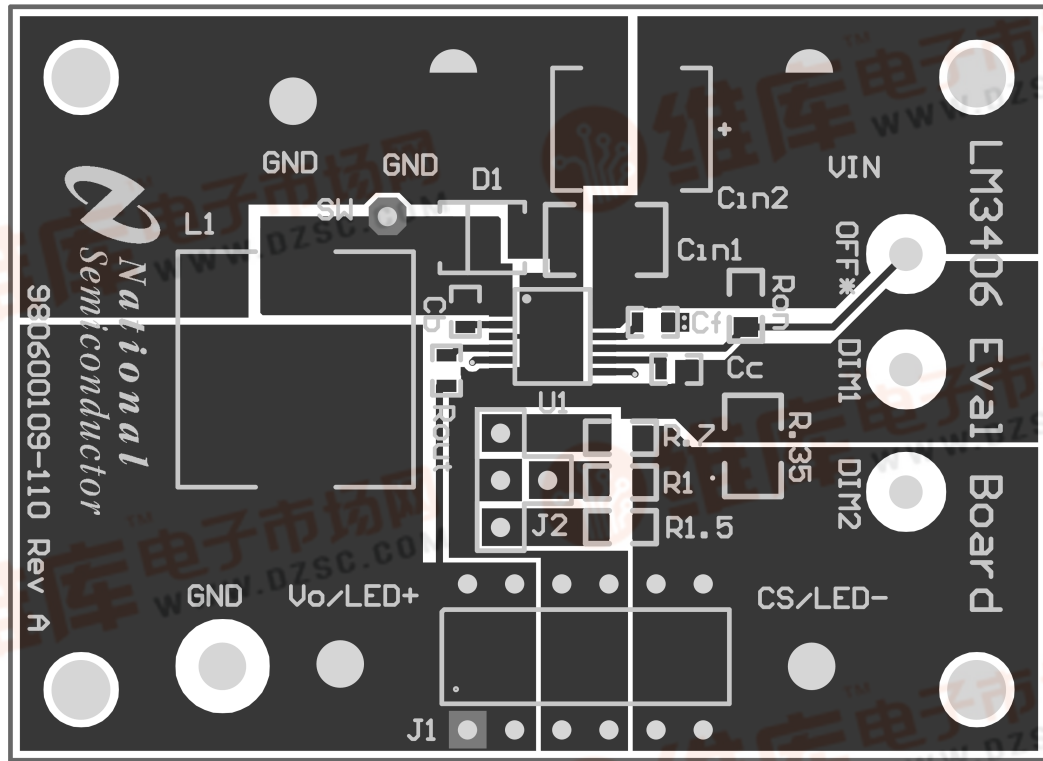

Top Layer and Top Overlay

30044306

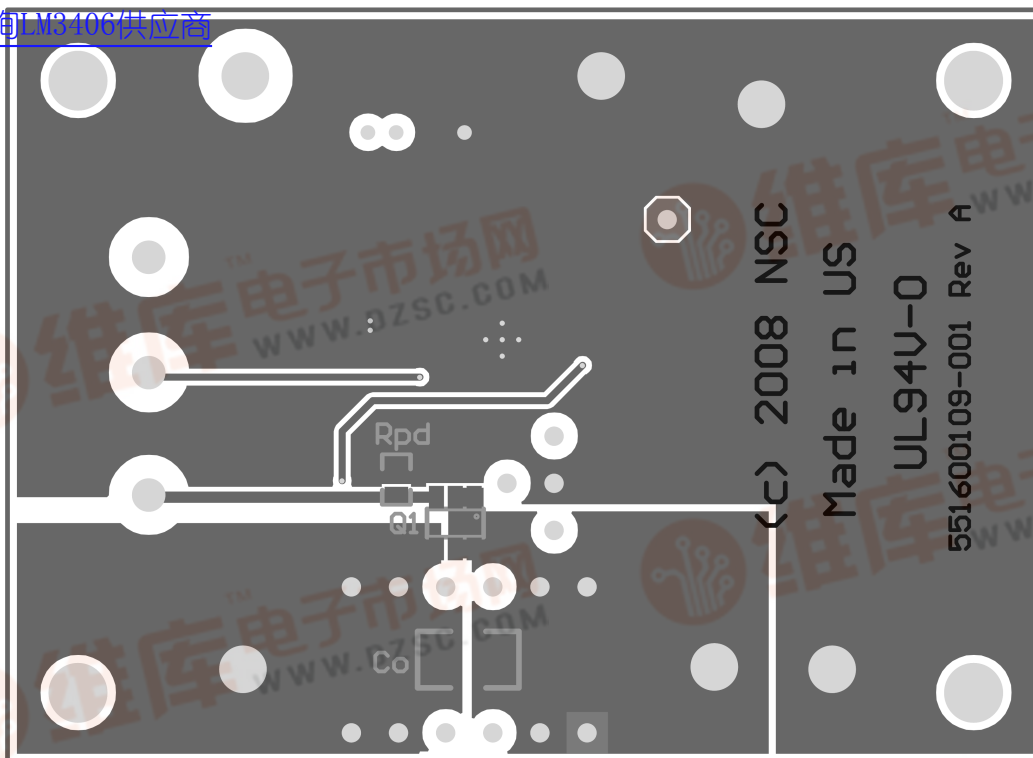[查询LM3406供应商](#)

Bottom Layer and Bottom Overlay

30044307



[查询LM3406供应商](#)

## Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Products		Design Support	
Amplifiers	<a href="http://www.national.com/amplifiers">www.national.com/amplifiers</a>	WEBENCH	<a href="http://www.national.com/webench">www.national.com/webench</a>
Audio	<a href="http://www.national.com/audio">www.national.com/audio</a>	Analog University	<a href="http://www.national.com/AU">www.national.com/AU</a>
Clock Conditioners	<a href="http://www.national.com/timing">www.national.com/timing</a>	App Notes	<a href="http://www.national.com/appnotes">www.national.com/appnotes</a>
Data Converters	<a href="http://www.national.com/adac">www.national.com/adac</a>	Distributors	<a href="http://www.national.com/contacts">www.national.com/contacts</a>
Displays	<a href="http://www.national.com/displays">www.national.com/displays</a>	Green Compliance	<a href="http://www.national.com/quality/green">www.national.com/quality/green</a>
Ethernet	<a href="http://www.national.com/ethernet">www.national.com/ethernet</a>	Packaging	<a href="http://www.national.com/packaging">www.national.com/packaging</a>
Interface	<a href="http://www.national.com/interface">www.national.com/interface</a>	Quality and Reliability	<a href="http://www.national.com/quality">www.national.com/quality</a>
LVDS	<a href="http://www.national.com/lvds">www.national.com/lvds</a>	Reference Designs	<a href="http://www.national.com/refdesigns">www.national.com/refdesigns</a>
Power Management	<a href="http://www.national.com/power">www.national.com/power</a>	Feedback	<a href="http://www.national.com/feedback">www.national.com/feedback</a>
Switching Regulators	<a href="http://www.national.com/switchers">www.national.com/switchers</a>		
LDOs	<a href="http://www.national.com/ldo">www.national.com/ldo</a>		
LED Lighting	<a href="http://www.national.com/led">www.national.com/led</a>		
PowerWise	<a href="http://www.national.com/powerwise">www.national.com/powerwise</a>		
Serial Digital Interface (SDI)	<a href="http://www.national.com/sdi">www.national.com/sdi</a>		
Temperature Sensors	<a href="http://www.national.com/tempsensors">www.national.com/tempsensors</a>		
Wireless (PLL/VCO)	<a href="http://www.national.com/wireless">www.national.com/wireless</a>		

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

### LIFE SUPPORT POLICY

**NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION.** As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2008 National Semiconductor Corporation

For the most current product information visit us at [www.national.com](http://www.national.com)



**National Semiconductor  
Americas Technical  
Support Center**  
Email: [support@nsc.com](mailto:support@nsc.com)  
Tel: 1-800-272-9959

**National Semiconductor Europe  
Technical Support Center**  
Email: [europe.support@nsc.com](mailto:europe.support@nsc.com)  
German Tel: +49 (0) 180 5010 771  
English Tel: +44 (0) 870 850 4288

**National Semiconductor Asia  
Pacific Technical Support Center**  
Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

**National Semiconductor Japan  
Technical Support Center**  
Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)