

# LM3881 Power Sequencer Evaluation Board

查询LM3881供应商

National Semiconductor  
Application Note 1785  
Timothy Hegarty  
August 27, 2009



## Introduction

The LM3881 evaluation board has been designed to permit the designer to connect it directly to the Enable or Remote ON/OFF pins of power supply devices of an existing system to facilitate system sequencing. The block diagram of a typical system application is given in [Figure 1](#).

Upon enabling the device, the three open drain output flags will rise in sequential order, 1-2-3. Once the part is disabled, the shutdown sequence will occur in reverse order 3-2-1. Therefore the last power supply that started up will be the first to shutdown.


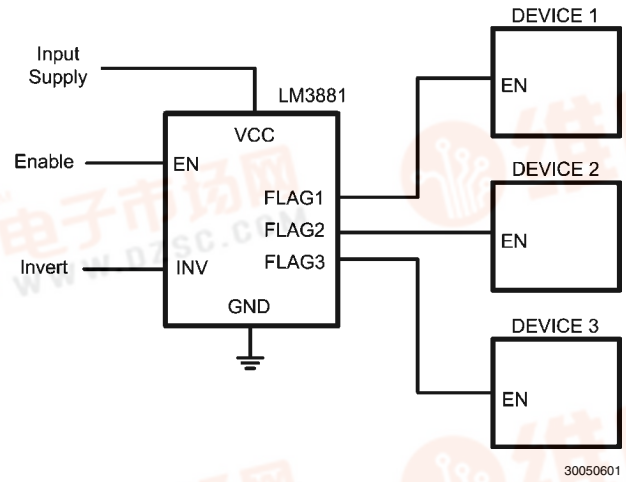


FIGURE 1. Typical System Application Using LM3881 Sequencer
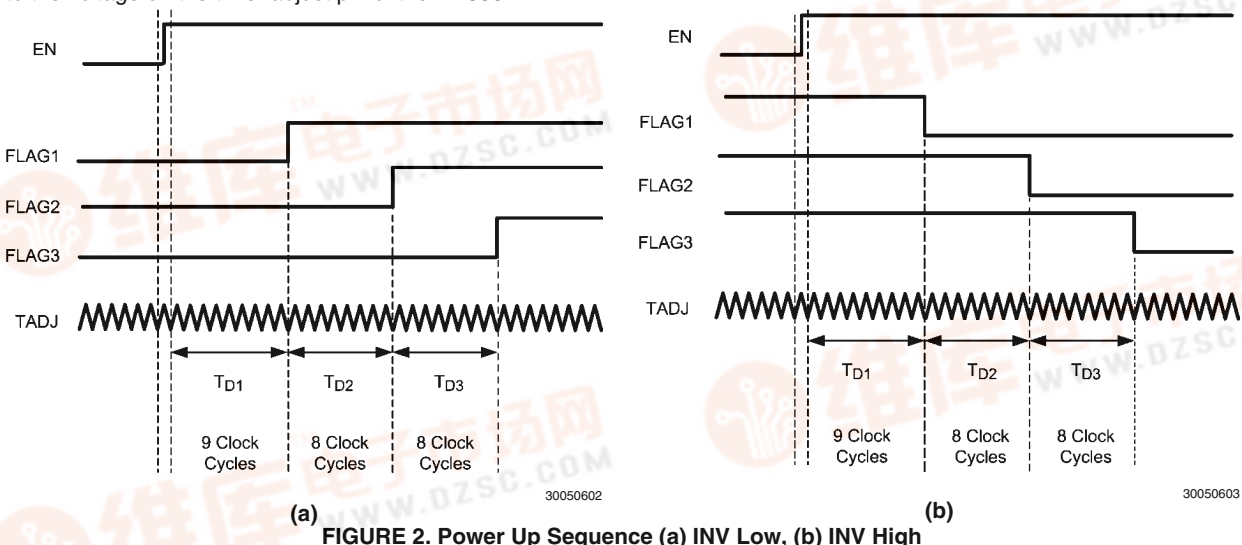
## Timing Sequence

[Figure 2](#) and [Figure 3](#) present the power up and power down timing sequence of the output flags with the INV at logic level low and high respectively. The waveform labeled TADJ refers to the voltage on the timer adjust pin of the LM3881.



(a) (b)  
FIGURE 2. Power Up Sequence (a) INV Low, (b) INV High



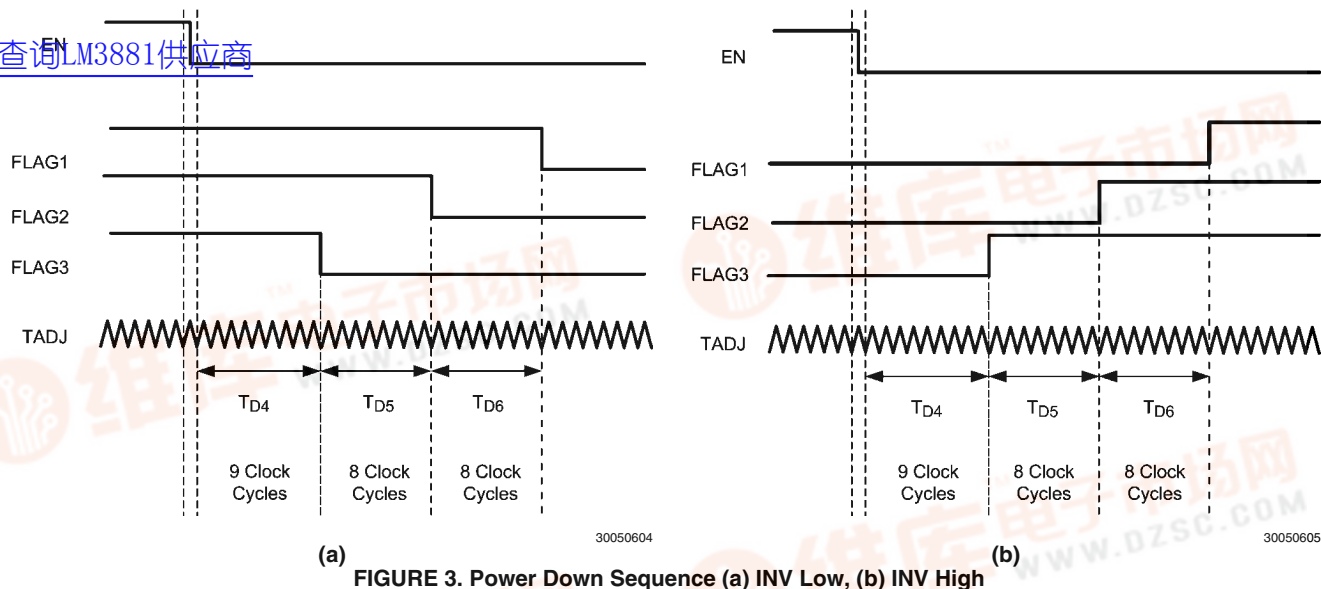
[查询LM3881供应商](#)


FIGURE 3. Power Down Sequence (a) INV Low, (b) INV High

## LM3881 Circuit Schematic

The evaluation board schematic is given in [Figure 4](#). The board contains the LM3881MFX device which has a timing capacitor,  $C_{ADJ}$ , of 10 nF so that each time delay between flags will be approximately 10 ms. The pull-up resistors of the flag outputs (R1, R2, R3) are each 100 k $\Omega$ .

The LM3881 has an enable pin that is pulled up by an internal 7  $\mu$ A current source. Thus, the associated PCB terminal, la-

beled EN, can be left open circuit if desired. In this case, the flags will release when the LM3881  $V_{CC}$  supply exceeds its UVLO level. Finally, the LM3881 has an invert pin that sets the polarity of the flags. The associated PCB terminal, labeled INV, needs to be connected to VCC or GND.

The evaluation board bill of materials, LM3881 pin-out and pin description are given in [Table 1](#), [Figure 5](#) and [Table 2](#) respectively.

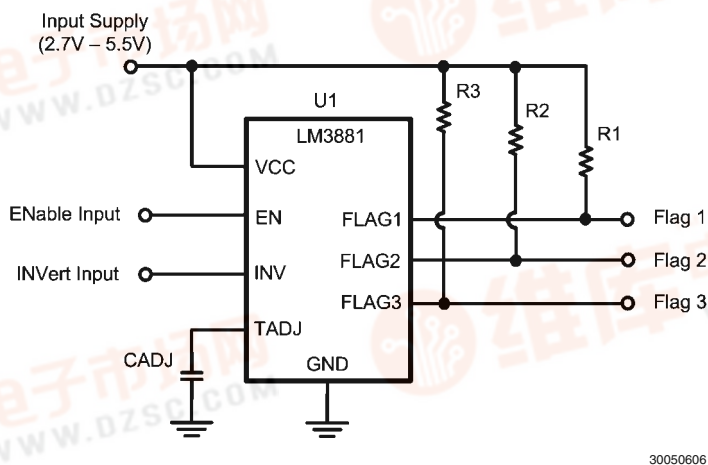


FIGURE 4. LM3881 Schematic

## LM3881 Evaluation Board Bill of Materials

[查询LM3881供应商](#)

TABLE 1.

Ref Des	Description	Case Size	Manufacturer	Manufacturer P/N
U1	LM3881 Sequencer	MSOP-8	National Semiconductor	LM3881MFX
R1	100 k $\Omega$	0603	Vishay Dale	CRCW06031003F-e3
R2	100 k $\Omega$	0603	Vishay Dale	CRCW06031003F-e3
R3	100 k $\Omega$	0603	Vishay Dale	CRCW06031003F-e3
CADJ	10 nF $\pm$ 10% X7R 16V	0603	Murata	GRM188R71C103KA01

## LM3881 Pin-Out

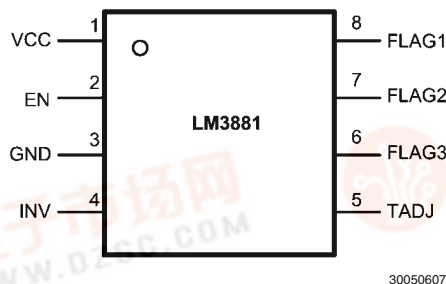


FIGURE 5. LM3881 Pin-Out

## LM3881 Pin Descriptions

TABLE 2.


Pin #	Name	Function
1	VCC	Input Supply
2	EN	Precision Enable
3	GND	Ground
4	INV	Output Logic Invert
5	TADJ	Timer Adjust
6	FLAG3	Open Drain Output #3
7	FLAG2	Open Drain Output #2
8	FLAG1	Open Drain Output #1

## PC Board Layout

查询LM3881供应商


The evaluation board is based on a small 1.09" x 0.76" FR4 PCB with two layers of copper. The actual layout can be seen

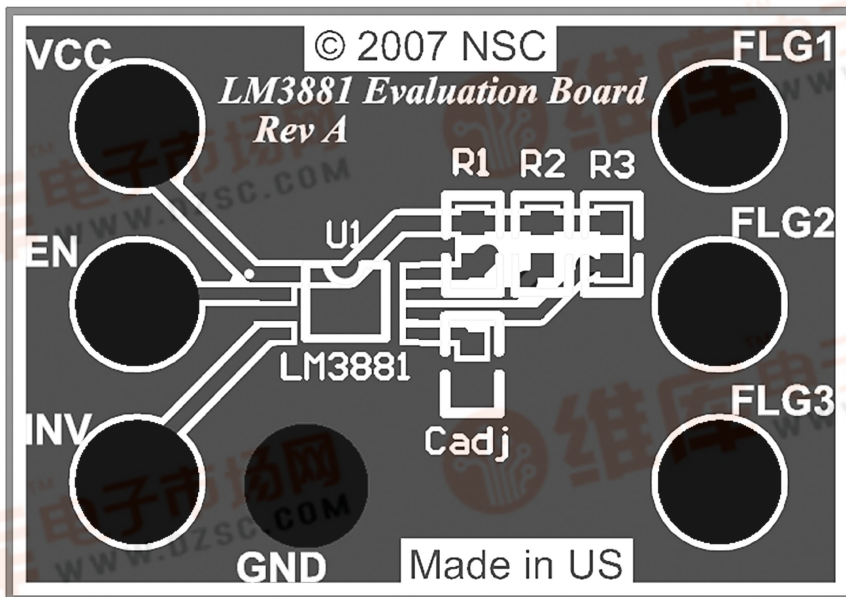in [Figure 6](#) and [Figure 7](#) below. When looking at the top layer, pin 1 of the LM3881 is on the upper left. An optional component, assigned reference designator R4, is placed on the bottom side of the PCB to facilitate connection of INV to GND.



30050608

FIGURE 6. Top Side PCB Layout

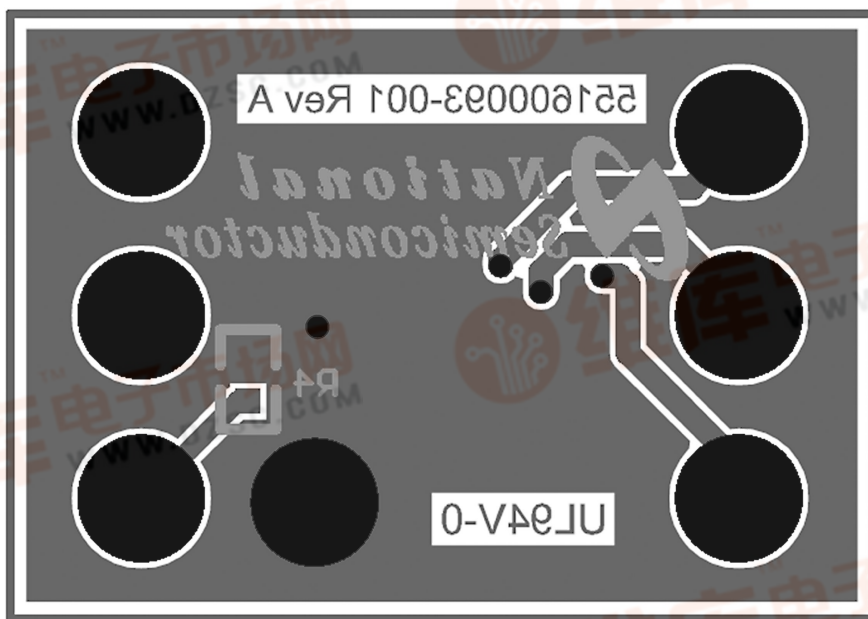


30050609

FIGURE 7. Bottom Side PCB Layout

[查询LM3881供应商](#)

## Notes

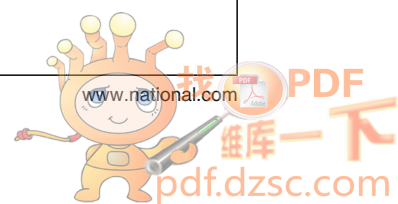



[查询LM3881供应商](#)

## Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Products		Design Support	
Amplifiers	<a href="http://www.national.com/amplifiers">www.national.com/amplifiers</a>	WEBENCH® Tools	<a href="http://www.national.com/webench">www.national.com/webench</a>
Audio	<a href="http://www.national.com/audio">www.national.com/audio</a>	App Notes	<a href="http://www.national.com/appnotes">www.national.com/appnotes</a>
Clock and Timing	<a href="http://www.national.com/timing">www.national.com/timing</a>	Reference Designs	<a href="http://www.national.com/refdesigns">www.national.com/refdesigns</a>
Data Converters	<a href="http://www.national.com/adc">www.national.com/adc</a>	Samples	<a href="http://www.national.com/samples">www.national.com/samples</a>
Interface	<a href="http://www.national.com/interface">www.national.com/interface</a>	Eval Boards	<a href="http://www.national.com/evalboards">www.national.com/evalboards</a>
LVDS	<a href="http://www.national.com/lvds">www.national.com/lvds</a>	Packaging	<a href="http://www.national.com/packaging">www.national.com/packaging</a>
Power Management	<a href="http://www.national.com/power">www.national.com/power</a>	Green Compliance	<a href="http://www.national.com/quality/green">www.national.com/quality/green</a>
Switching Regulators	<a href="http://www.national.com/switchers">www.national.com/switchers</a>	Distributors	<a href="http://www.national.com/contacts">www.national.com/contacts</a>
LDOs	<a href="http://www.national.com/ldo">www.national.com/ldo</a>	Quality and Reliability	<a href="http://www.national.com/quality">www.national.com/quality</a>
LED Lighting	<a href="http://www.national.com/led">www.national.com/led</a>	Feedback/Support	<a href="http://www.national.com/feedback">www.national.com/feedback</a>
Voltage Reference	<a href="http://www.national.com/vref">www.national.com/vref</a>	Design Made Easy	<a href="http://www.national.com/easy">www.national.com/easy</a>
PowerWise® Solutions	<a href="http://www.national.com/powerwise">www.national.com/powerwise</a>	Solutions	<a href="http://www.national.com/solutions">www.national.com/solutions</a>
Serial Digital Interface (SDI)	<a href="http://www.national.com/sdi">www.national.com/sdi</a>	Mil/Aero	<a href="http://www.national.com/milaero">www.national.com/milaero</a>
Temperature Sensors	<a href="http://www.national.com/tempsensors">www.national.com/tempsensors</a>	SolarMagic™	<a href="http://www.national.com/solarmagic">www.national.com/solarmagic</a>
Wireless (PLL/VCO)	<a href="http://www.national.com/wireless">www.national.com/wireless</a>	PowerWise® Design University	<a href="http://www.national.com/training">www.national.com/training</a>

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

### LIFE SUPPORT POLICY

**NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION.** As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2009 National Semiconductor Corporation

For the most current product information visit us at [www.national.com](http://www.national.com)



**National Semiconductor  
Americas Technical  
Support Center**  
Email: [support@nsc.com](mailto:support@nsc.com)  
Tel: 1-800-272-9959

**National Semiconductor Europe  
Technical Support Center**  
Email: [europe.support@nsc.com](mailto:europe.support@nsc.com)

**National Semiconductor Asia  
Pacific Technical Support Center**  
Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

**National Semiconductor Japan  
Technical Support Center**  
Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)

