LMH6733 High Definition Video Transmission Over CAT5

Sending component 1080i High Definition (HD) video over CAT5 twisted-pair is achievable with a low cost solution using National Semiconductor's Current Feedback (CFB) LMH6733 operational amplifier. The LMH6733 is a triple operational amplifier with disable that has a slew rate of 1900 V/ us and a 2 V_{PP} output signal bandwidth of 480 MHz, making it ideal for this application. Component video signals are made up of luma (Y) signal which contains the brightness and synchronizing information, and the two color-difference signals Pr and Pb.

Standard CAT5 cable consists of 4 twisted-pairs of AWG-24 cables with characteristic impedance of 100Ω . The DC resistance is $10\Omega/100m$ and capacitance of 4.5 nF/100m. Attenuation within CAT5 cable increases exponentially with respect to cable length and is a concern that will be addressed with equalization. Figure 1 illustrates this loss at various cable lengths.

National Semiconductor Application Note 1822 Vannavong Philavanh January 14, 2009



.com

By utilizing 3 of the 4 twisted-pairs, the entire signal path can be designed using the LMH6733 amplifier for the driver, receiver, and equalizer circuits to drive 75 ft, 250 ft, and 500 ft of CAT5 cable. Figure 3 shows the block diagram consisting of all three circuit sections. Each circuit section will be explained in further detail in this application note.

Video Transmitter

The video transmit board has one LMH6733 device configured to drive component video input from an HD video source onto selectable CAT5 cable lengths of 75 ft, 250 ft, and 500 ft. The cable length select switch is located on the video receive board. Figure 2 shows one channel of the LMH6733 configured for a gain of 2 V/V to drive one CAT5 twisted-pair. The 50 Ω output series resistor isolates the device from the long CAT5 transmission twisted-pair with one of the wires connected to ground through a 50Ω resistor to balance the load.





FIGURE 4. CAT5 Transmit Board

Video Receiver and Equalization

The video receiver board has one LMH6733 device to function as a differential input signal receiver and three additional LMH6733 devices to perform signal equalization for cable lengths of 75 ft, 250 ft, and 500 ft. Each channel of the LMH6733 receiver device is configured for a gain of -2 V/V to handle a differential input signal from the three twisted-pairs for the Y, Pr, and Pb video signals. A first order RC, low-pass filter with a -3 dB roll-off of 200 MHz is place between the receiver output and equalizer input to filter out high frequency noise components. Due to the non-inverting input capacitance of 1 pF, an inverting gain topology is recommended for the equalization circuit to minimize gain peaking and potential oscillation due to excessive parasitic capacitance and inductance associated with device package and board routing. The equalization circuit is implemented with an

additional LMH6733 channel along with a network of RC branches in parallel with the gain resistor, R_G, to provide a zero-pole compensation for attenuation of higher frequency signals in the CAT5 twisted-pair wires. Each branch compensates for the set frequency of attenuation depending on the cable length, such that the video signal maintains a flat frequency response to accommodate the 31 MHz of large signal bandwidth required for 1080i HD signal. For example, to transmit HD video signal up to 500 ft of CAT5 cable the three set frequencies are approximately 2.5 MHz, 9 MHz, and 31 MHz, respectively. Because of it's high slew rate value, the advantage of using CFB amplifiers as the equalizer is it's ability to boost equalization gain at high frequencies. The output of the equalizer drives a $R_{\Omega} = 75\Omega$ load to match the input impedance of the video display. Figure 5 shows the circuit implementation of one receive channel driving one equalization channel.





AN-1822

Figure 6 shows the details of the equalization circuit config-Pb. However, the entire equalization circuitry is made up of three LMH6733 devices for Y, Pr, and Pb signals and is shown

in Figure 7. Each channel of the LMH6733 is optimized through the RC network to drive CAT5 cable lengths of 75 ft, 250 ft, and 500 ft.



TABLE 1. RC Network Equalization Tal	ble
--------------------------------------	-----

TABLE 1. RC Network Equalization Table									
RF	RG	Channel A: 75 ft CAT5		Channel B: 250 ft CAT5		Channel C: 500 ft CAT5			
<mark>55</mark> 0Ω	383 Ω	R _{1A} = OPEN	C _{1A} = OPEN	R _{1B} = 200Ω	C _{1B} = 68 pF	R _{1C} = 25Ω	C _{1C} = 120 pF		
		$R_{2A} = OPEN$	$C_{2A} = OPEN$	R _{2B} = 1.35 kΩ	C _{2B} = 1.5 pF	R _{2C} = 700Ω	C _{2C} = 1.8 pF		
		R _{3A} = OPEN	C _{3A} = OPEN	R _{3B} = 8.4 kΩ	C _{3B} = 18 pF	R _{3C} = 909Ω	C _{3C} = 47 pF		
						W W	DZSU		

O

f.dzsc.com

Ing the rotary switch to SHOR1, MEDIUM, or LONG to select the desired length of CAT5 to equalize. Enabling of the channels is achieved by connection DISA, DISB, or DISC to +5V. The other two channels are disabled by a 1 k Ω pull down resistor. For example, when SHORT is selected for a maximum cable length of 75 ft, channel A of all three LMH6733 equal-

ization devices are enabled while channels B and C of all three devices are disabled. The output can be sent to a video monitoring device through the RCA connector with indicators green-Y, red-Pr, and blue-Pb. The table below shows the switch positions, CAT5 cable lengths, and associated amplifier channels.

Rotary Switch Position	Maximum CAT5 Cable Length	LMH6733 Channel Enabled
SHORT	75 ft	A
MEDIUM	250 ft	В
LONG	500 ft	C C C C C C C C C C C C C C C C C C C

Output resistors, R_0 , are positioned to isolate the enabled channel from parasitic capacitance of the disabled channels. Each disabled channel may add up to 2 pF of capacitance to the enabled channel and may cause the circuit to oscillate. To achieve an overall cascaded gain of +2 V/V for the receiver

and equalization amplifiers, the equalizer amplifier should have a gain of -1 V/V. However, due to the signal attentuation by the low-pass filters, R_O, and R_L the gain is increased slightly to -1.4 V/V, thus making R_G = 383 Ω and R_F = 550 Ω

com

sc com

Power Supply and Signal Coupling

香间LMH6733供应商 Both reterence boards have the capability to be configured for either DC or AC coupled applications. If the desired signal path is to be DC-coupled there are two power supply options. Option one is to connect a single +5V power supply and have the LM2734 buck-boost regulator generate the -5V supply voltage to power the LMH6733 amplifier(s) with jumpers on REG_DIS and V-_SEL set for regulator output REG_OUT. Figure 9shows the LM2734 circuit and equations. From the equations, if R2 = 750 Ω and $|V_{\Omega}|$ = 5V, then R1 = 4 k Ω by calculation. The second option is to bypass the LM2734 regulator and directly power the board with +5V and -5V supplies using the three terminal power supply connector with a jumper on V-_SEL set for external negative supply EXT V-. The third option is to bypass both the LM2734 regulator and use a single +5V power supply. For this option, modifications to the board will have to be made to AC couple and appropriately bias the inputs of the LMH6733 device.

Transmit Board Modifications for AC-Coupling

(1) Cut traces on C1A, C1B, and C1C. Replace with 47 μF tantalum capacitors.

(2) Add 1 k Ω resistors for R1A, R1B, R1C, R2A, R2B, and R2C.

(3) Add 1.5 μ F tantalum capacitors for C2A, C2B, and C2C. (4) Add 2 k Ω resistors for R3A, R3B, and R3C.

(5) Add 766 Ω resistors for R4A, R4B, and R4C. Replace RGA, RGB, and RGC resistor value of 383 Ω with 766 Ω .

Receive & Equalization Board Modifications for AC-Coupling

(1) Cut traces on C1-C6. Replace with 4.7 μF tantalum capacitors.

(2) Add 200 Ω resistor for R13, R23, and R33. Replace 100 Ω resistors R12, R22, and R32 with 200 Ω .

(3) Replace R, R, and R with 470 µF tantalum capacitors.

查询LMH6733供应商

Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Pro	oducts	Design Support		
Amplifiers	www.national.com/amplifiers	WEBENCH® Tools	www.national.com/webench	
Audio	www.national.com/audio	App Notes	www.national.com/appnotes	
Clock and Timing	www.national.com/timing	Reference Designs	www.national.com/refdesigns	
Data Converters	www.national.com/adc	Samples	www.national.com/samples	
Interface	www.national.com/interface	Eval Boards	www.national.com/evalboards	
LVDS	www.national.com/lvds	Packaging	www.national.com/packaging	
Power Management	www.national.com/power	Green Compliance	www.national.com/quality/green	
Switching Regulators	www.national.com/switchers	Distributors	www.national.com/contacts	
LDOs	www.national.com/Ido	Quality and Reliability	www.national.com/quality	
LED Lighting	www.national.com/led	Feedback/Support	www.national.com/feedback	
Voltage Reference	www.national.com/vref	Design Made Easy	www.national.com/easy	
PowerWise® Solutions	www.national.com/powerwise	Solutions	www.national.com/solutions	
Serial Digital Interface (SDI)	www.national.com/sdi	Mil/Aero	www.national.com/milaero	
Temperature Sensors	www.national.com/tempsensors	Solar Magic®	www.national.com/solarmagic	
Wireless (PLL/VCO)	www.national.com/wireless	Analog University®	www.national.com/AU	

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2009 National Semiconductor Corporation

For the most current product information visit us at www.national.com

C

AN-1822

National Semiconductor Americas Technical Support Center Email: support@nsc.com Tel: 1-800-272-9959 National Semiconductor Europe Technical Support Center Email: europe.support@nsc.com German Tel: +49 (0) 180 5010 771 English Tel: +44 (0) 870 850 4288 National Semiconductor Asia Pacific Technical Support Center Email: ap.support@nsc.com National Semiconductor Japan Technical Support Center Email: jpn.feedback@nsc.com

0