

**BR**  
A DIVISION OF **CIRRUS LOGIC**

**CS5360**

## 24-Bit Stereo A/D Converter for Digital Audio

The following information is based on the technical datasheet:

*CS5360 DS280PP1 SEP '97*

Please contact Cirrus Logic : Crystal Semiconductor Products Division for further information.




---

### **CRYSTAL SEMICONDUCTOR PRODUCTS DIVISION PRODUCT INFORMATION**

Copyright © Cirrus Logic, Inc. 1998  
(All Rights Reserved)

PI280PP1 MAR '98



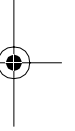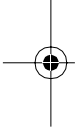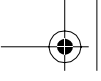



## CS5360 Features

---

### ***24-Bit Stereo A/D Converter for Digital Audio***

---

#### **Features**

- 24 Bit Digital Output
- 105 dB Dynamic Range
- -95 dB THD+N
- 128X Oversampling
- Fully Differential Inputs
- Linear Phase Digital Anti-Alias Filtering
  - 21.7 kHz passband ( $F_s = 48\text{kHz}$ )
  - 85 dB stop band attenuation
  - 0.0025 dB pass band ripple
- High Pass Filter - DC Offset Removal
- Peak Signal Level Detector
  - High Resolution and Bar Graph Modes
- Pin Compatible with CS5334 and CS5335

#### **Description**


The CS5360 is a 2-channel, single +5 V supply, 24-bit analog-to-digital converter for digital audio systems. The CS5360 performs sampling, analog-to-digital conversion and anti-alias filtering, generating 24-bit values for both left and right inputs in serial form. The output word rate can be up to 50 kHz per channel.

The CS5360 uses 4th-order, delta-sigma modulation with 128X oversampling followed by digital filtering and decimation, which removes the need for an external anti-alias filter. This ADC uses a differential architecture which provides excellent noise rejection.


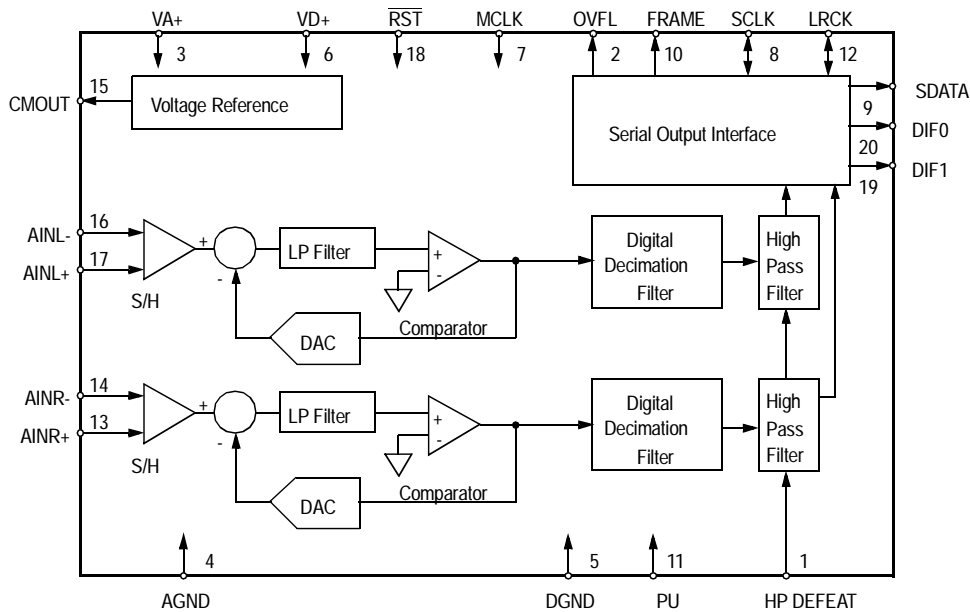
## CS5360 Overview

The CS5360 has a filter passband to 21.7 kHz. The filter has linear phase, 0.0025 dB passband ripple, and >85 dB stopband rejection. An on-chip high pass filter is also included to remove DC offsets.



### Overview

The CS5360 is a 24-bit, 2-channel analog-to-digital converter designed for digital audio applications. This device uses two one-bit delta-sigma modulators which simultaneously sample the analog input signals at 128 times the output sample rate ( $F_s$ ). The resulting serial bit streams are digitally filtered, yielding a pair of 24-bit values. This technique yields nearly ideal conversion performance independent of input frequency and amplitude. The converter does not require difficult-to-design or expensive anti-alias filters and does not require external sample-and-hold amplifiers or a voltage reference. Very few external components are required to support this ADC. Normal power supply decoupling components and a resistor and capacitor on each input for anti-aliasing are all that's required.



## CS5360 FAQs

An on-chip voltage reference provides for a differential input signal range of 2.0 Vrms. Output data is available in serial form, coded as 2's complement, 24-bit numbers. Typical power consumption is 325 mW which can be reduced to 1.0 mW by using the power-down feature.

### FAQs

- 1) Is the CS5360 Crystal's lowest priced 24-bit converter?  
A: Yes. The CS5360 is the lowest priced 24-bit converter offering 105 dB dynamic range and -95 dB total harmonic distortion + noise. Crystal also offers three higher performance 24-bit audio A/D converters - the CS5394, CS5396, and CS5397. The CS5394 offers 117 dB dynamic range with -103 dB THD+N and the CS5396 and CS5397 are the worlds only 24-bit, 96 kHz audio A/D converters. The CS5396 and CS5397 are also the first audio A/D converters to achieve 120 dB dynamic range.
- 2) When used with the CS4390 24-bit DAC, what is the dynamic range performance in loopback mode (analog in to analog out)?  
A: 102-103 dB dynamic range.
- 3) What advantage does the high pass filter offer over traditional calibration techniques to reduce offsets?  
A: The CS5360 high pass filter can remove both offsets in the input circuitry driving the ADC and internal offsets generated within the ADC. The use of a digital high pass filter technique to reduce offsets consistently produces a zero LSB offset which cannot be achieved with traditional calibration techniques.
- 4) Is the high pass filter defeatable for applications where DC information is important?  
A: Yes.



## CS5360 Ordering Information

- 5) How is the peak signal level detector used?
- A: The peak signal detector monitors the input signal level into the ADC and outputs 8 bits which correspond to the peak input level. These bits can be used to implement a low cost bar graph display. These 8 bits are output from the ADC following the audio data, and they indicate whether the input signal is clipping (5 dB above full scale) or -60 dB from full scale in 1 dB step resolution. The peak signal detector is updated by toggling the PU (peak update) pin.
- 6) How is the overflow output used?
- A: The OVFL pin goes high when the audio data exceeds the analog input range of the ADC. This pin can be used to light an LED on a system front panel indicating an overrange condition. This pin is cleared with the PU (peak update) pin.

### Ordering Information

CS5360-KS      -10° to 70°C      20-pin Plastic SSOP

For further information on Crystal products, please visit our website “[www.crystal.com](http://www.crystal.com)” or call our literature department (800) 888-5016 ext. 3594 or (512) 912-3594 for data sheets and application notes.

### Schematic & Layout Review Service

Confirm Optimum  
Schematic & Layout  
Before Building Your Board.



For Our Free Review Service  
Call Applications Engineering.

**C a l l : ( 5 1 2 ) 4 4 5 - 7 2 2 2**

## Sales Office and Applications Support

### UNITED STATES

#### Western Area

Cirrus Logic, Inc.  
3100 West Warren Ave.  
Fremont, CA 94538  
Ph: 510-623-8300  
FAX: 510-252-6020

Southern California, Sales  
Westlake Village  
The Townsgate Executive Bldg.  
2659 Townsgate Road,  
Suite 238  
Westlake Village, CA 91361  
Ph: 805-371-5860  
FAX 805-371-5861

Cirrus Logic, Inc.  
6650 S.W. Redwood Lane,  
Ste. 105, First Floor Bldg. 16  
Portland, Oregon 97224  
Ph: 503-620-5547  
FAX: 503-620-5665

#### Central Area

Cirrus Logic, Inc.  
14205 Burnet Rd., Ste. 400  
Austin, TX 78728  
Ph: 512-255-8893  
FAX: 512-255-0733

#### Sotheastern Area

Cirrus Logic, Inc..  
5511 Capital Center Dr., Ste. 103  
Raleigh, NC 27606  
Ph: 919-859-5210  
FAX: 919-859-5334

#### Northeastern Area

Cirrus Logic, Inc.  
10 New England Business  
Center, Ste. 100  
Andover, MA 01810  
Ph: 978-794-9992  
FAX: 978-794-9998

Cirrus Logic, Inc.  
10440 Little Patuxent Pkwy.,  
Ste. 300  
Columbia, MD 21044-3559  
Ph: 410-740-5654  
FAX: 410-740-6961

### EUROPE

Cirrus Logic International SARL  
Immeuble Andre Malraux  
1 rue de Rome  
F-93561 Rosny-sous-Bois  
CEDEX, France  
Ph: +33148122812  
FAX: +33148122810

Cirrus Logic UK.  
Angler's Court  
4-5 Spittal St.  
Marlow  
Bucks, England SL7 1DB  
Ph: +44(0)1628 472 211  
FAX: +44(0)1628 486 114

Cirrus Logic GmbH  
Muehlfelder-Strasse 2  
D-82211 Herrsching, Germany  
Ph: +49815292460  
FAX: +498152924699

### FAR EAST

#### China

Cirrus Logic International Ltd.  
A-1403, Qiancun Commercial  
Mansion  
Beijing, China 100029  
Ph: (8610)6443-0783  
Ph: (8610)6443-0784  
Ph: (8610)6443-0785  
FAX: (8610)6443-0786

#### Hong Kong

Cirrus Logic International Ltd.  
1203 Park Tower  
15 Austin Rd., Tsimshatsui  
Kowloon, Hong Kong  
Ph: (852)2376-0801  
FAX: (852)2375-1202

### Korea

Cirrus Logic, Korea Co., Ltd.  
Rm 1302 SangKyung  
Bldg., 824-21 YeokSam-Dong,  
Kang Nam-Ku,  
Seoul, Korea  
Ph: +82(2)565-8561  
FAX: +82(2)565-8565

### Singapore

Cirrus Logic  
6 Kaki Bukit Ave. 1,  
Ste. 03-03  
Singapore 417940  
Ph: +65-743-4111  
FAX: +65-742-4111

### Taiwan

Cirrus Logic International Ltd.  
Taiwan Branch  
10F, No.214 Tun Hwa North Rd.  
Taipei, Taiwan R.O.C.  
Ph: +886(22)718-4533  
FAX: +886(22)718-4526

### JAPAN

Cirrus Logic K.K.  
Shinjuku Green Tower,  
Bldg. 26F  
6-14-1 Nishi-Shinjuku,  
Shinjuku-ku,  
Tokyo, 160  
Japan  
Ph: +81(03)3340-9111  
FAX: +81(03)3340-9120

**CRYSTAL**  
A DIVISION OF  CIRRUS LOGIC®

**CRYSTAL SEMICONDUCTOR  
PRODUCTS DIVISION**

**PO BOX 17847  
4210 S. INDUSTRIAL DRIVE  
AUSTIN, TEXAS 78744  
512.445.7222 / 800.888.5016  
FAX: 512.445.7581**

**WORLDWIDE WEB:  
<http://www.crystal.com>**