

查询DBL339供应商

捷多邦，专业PCB打样工厂，24小时
急出货

DBL 339

QUAD VOLTAGE COMPARATOR


Specially designed to offer a versatility as high as possible

FEATURES

- Low current drain : 0.8mA
- Allows sensing near ground
- Logic output compatible with TTL, DTL, ECL, MOS and CMOS
- Low input biasing current
- Low input offset current
- Low output saturation voltage
- Wide supply voltage range :
 - Single : 2V~36V
 - Dual : ±1V~18V

14DIP

Unit: mm

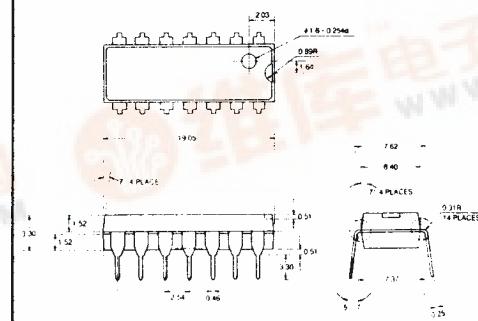

APPLICATIONS


- High precision comparators
- Driving logic systems
- Various multivibrators
- Generators and Oscillators

MAXIMUM RATINGS


Characteristic	Symbol	Rating	Unit
Supply Voltage	V _{CC}	36 or ±18	V
Differential Input Voltage	V _{IND}	36	V
Input Voltage	V _{IN}	-0.3~36	V
Power Dissipation	P _D	570	mW
Operating Temperature	T _{opr}	0~+70	°C
Storage Temperature	T _{stg}	-55~+150	°C

DBL 339

BLOCK DIAGRAM

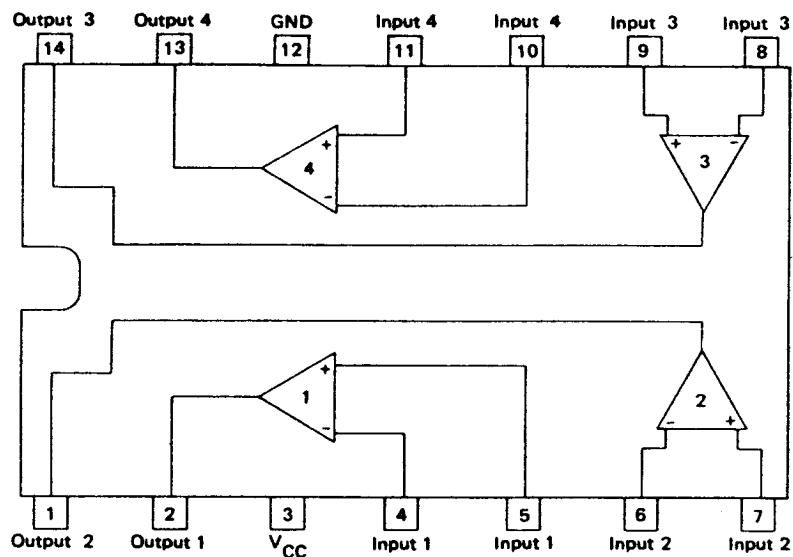

EQUIVALENT CIRCUIT (One section)

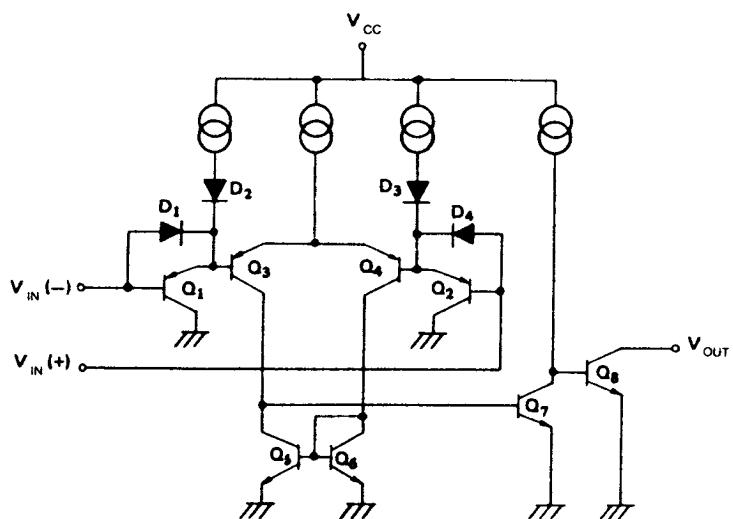

DBL 339

□ ELECTRICAL CHARACTERISTICS


(Unless otherwise specified, $V_{CC} = 5V$ and $0^\circ C \leq Ta \leq 70^\circ C$)

Characteristic	Symbol	Test Condition		Min.	Typ.	Max.	Unit	
Input Offset Voltage	V_{IOS}	$V_{OUT} = 1.4V$, $5V \leq V_{CC} \leq 30V$	$Ta = 25^\circ C$	—	± 2	± 5	mV	
		$R_g = 0\Omega$, $0V \leq V_{IC} \leq V_{CC} - 1.5V$	—	—	—	± 9	mV	
Input Offset Current	I_{IOS}	—		$Ta = 25^\circ C$	—	± 5	± 50	
		—		—	—	± 150	nA	
Input Bias Current	I_{IB}	—		$Ta = 25^\circ C$	—	25	250	
		—		—	—	400	nA	
Input Common Mode Voltage Range	V_{ICR}	—		$Ta = 25^\circ C$	0	—	$V_{CC} - 1.5$	
		—		—	0	—	$V_{CC} - 2$	
Supply Current	I_{CC}	$R_L = \infty$, $Ta = 25^\circ C$		—	0.8	2	mA	
Voltage Gain	G_V	$R_L \geq 15K\Omega$, $V_{CC} = 15V$, $Ta = 25^\circ C$		—	200	—	V/mV	
Response Time	Large Signal t_R	$V_{RL} = 5V$	$V_{IN} = TTL$ Logic swing	—	300	—	nS	
			$V_{REF} = 1.4V$	—	—	—	—	
		$R_L = 5.1K\Omega$	$V_{IN} = 100mV$ step	—	—	—	—	
Small Signal		$Ta = 25^\circ C$	with 5mV overdriver	—	1.3	—	μS	
		—	—	—	—	—	—	
Output sink Current	I_{SINK}	$V_{IN^-} \geq 1V$, $V_{IN^+} = 0V$		6	16	—	mA	
		$V_{OUT} \leq 1.5V$, $Ta = 25^\circ C$		—	—	—	—	
Output Leakage Current	I_{LEAK}	$V_{IN^+} > 1V$ $V_{IN^-} = 0V$	$V_{OUT} = 5V$	—	0.1	—	nA	
			$Ta = 25^\circ C$	—	—	1	μA	
Saturation Voltage	V_{SAT}	$V_{IN^-} \geq 1V$, $V_{IN^+} = 0V$		$Ta = 25^\circ C$	—	250	400	
		$I_{SINK} \leq 4mA$		—	—	700	mV	
Differential Input Voltage	V_{IND}	Keep all $V_{IN'S} \geq 0V$		—	—	36	V	

* V_{IC} : Input Common Mode Voltage

DBL 339

□ TYPICAL PERFORMANCE CHARACTERISTICS

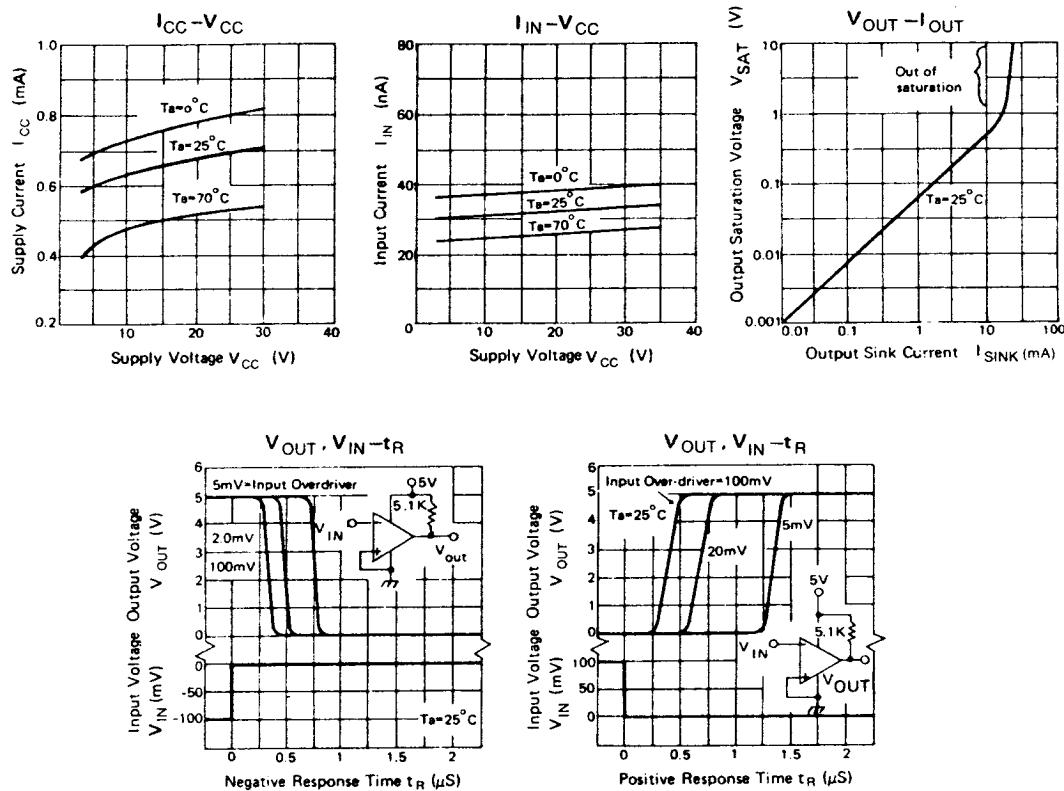

□ APPLICATION INFORMATION

During the output voltage transition intervals as the comparator change states, the DBL339 can easily oscillate if the output lead is inadvertently allowed to capacitively couple to the inputs via stray capacitance. PC board layout is helpful as it reduces stray input-output coupling. Reducing the input resistors to less than $10K\Omega$ reduces the feedback signal levels and finally. Adding even a small amount (1 to 10mV) of positive feedback(hysteresis)causes such a rapid transition that oscillations due to stray feedback are not possible. It is good design practice to ground all pins of and unused comparator


The differential input voltage may be larger than V_{cc} without damaging the device. Because input voltage more negative than $-0.3V$ (at $25^\circ C$)should not be used, an input clamp diode can be used as protection. The output of the DBL339 is the uncommitted collector of a grounded-emitter NPN output transistor. Many collectors can be tied together to provide wired-OR output function.

When the output sink current limit(approximately 16mA)is exceeded, the output transistor will come out of saturation and output voltage will rise very rapidly. Under this limit, the output saturation voltage is limited by the approximately 60Ω saturation resistance of the output transistor.


DBL 339

APPLICATION CIRCUITS ($V_{CC} = 5V$)


1. Basic Comparator

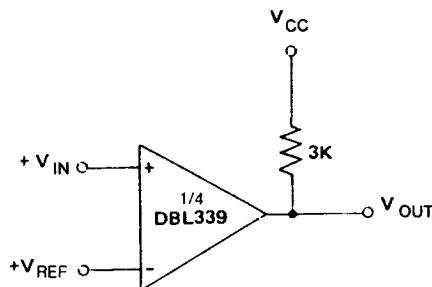

2. Driving CMOS

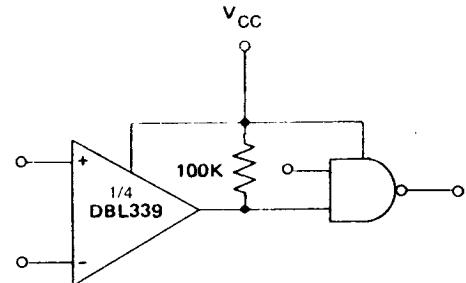


3. Two decade High frequency VCO

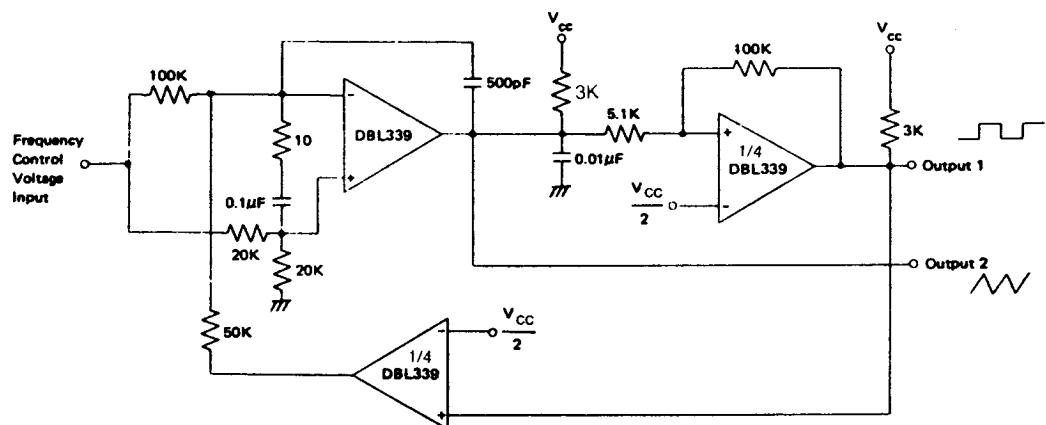


DBL 339

□ APPLICATION CIRCUITS ($V_{CC} = 15V$)


4. AND Gate

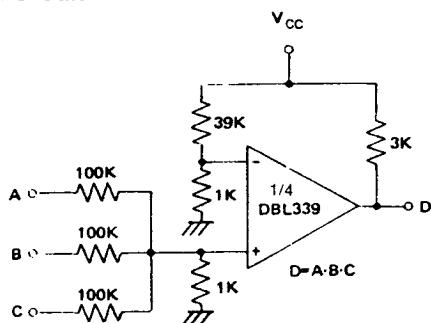


5. OR Gate

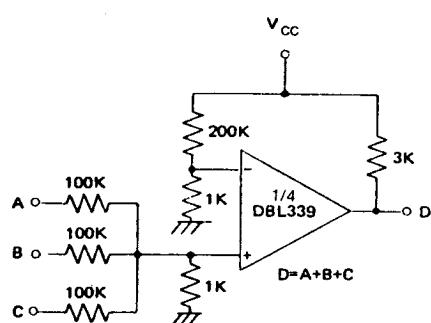

6. Squarewave Oscillator

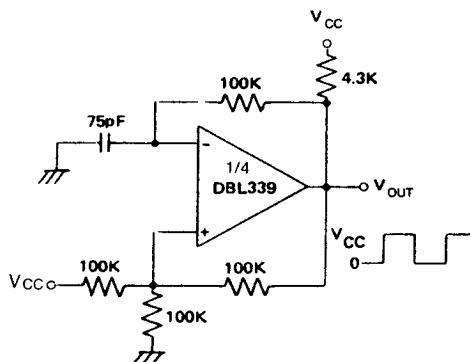

7. Pulse Generator

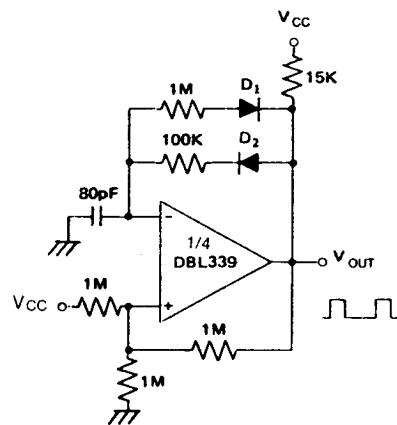

8. One-Shot Multivibrator with Input Lock Out

