
捷多邦,专业PCB打样工厂,24小时加急出货

 

Monolithic Linear IC

LA4145

0.6 to 0.9 W AF Power Amplifier for Radio Cassette Recorders


Features

- The LA4145 is especially suited for use in cassette tape recorder, radio-cassette, recorder, stereo cassette player applications.
- 0.6 W typ/V_{CC} = 6.0 V, $R_L = 8 \Omega$, THD = 10% 0.9 W typ/V_{CC} = 6.0 V, R_L = 4 Ω , THD = 10%
- Minimum number of external parts required
- Soft clip
- Small pop noise at V_{CC} ON/OFF mode
- Voltage gain fixed at 50 dB. An external resistor can be connected to reduce this value.

Package Dimensions

unit : mm

3017C-SIP9

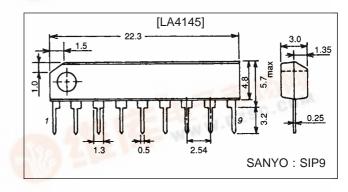

Specifications

Maximum Ratings at $Ta = 25^{\circ}C$

Parameter	Symbol	Conditions	Ratings	Unit
	V/ mov	Quiescent mode	9	V
Maximum supply voltage	V _{CC} max	Operating mode $R_L = 8 \Omega$	8	V
Maximum output current	I _O peak	4415	500	mA
Allowable power dissipation	Pd max	$50 \times 50 \text{ mm}^2 \text{ with PCB}$	0.9	W
Operating temperature	Topr		-20 to +70	°C
Storage temperature	Tstg	5 A 2	-40 to +150	°C

Operating Conditions at Ta = 25°C

Parameter	Symbol	Conditions	Ratings	Unit
Recommended supply voltage	V _{CC}		6	V
Recommended load resistance	RL		4 to 8	Ω
Operating voltage range	V _{CC}		3.6 to 8	V

Operating Characteristics at Ta = 25° C, $V_{CC} = 6.0$ V, $R_L = 8 \Omega$, $Rg = 600 \Omega$, f = 1 kHz

Parameter	Symbol	Conditions	min	typ	max	Unit
Quiescent current	Icco	LA4145		10	20	mA
Voltage gain	VG		48	50	52	dB
Output power	P	THD = 10%, $R_L = 4 \Omega$		0.9		W
	PO	THD = 10%, R _L = 8 Ω	0.45	0.6		W
Total harmonic distortion	THD	$P_0 = 0.1 \text{ W}$		0.2	1.0	%
Input resistance	r _i			30		kΩ
Output noise voltage	V _{NO}	Rg = 10 kΩ, B.P.F. = 20 Hz to 20 kHz		0.6	1.2	mV
Ripple rejection ratio	SVRR	Rg = 0, f _R = 100 Hz, V _R = 150 mV	-35	-40		dB



Proper care in changing voltage gain

An external resistor can be connected in series with the feedback capacitor at pin 2 to reduce the voltage gain. (See RNF-VG characteristic.)

IC usage notes

1. Maximum ratings

If the IC is used in the vicinity of the maximum ratings, even a slight variation in conditions may cause the maximum ratings to be exceeded, thereby leading to breakdown. Allow an ample margin of variation for supply voltage, etc. and use the IC in the range where the maximum ratings are not exceeded.

2. Pin-to-pin short


If power is applied when the space between pins is shorted, breakdown or deterioration may occur. When mounting the IC on the board or applying power, make sure that the space between pins is not shorted with solder, etc.

- 3. Radio applications For use in radio applications, keep a good distance between IC and bar antenna.
- 4. Printed circuit pattern


When designing the printed circuit pattern, make the power supply, output, and ground lines thicker and shorter and determine the pattern and parts placement so that no feedback loop is formed between input and output. Place power capacitor C_6 , oscillation blocking capacitor C_3 as close to the IC pin as possible to prevent oscillation from occurring. (See the sample printed circuit pattern.)

C ₁ (47 μF)	Feedback capacitor (NF capacitor)	Low cutoff frequency f_L depends on this capacitor. $f_L = 90$ Hz for $C_1 = 47 \mu$ F. Decreasing the capacitor value makes the starting time earlier.
C ₂ (100 μF)	Bootstrap capacitor	
C ₃ (0.15 μF)	Oscillation blocking capacitor	It is recommended to use a polyester film capacitor being good in temperature characteristic, high frequency characteristic.
C ₄ (470 μF)	Output capacitor	
C ₅ (47 μF)	Decoupling capacitor	Serves to reject ripple. The starting time depends on this capacitor. Increasing the capacitor value makes the starting time later.
C ₆ (470 μF)	Power capacitor	Place as close to the power pin of the IC as possible.
R ₁ (30 kΩ)	Input bias resistor	Serves to apply input bias. The input impedance almost entirely depends on this resistor value. If a variable resistor also serves for this purpose, this resistor can be omitted. In this case, it is recommended to use a resistor of 30 k Ω .


Description of external parts

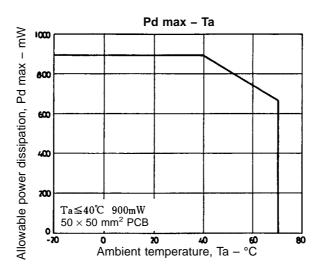

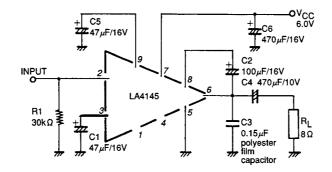
Sample Application Circuit: AF power amplifier




Sample Printed Circuit Pattern (Cu-foiled area)

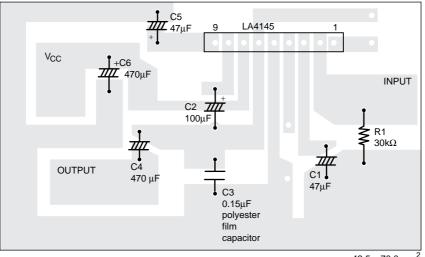




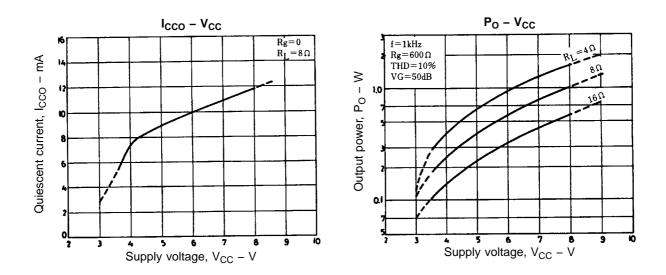

LA4145

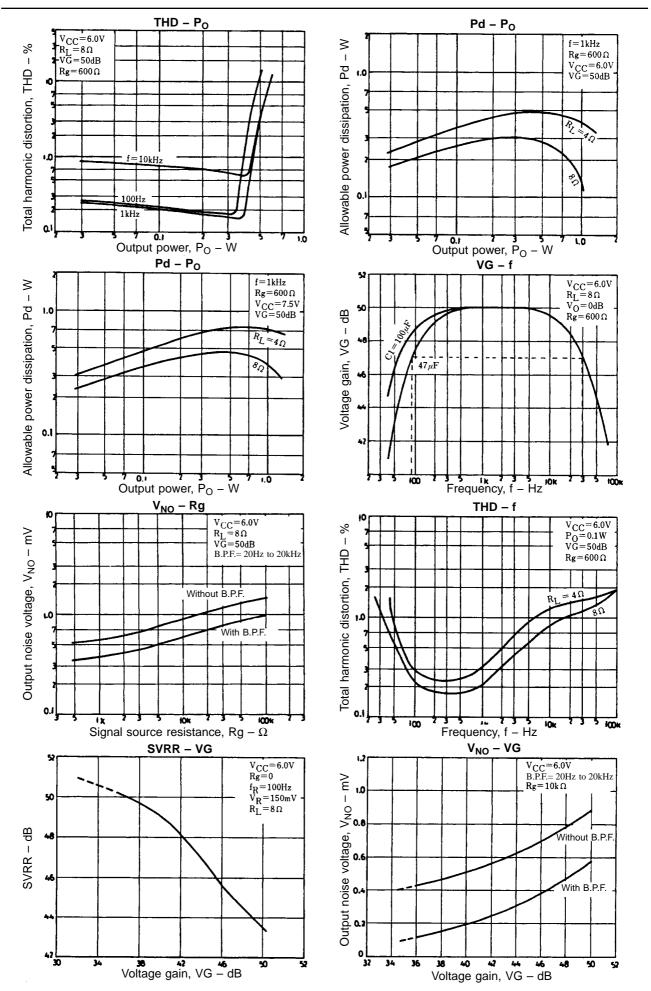

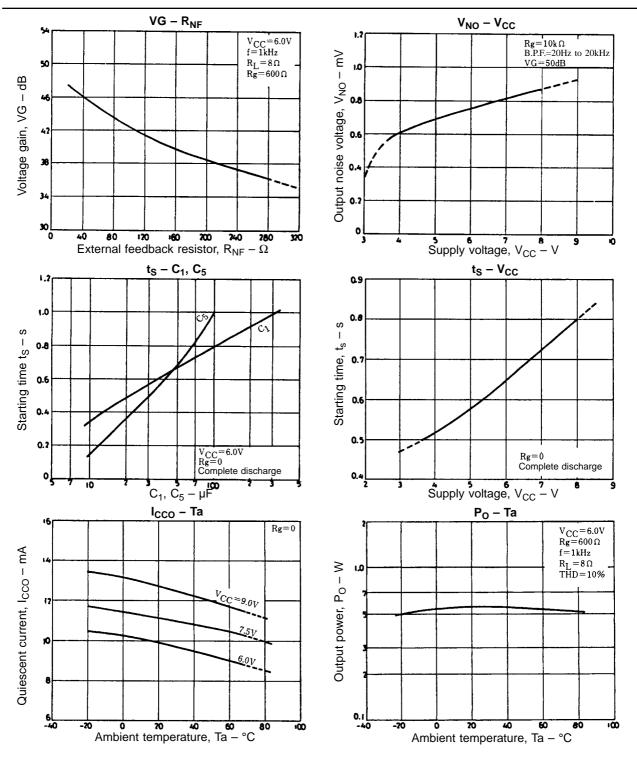

- No products described or contained herein are intended for use in surgical implants, life-support systems, aerospace equipment, nuclear power control systems, vehicles, disaster/crime-prevention equipment and the like, the failure of which may directly or indirectly cause injury, death or property loss.
- Anyone purchasing any products described or contained herein for an above-mentioned use shall:
 - ① Accept full responsibility and indemnify and defend SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors and all their officers and employees, jointly and severally, against any and all claims and litigation and all damages, cost and expenses associated with such use:
 - ② Not impose any responsibility for any fault or negligence which may be cited in any such claim or litigation on SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors or any of their officers and employees jointly or severally.
- Information (including circuit diagrams and circuit parameters) herein is for example only; it is not guaranteed for volume production. SANYO believes information herein is accurate and reliable, but no guarantees are made or implied regarding its use or any infringements of intellectual property rights or other rights of third parties.

This catalog provides information as of May, 1996. Specifications and information herein are subject to change without notice.