

Monolithic Linear IC



The LA5655 is an IC containing all the voltage regulators required for an FLT display desk-top calculator with a printer.

Features and Functions

- a. On-chip voltage regulators required for desk-top calculator (FLT display) with a printer.
 - 1. Printer voltage regulator.
 - 2. LSI voltage regulator.
 - 3. FLT anode, grid voltage regulator.
 - 4. FLT heater grid voltage regulator.
 - 5. FLT bias grid voltage regulator.


- b. On-chip printer motor brake circuit

Maximum Ratings at Ta=25°C


		unit
Voltage Regulator Input Voltage 1	V _{IN1}	50 V
Voltage Regulator Input Voltage 2	V _{IN2}	25 V
Output Current 1	I _{OUT1}	40 mA
Output Current 2	I _{OUT2}	2.0 A
Output Current 3	I _{OUTX}	(X=3,4,5) other regulator 40 mA
Allowable Power Dissipation	P _{dmax}	2.45 W
Operating Temperature	T _{opr}	-20 to +75 °C
Storage Temperature	T _{stg}	-40 to +125 °C

Operating Conditions at Ta=25°C

	unit
Voltage Regulator	V _{IN1}
Input Voltage Range	+20 to +50 V
MT Pin H Voltage	V _{ENAH}
MT Pin L Voltage	V _{ENAL}

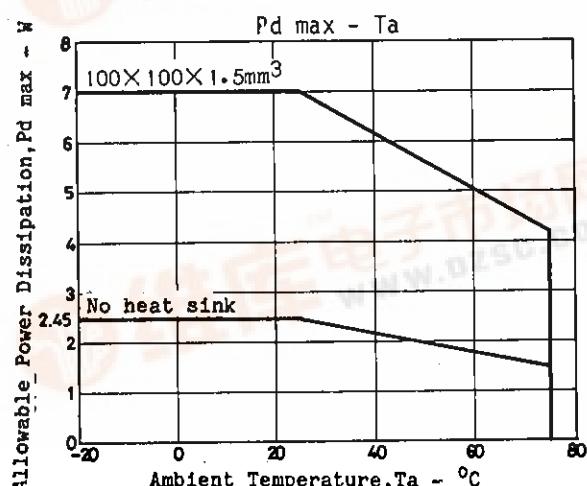

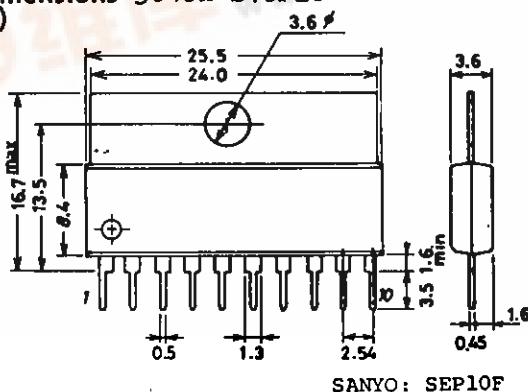Package Dimensions 3046A-S10FIC
(unit: mm)




SANYO: SEP10F

LA5655


Operating Characteristics at $T_a=25^{\circ}\text{C}$		$V_{\text{IN}1}=35\text{V}, V_{\text{IN}2}=10\text{V}, I_{\text{OUT}2}=200\text{mA}$	min	typ	max	unit	
Output Voltage 1	$V_{\text{OUT}1}$	①→⑧ $I_{\text{OUT}1}=30\text{mA}$	28.5	30	32.5	V	
Output Voltage 2	$V_{\text{OUT}2}$	⑦→⑧ $I_{\text{OUT}2}=5\text{mA}$	5.3	5.6	6.0	V	
Output Voltage 3	$V_{\text{OUT}3}$	①→⑩ $I_{\text{OUT}3}=-12\text{mA}$	13.8	15	16.2	V	
Output Voltage 4	$V_{\text{OUT}4}$	③→④ $I_{\text{OUT}4}=-30\text{mA}$	4.6	5	5.4	V	
Output Voltage 5	$V_{\text{OUT}5}$	③→⑧ $I_{\text{IN}5}=30\text{mA}$	7.3	8	8.7	V	
Load Regulation 1	$\Delta V_{01\text{LOAD}}$	$10\text{mA} < I_{\text{OUT}1} < 30\text{mA}$			250	mA	
Load Regulation 2	$\Delta V_{02\text{LOAD}}$	$100\text{mA} < I_{\text{OUT}2} < 2\text{A}$			250	mA	
Load Regulation 3	$\Delta V_{03\text{LOAD}}$	$-20\text{mA} < I_{\text{OUT}3} < -5\text{mA}$			100	mA	
Load Regulation 4	$\Delta V_{04\text{LOAD}}$	$-40\text{mA} < I_{\text{OUT}4} < -10\text{mA}$			100	mA	
Load Regulation 5	$\Delta V_{05\text{LOAD}}$	$20\text{mA} < I_{\text{IN}5} < 40\text{mA}$			200	mA	
Line Regulation 1	$\Delta V_{01\text{LINE}}$	$33\text{V} < V_{\text{IN}1} < 45\text{V}$			250	mA	
Line Regulation 2	$\Delta V_{02\text{LINE}}$	$7.5\text{V} < V_{\text{IN}2} < 20\text{V}$			100	mA	
Line Regulation 3	$\Delta V_{03\text{LINE}}$	$33\text{V} < V_{\text{IN}1} < 45\text{V}$			100	mA	
Line Regulation 4	$\Delta V_{04\text{LINE}}$	$6.5\text{V} < V_{\text{IN}5} < 8\text{V}$			100	mA	
Quiescent Current 1	$I_{\text{CC}1}$				6.5	mA	
Quiescent Current 2	$I_{\text{CC}2}$				8.5	12.0	mA
Input-Output Voltage Drop	V_{D1}	$V_{\text{OUT}1} \Delta V_{01} = 10\%, I_{\text{OUT}1} = 35\text{mA}$			1.3	V	
Saturation Voltage at $V_{\text{OUT}2}$ OFF Mode	V_{D2-1}	$V_{\text{OUT}2} \Delta V_{02} = 10\%, I_{\text{OUT}2} = 1\text{A}$			1.4	V	
	V_{D2-2}	$V_{\text{OUT}2} \Delta V_{02} = 10\%, I_{\text{OUT}2} = 2\text{A}$			1.9	V	
	V_{D2-2} OFF(sat)	$I_{\text{OUT}2} = -1\text{A}$			1.4	V	

Pin Assignment

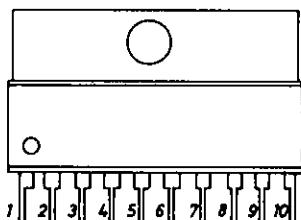

Pin No.	Pin Name	Pin No.	Pin Name
1	$V_{\text{OUT}1}$	6	$V_{\text{IN}2}$
2	$V_{\text{IN}1}$	7	$V_{\text{OUT}2}$
3	$V_{\text{OUT}5}$	8	GND
4	$V_{\text{OUT}4}$	9	R
5	MT	10	$V_{\text{OUT}3}$

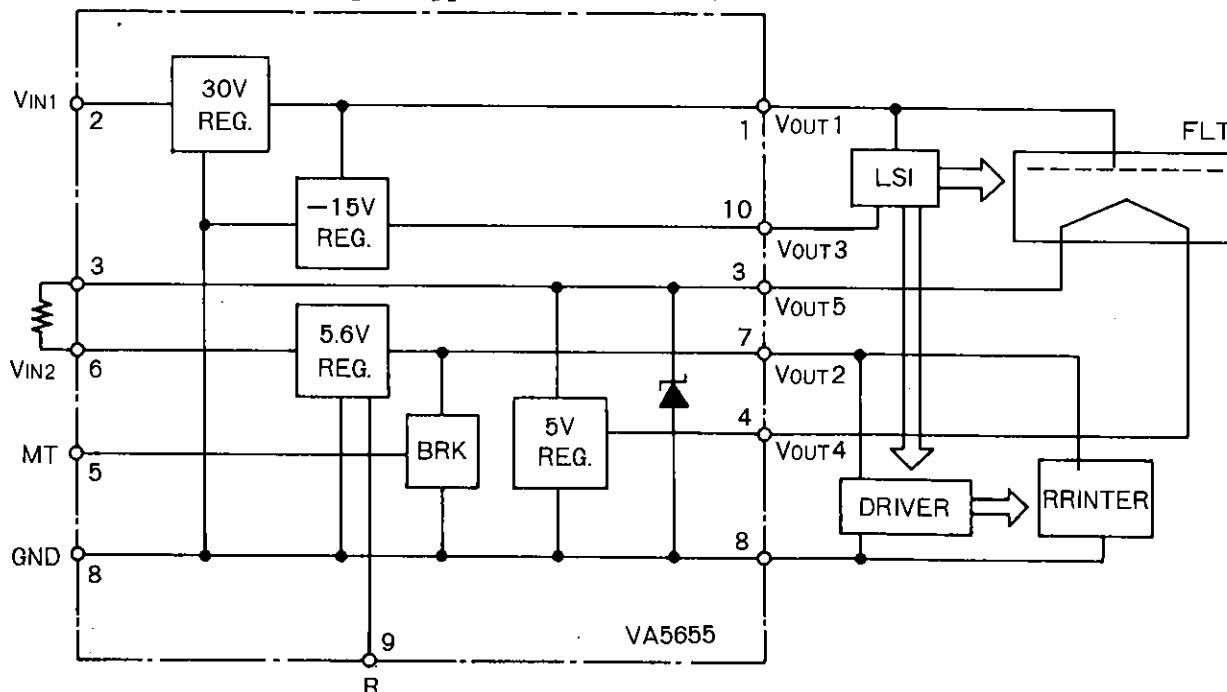Block Diagram and Sample Application Circuit



- No products described or contained herein are intended for use in surgical implants, life-support systems, aerospace equipment, nuclear power control systems, vehicles, disaster/crime-prevention equipment and the like, the failure of which may directly or indirectly cause injury, death or property loss.
- Anyone purchasing any products described or contained herein for an above-mentioned use shall:
 - ① Accept full responsibility and indemnify and defend SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors and all their officers and employees, jointly and severally, against any and all claims and litigation and all damages, cost and expenses associated with such use;
 - ② Not impose any responsibility for any fault or negligence which may be cited in any such claim or litigation on SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors or any of their officers and employees jointly or severally.
- Information (including circuit diagrams and circuit parameters) herein is for example only; it is not guaranteed for volume production. SANYO believes information herein is accurate and reliable, but no guarantees are made or implied regarding its use or any infringements of intellectual property rights or other rights of third parties.