



# Technical Data TCA 440 / T

Edition 12/95

## AM - Receiver Circuit

### Description


This is an efficient bipolar monolithic circuit to apply in battery - powered or mains - operated radio receivers up to 30 MHz. It contains controlled RF stage, mixer, separated oscillator and regulated multistage IF amplifier.



### Features

- symmetrical structured circuitry
- controlled RF prestage
- multiplicative balanced mixer, separated oscillator
- very well implemented large - signal characteristic begins already from 4.5 V supply voltage
- terminals for indicating instrument
- controlled IF amplifier implementing 60 dB control range
- external demodulator (diode)
- wide range of supply voltage between 4.5 and 15 V

### Package

TCA 440 • DIP 16

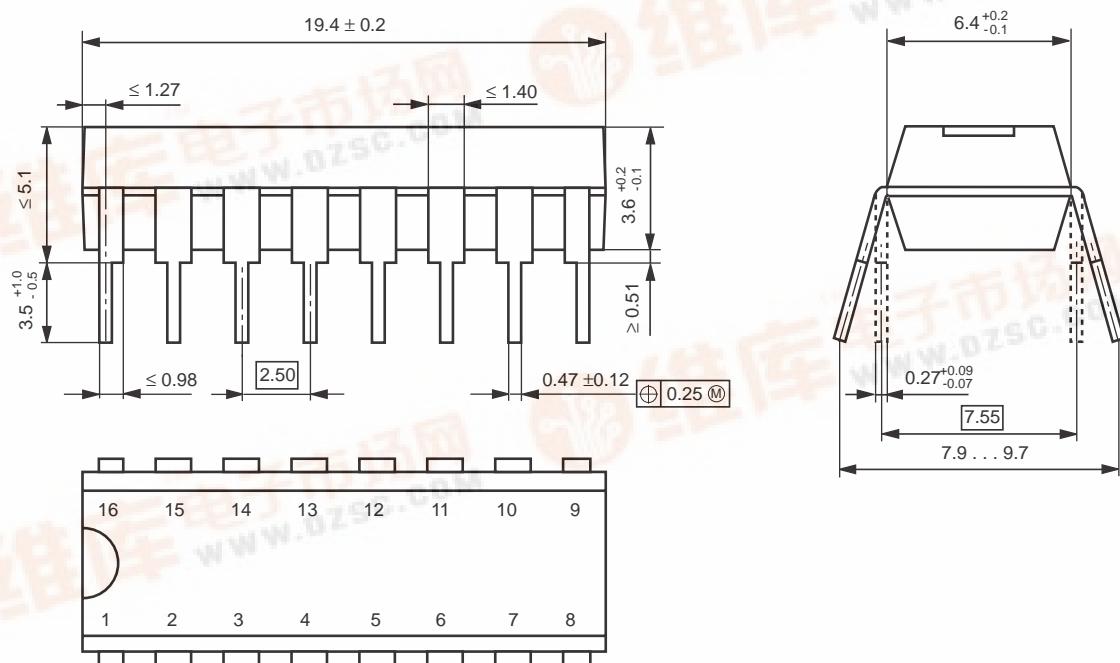


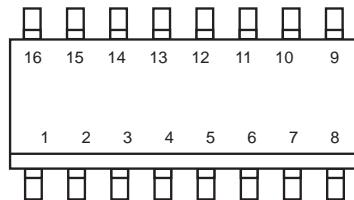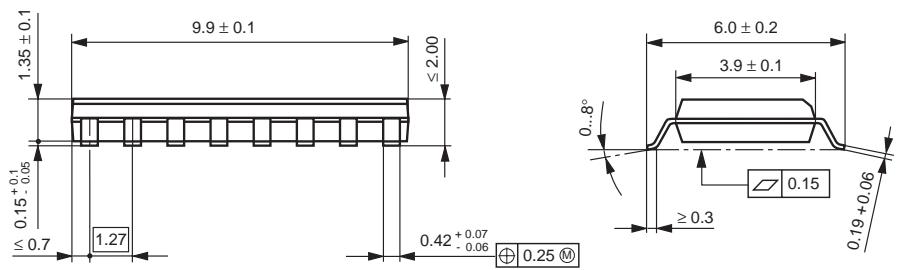

### Pin configuration

1	RF prestage, input 1	9	input IF control amplifier
2	RF prestage, input 2	10	indicator output IF control amplifier
3	RF control amplifier input	11	IF blocking
4	oscillator circuit pin 1	12	input IF amplifier
5	oscillator circuit pin 2	13	IF blocking
6	oscillator circuit pin 3	14	supply voltage
7	IF output	15	mixer output 1
8	ground	16	mixer output 2

### Block diagram

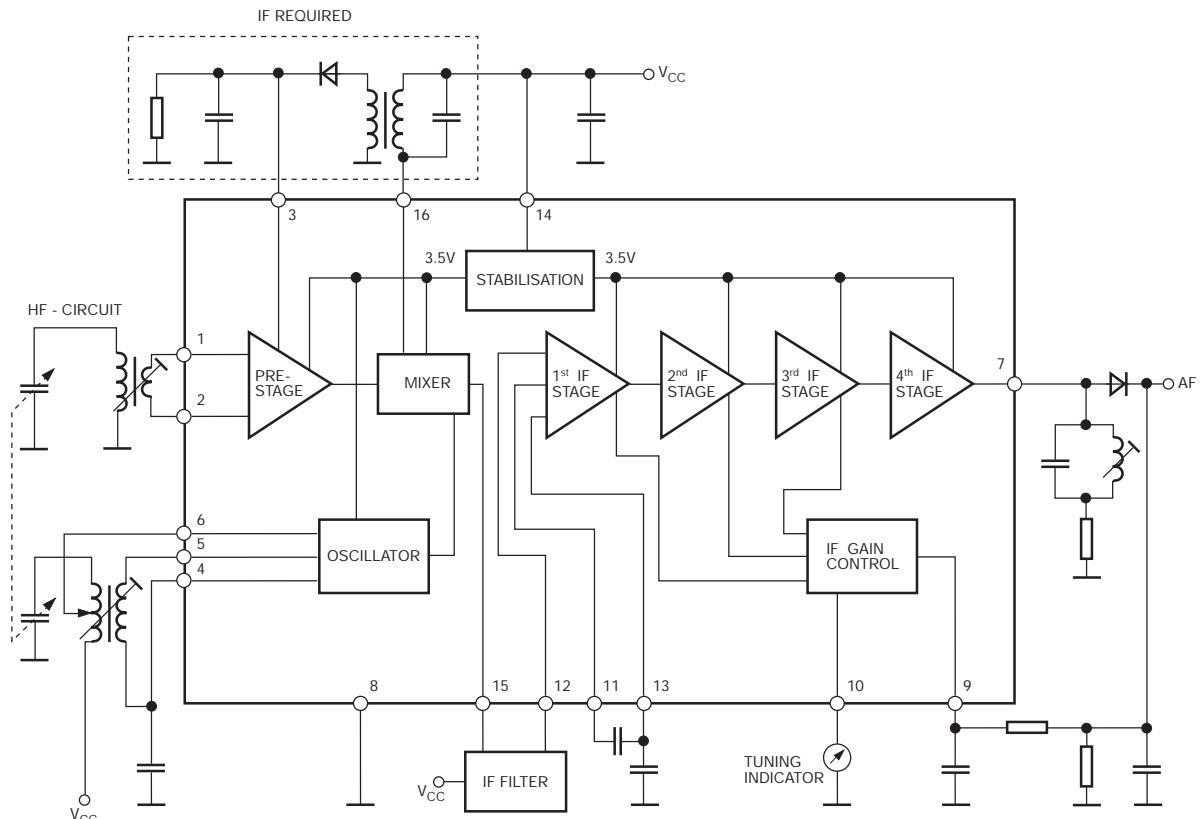

## Functional description

It contains several function units, which enable designing and assembling of efficient AM tuners. Caused by internal voltage stabilization characteristics are rather independent from supply voltage.

The RF input signal reaches via a controllable and overdriving proof preselector stage a balanced mixer. By means of a RF - signal generated by a separated oscillator the input signal is transported into IF. Multiplicative mixing causes only few harmonic content. Gain control is carried out by means of two separated feedback control loops for preselector stage and IF amplifier. By these a loop bandwidth of approximately 100 dB is obtained. The control voltage of the IF - amplifier can be used to drive a moving - coil instrument (field strength indicator). The IF amplifier consists of 4 amplifier stages, the first, second and third can be controlled. The bandwidth of the IF amplifier is approximately 2 MHz and on that account sufficient for usual IF frequencies in the AM range of approximately 460 kHz.

The symmetrical arrangement of the entire circuitry guarantees well oscillating. The bridge of the mixer avoids direct breakdown.

## Absolute maximum ratings

		min	max	unit
Supply voltage	$V_{CC}$	4.5	15.0	V
Junction temperature	$T_j$		150	°C
Ambient operating temperature	$T_a$	-15	80	°C
Storage temperature	$T_s$	-40	125	°C
Total thermal resistance	$R_{thja}$		120	K/W

## Recommended operational conditions

		min	max	unit
Supply voltage	$V_{CC}$	4.5	15	V
Ambient operating temperature	$T_a$	-10	70	°C

## Characteristics

refer to application examples,  $f_i = 1 \text{ MHz}$ ,  $f_{osc} = 1.455 \text{ kHz}$ ,  $f_{IF} = 455 \text{ kHz}$ ,  $V_{CC} = 9 \text{ V}$ ,  $f_m = 1 \text{ kHz}$ ,  $m = 0.8$ , voltages refer to ground,  $T_a = 20 \text{ to } 25 \text{ }^\circ\text{C}$ , unless specified otherwise

		min	typ	max	unit
<u>Current and voltage supply (no RF signal)</u>					
Supply voltage $V_{14-8} = 4.5 \text{ V}$	$V_{14-8}$	4.5	9	15	V
Current consumption $V_{14-8} = 9 \text{ V}$	$I_{14}$		7		mA
$V_{14-8} = 15 \text{ V}$	$I_{14}$		10.5	16	mA
	$I_{14}$		12		mA
<u>Entire receiver</u>					
RF level variation with $\Delta V_{NF} = 6 \text{ dB}$	$\Delta V_{RF}$		65		dB
with $\Delta V_{NF} = 10 \text{ dB}$	$\Delta V_{RF}$		80		dB
NF output voltages (symmetrically measured at 1-2)					
$V_{iHF} = 20 \mu\text{V}$ , $m = 0.8$	$V_{NF(rms)}$	60	140		mV
$V_{iHF} = 1 \text{ mV}$ , $m = 0.8$	$V_{NF(rms)}$		260		mV
$V_{iHF} = 500 \text{ mV}$ , $m = 0.8$	$V_{NF(rms)}$	100	350	560	mV
$V_{iHF} = 20 \mu\text{V}$ , $m = 0.3$	$V_{NF(rms)}$		50		mV
$V_{iHF} = 1 \text{ mV}$ , $m = 0.3$	$V_{NF(rms)}$		100		mV
$V_{iHF} = 500 \text{ mV}$ , $m = 0.3$	$V_{NF(rms)}$		130		mV
RF input sensitivity measured at $60 \Omega$ , $m = 0.3$ , $R_G = 540 \Omega$					
signal-to-noise ratio $S + N/N = 6 \text{ dB}$	$V_{iRF}$		1		$\mu\text{V}$
$S + N/N = 26 \text{ dB}$	$V_{iRF}$		7		$\mu\text{V}$
$S + N/N = 58 \text{ dB}$	$V_{iRF}$		1		mV
Maximum RF input voltage (THD = 10 %)	$V_{iHF}$			1.5	V
Total harmonic distortion					
$V_{HF} = 500 \text{ mV}$	THD		4.5	10	%
$V_{HF} = 30 \text{ mV}$	THD		2.8	8	%
<u>RF part</u>					
Input frequency range	$f_{iHF}$	0		50	MHz
Output frequency $f_{IF} = f_{osc} - f_{iHF}$	$f_{IF}$		455		kHz
Control range	$\Delta G_V$		38		dB





		min	typ	max	unit
IF suppression between 1 - 2 and 15	$a_{IF}$		20		dB
RF input impedance unbalanced coupling $V_{iHFmax}$	$Z_i$		2 II 5		$k\Omega II pF$
$V_{iHFmin}$	$Z_i$		2.2 II 1.5		$k\Omega II pF$
balanced coupling $V_{iHFmax}$	$Z_i$		4.5		$k\Omega$
$V_{iHFmin}$	$Z_i$		4.5 II 1.5		$k\Omega II pF$
Mixer output impedance (pin 15 or 16)	$Z_o$		250 II 4.5		$k\Omega II pF$
Steepness	$S_{HF}$		28		mS
<u>IF part</u>					
Input frequency range	$f_{iIF}$	0		2	MHz
Control range $f_{iIF} = 455 \text{ kHz}, \Delta V_{NF} = 10 \text{ dB}$	$\Delta G_V$		62		dB
Start of control $(\Delta V_{iIF} / \Delta V_{NF} = 10 \text{ dB} / 3 \text{ dB})$	$V_{ctrlIF}$		140		$\mu\text{V}$
maximum IF input voltage $(\text{THD}_{NF} = 10 \%)$	$V_{iIFmax}$		200		$\text{mV}$
NF output voltage applied to $60 \Omega$ $V_{ZF} = 30 \mu\text{V}$	$V_{NF(rms)}$		50		$\text{mV}$
$V_{ZF} = 3 \text{ mV}$	$V_{NF(rms)}$		200		$\text{mV}$
$V_{ZF} = 3 \text{ mV}; m = 0.3$	$V_{NF(rms)}$		70		$\text{mV}$
IF input impedance (unbalanced coupling)	$Z_{iIF}$		3 II 3		$k\Omega II pF$
IF output impedance (pin 7)	$Z_o$		200 II 8		$k\Omega II pF$





## Indication instrument





Recommended indication instruments:  $500 \mu\text{A}$  ( $R_i = 800 \Omega$ )  
 $300 \mu\text{A}$  ( $R_i = 1.5 \text{ k}\Omega$ )





For indication a voltage source of  $600 \text{ mV}_{(\text{EMF})}$  and an internal source impedance of  $400 \Omega$  is available.


## Dependences

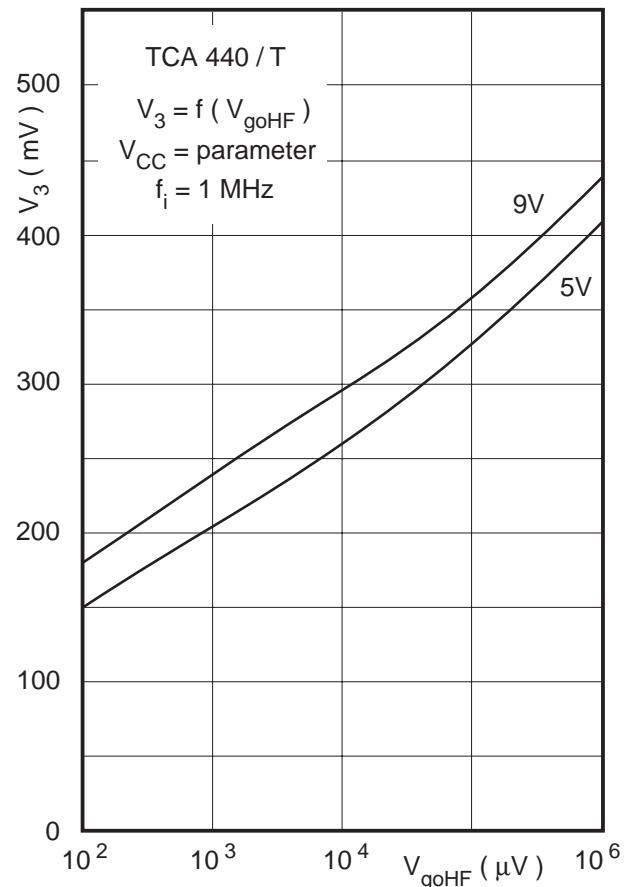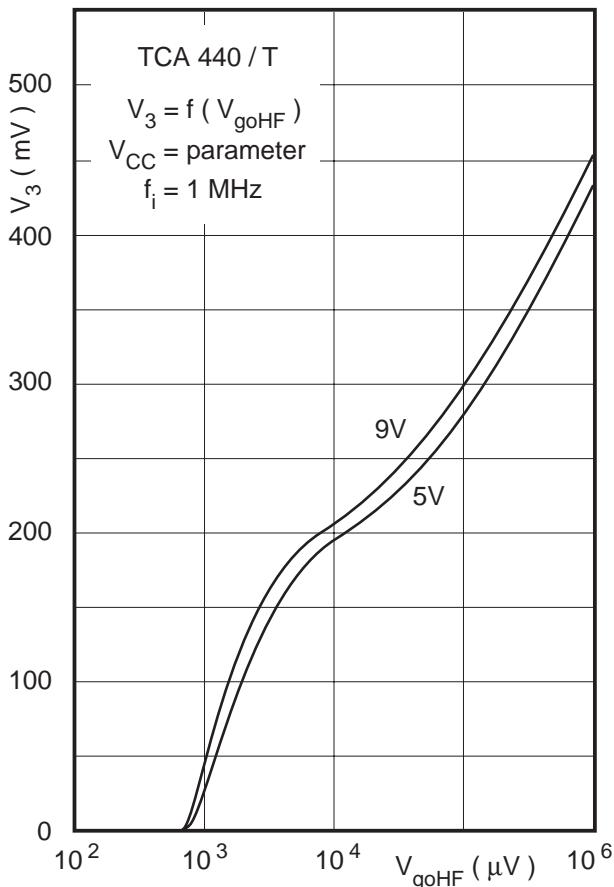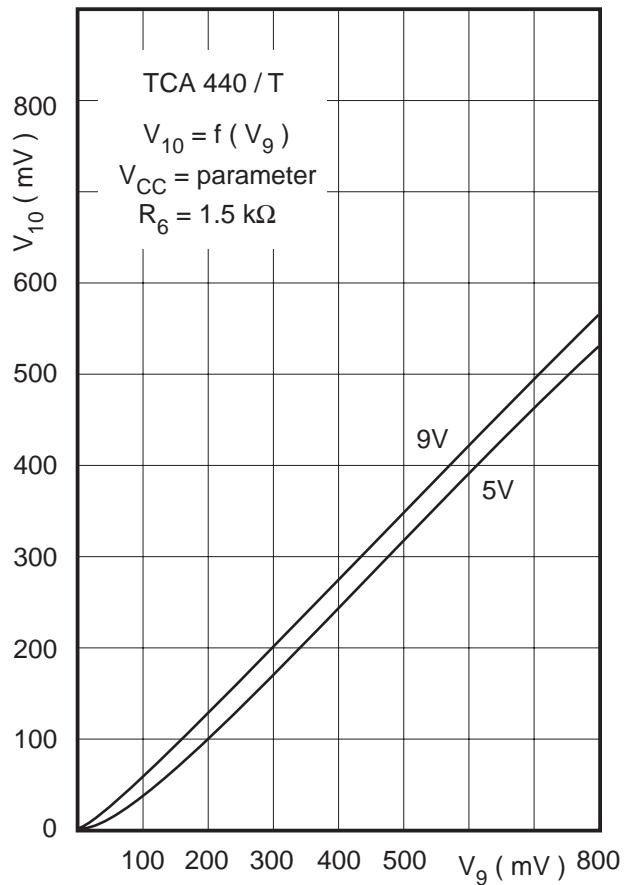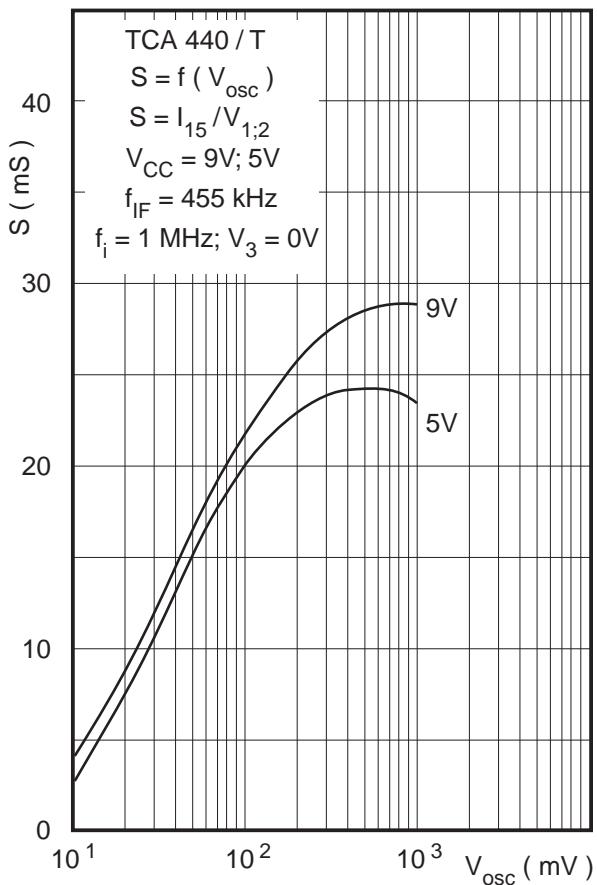

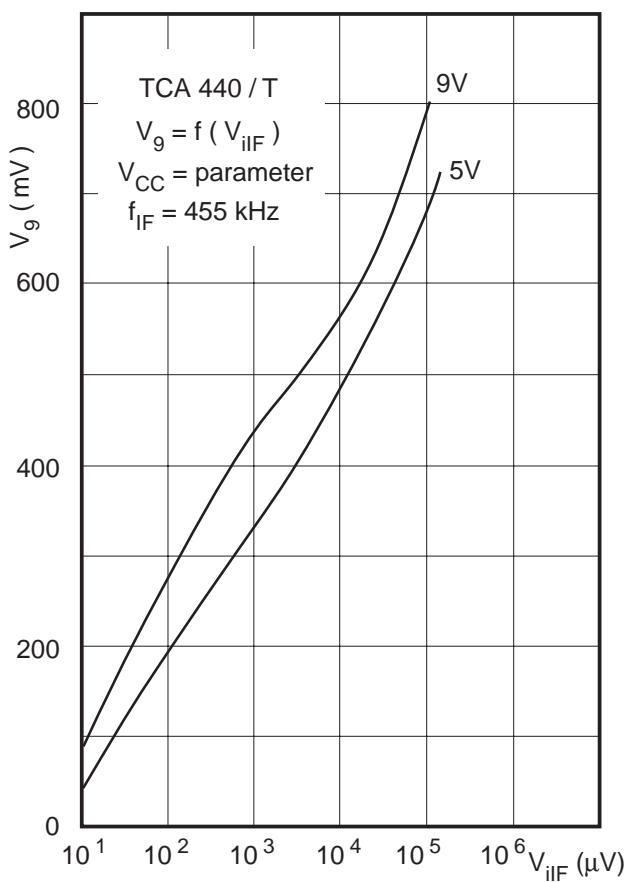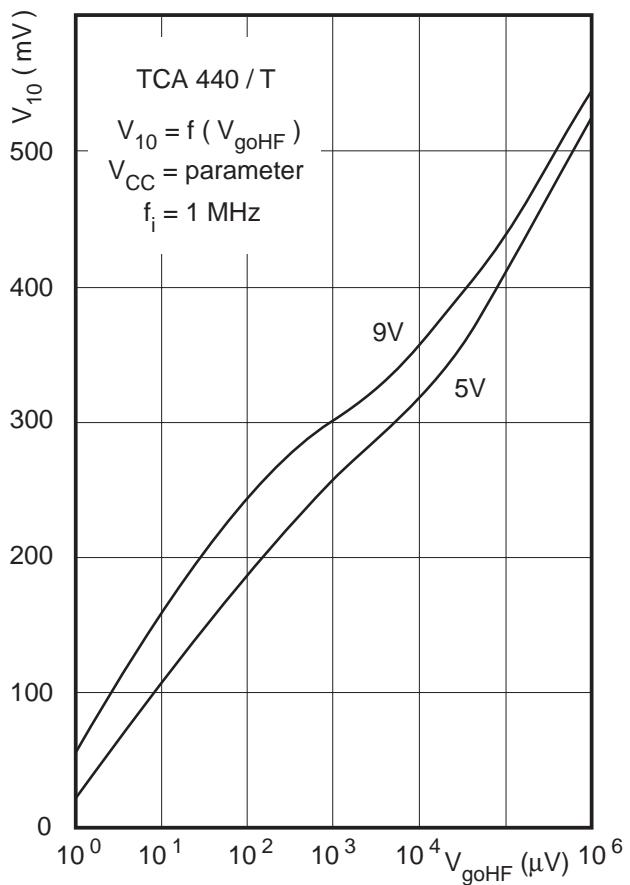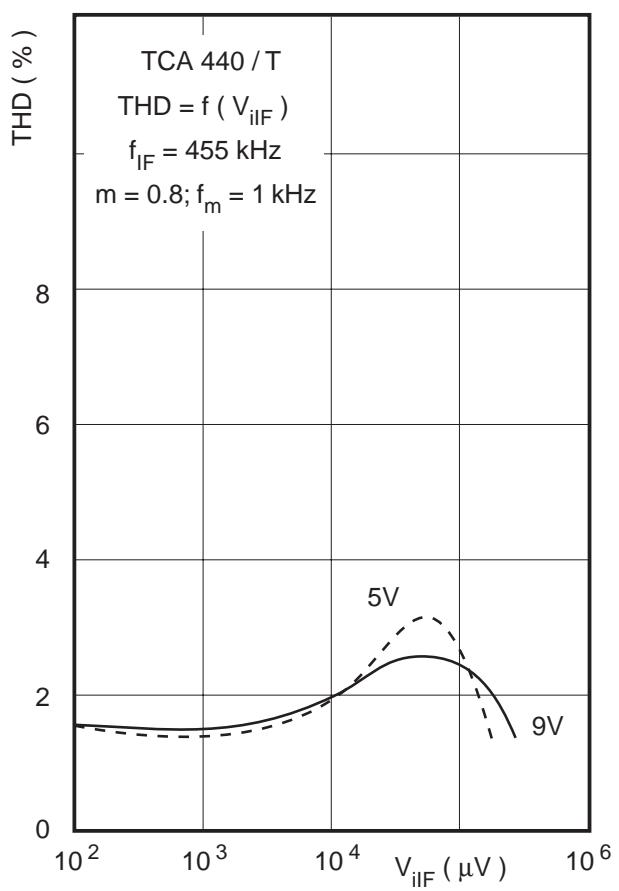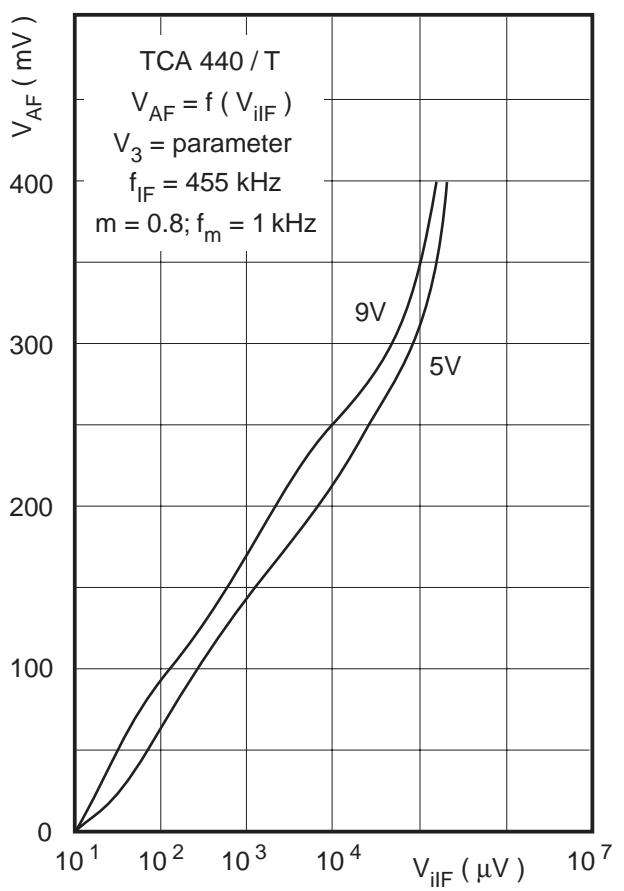

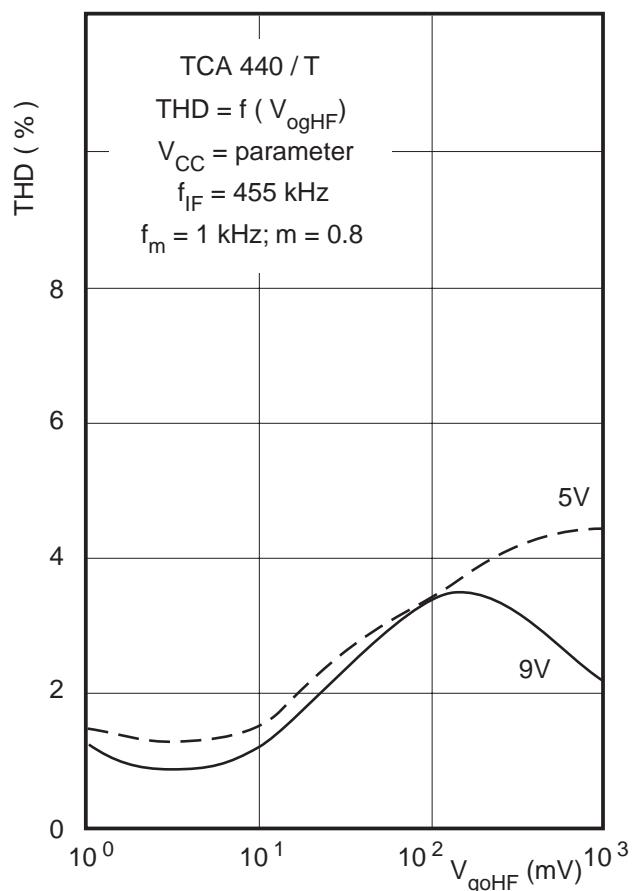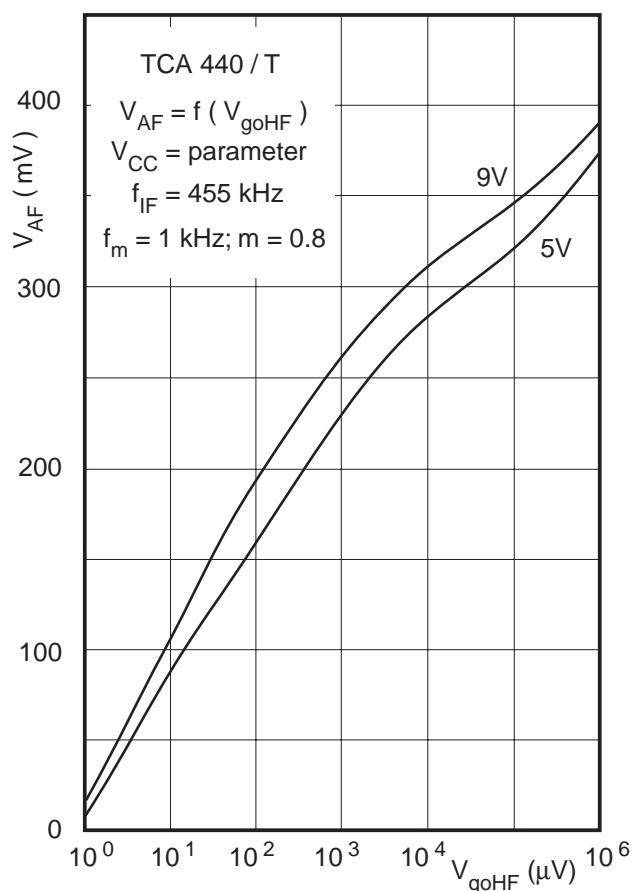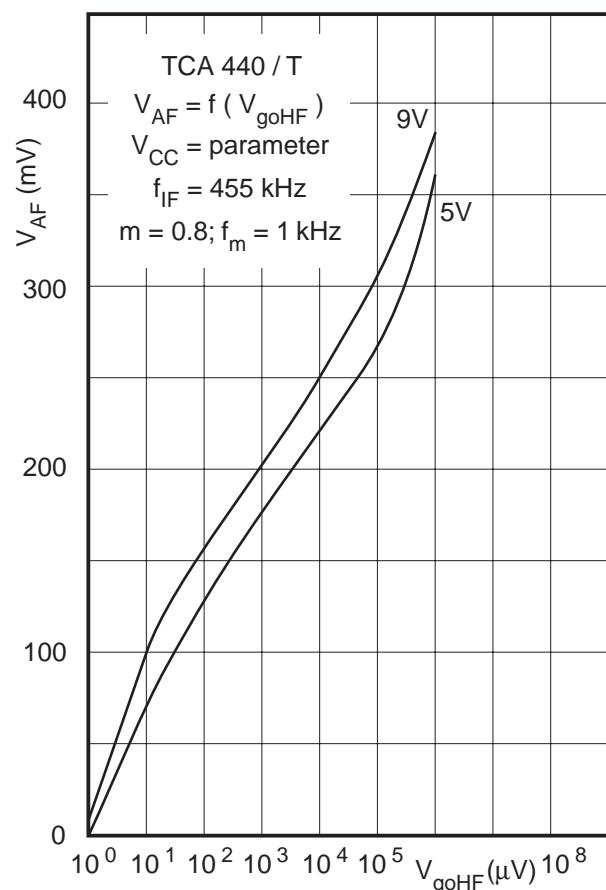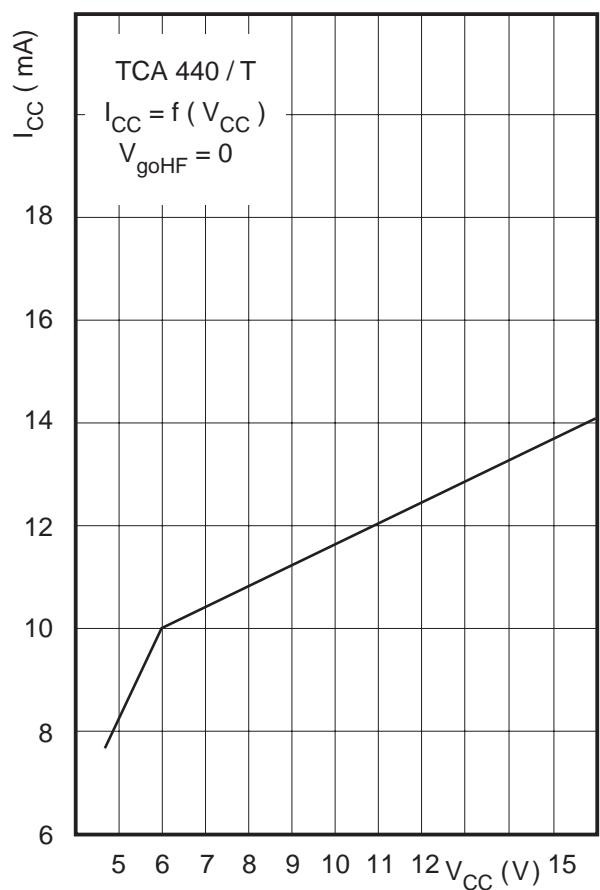


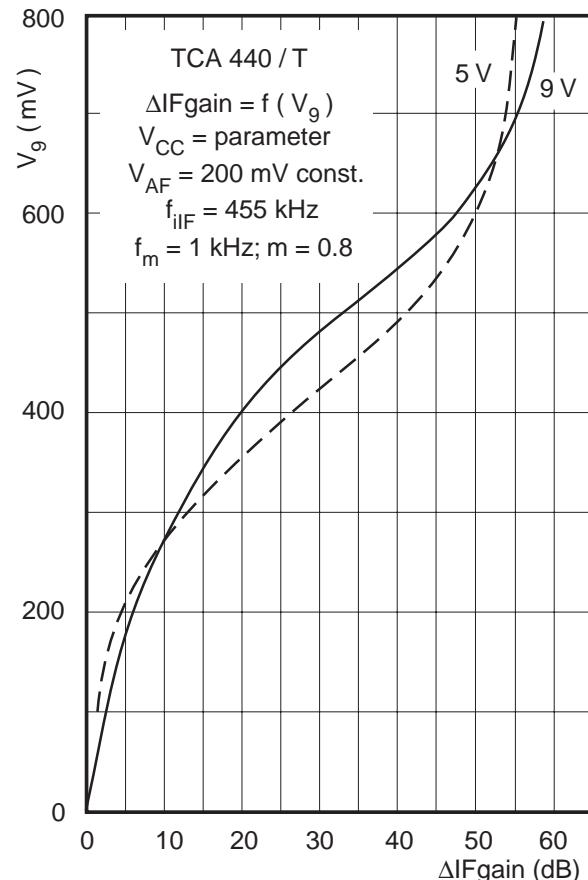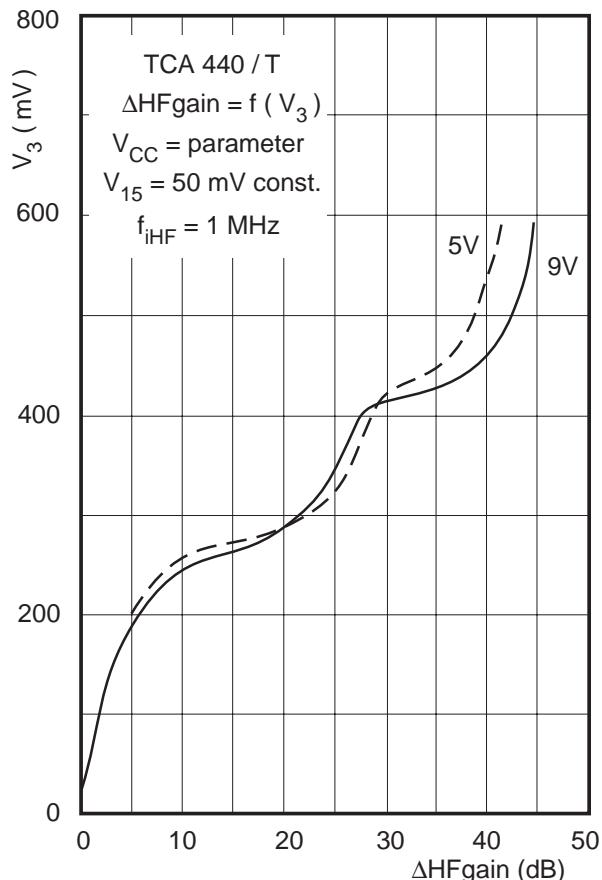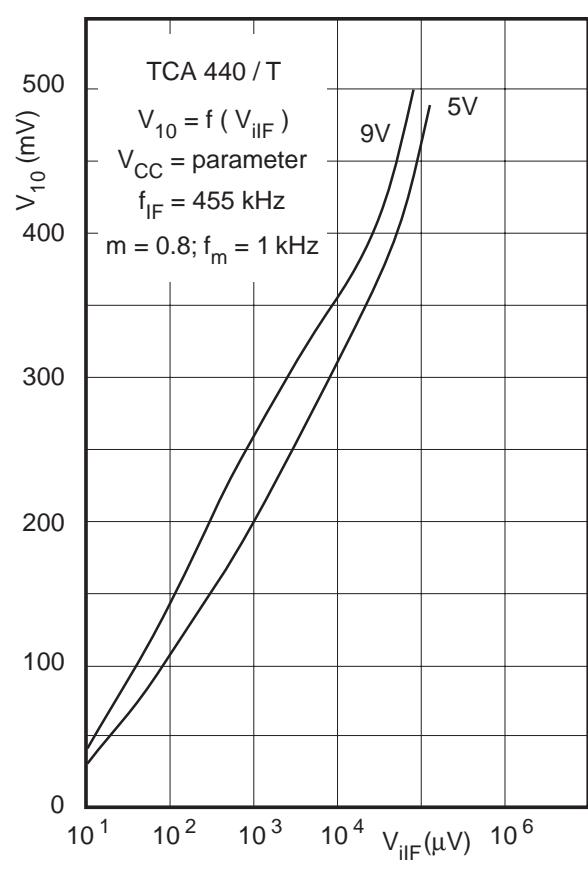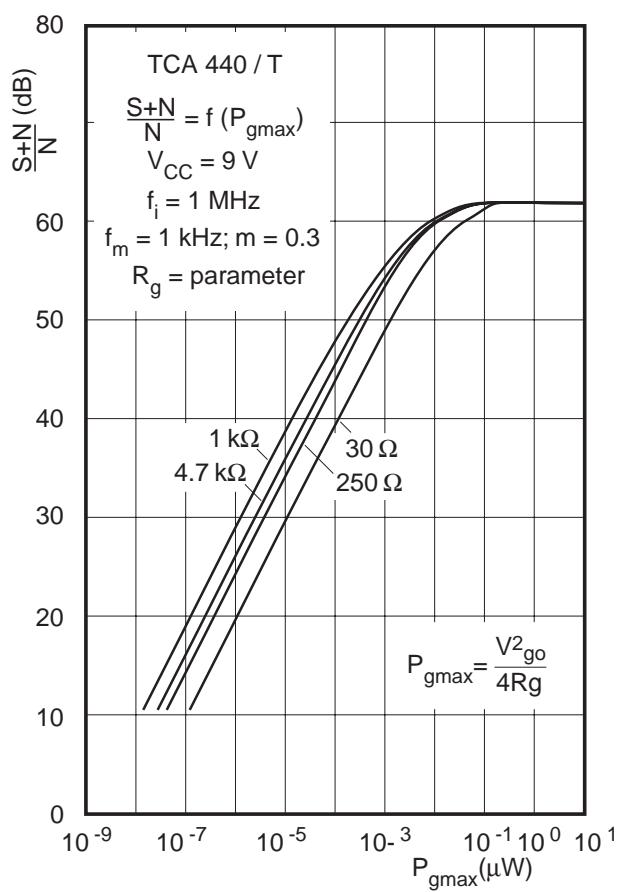

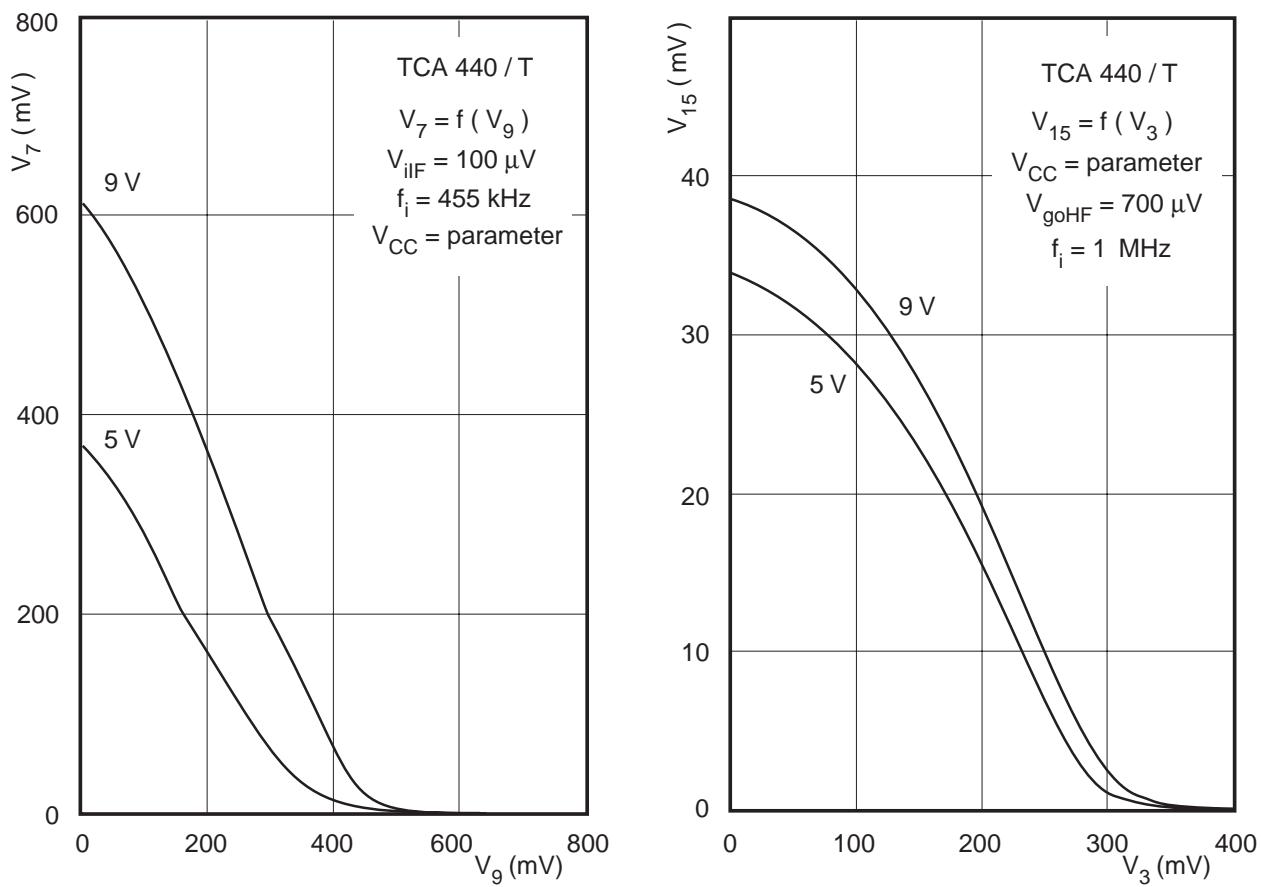


## Application examples

- **TCA 440**

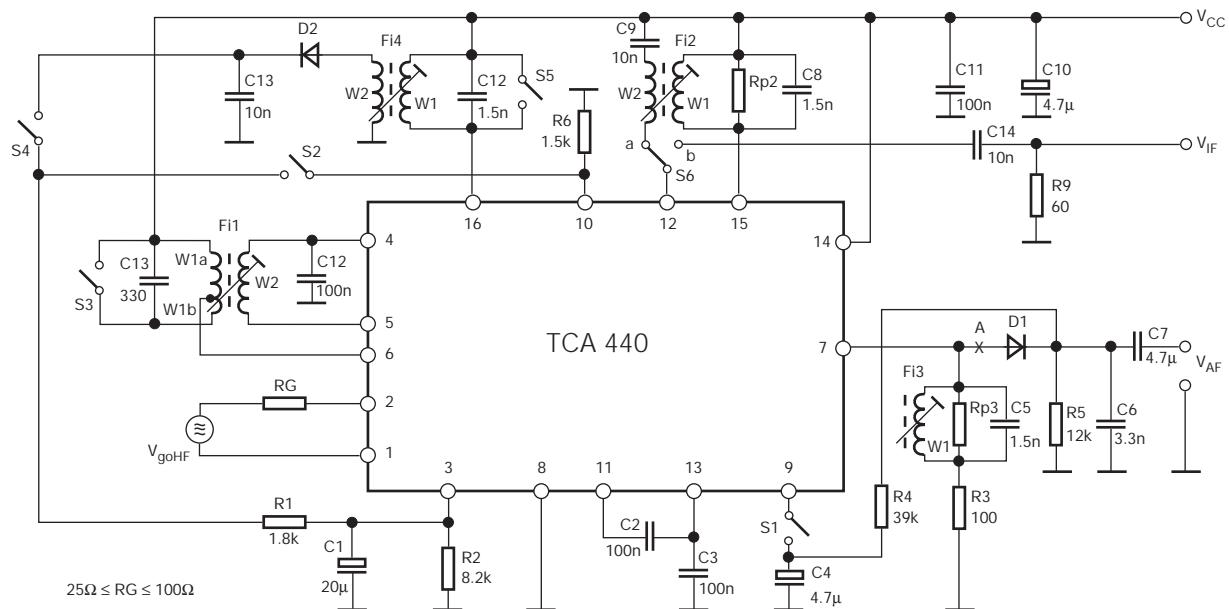

- TCA 440 T

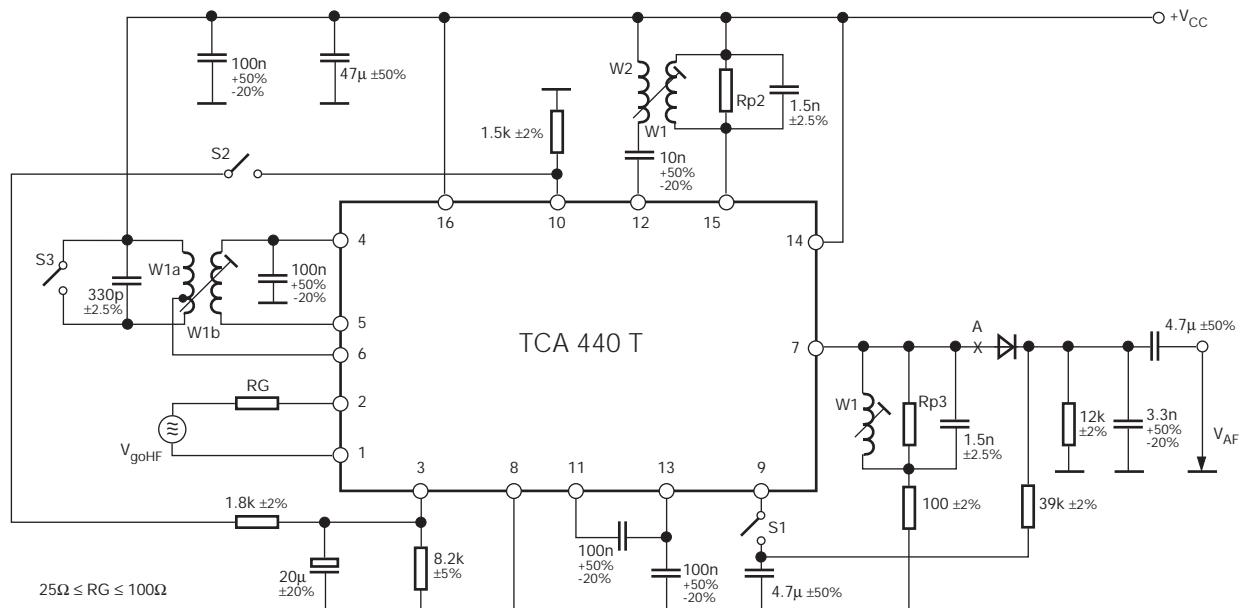

## Application hints

The PCB is to arrange such that there are maximum ground lines (ground area) voltage supply has to be blocked to ground by a capacitor of 10...100 nF in order to avoid distortions. Blocking should be as close as possible to the circuit.

The RF circuit has to layout such that 150 mV<sub>(rms)</sub> oscillator voltage are applied to pin 5. Symmetrically applying an external oscillator is possible to pin 4 or pin 5. The unused input must be connected to ground via capacitor and in the same time be connected to supply voltage at pin 6.

It is recommendable to profile off earth connections 1 and 3, because in this way common - mode interferences more effectively can be suppressed. Single - sided capacitive control of pin 1 and 2 is possible, the unused input must be connected to ground via capacitor.

Mixer outputs 15 and 16 can be used equivalently.

Load resistances of the mixer (IF selection) at pin 15 respectively pin 16 should run to approximately 7 k $\Omega$ .

To avoid saturation of the multiplier the maximum peak voltage occurring during operation should not exceed the level ( $V_{CC} - 3$  V) IF response to voltage from pin 15 respectively pin 16 to pin 12 should be approximately - 18 dB that the control characteristics of IF - and RF - part optimally be matched.

Peak voltage at pin 7 occurring during operation should not exceed 2 V that the IF output does not go into saturation.

All the RF bypass capacitors should amount to 100 nF. Sufficient decoupling of wavemagnet and oscillator coil is to be taken into consideration.

All components and parts must be carefully proportioned in order to obtain optimum wise characteristics.

Wavemagnets applied should so much mass as possible. The transformation ratio of the input circuitry should run 1:12-13.

In order to improve RF response characteristic a RF preselector can be additionally preceded or the wavemagnet by a matching load having a low quality factor, such as a short piece of

Improvement of signal - to - noise ratio at average input voltages can be obtained by delayed control of the RF

Downloaded from https://academic.oup.com/imrn/article/2020/11/3633/3290333 by guest on 10 August 2021

Reprinting is generally permitted, indicating the source. However, our consent must be obtained before reprinting.

SMI reserves the right to make changes in specifications at any time and without notice.  
The information and suggestions are given without obligation and cannot give rise to any liability, they do not indicate the availability of the components mentioned.

The information included herein is believed to be accurate and reliable. However, the SMI assumes no responsibility for its use; nor for any infringements of patents or of other rights of third parties which may result from its use.