

DESCRIPTION

2SD1447 is a silicon NPN epitaxial type transistor designed for 2 to 3.5W output low frequency power amplify application.

Complementary with 2SB1035.

FEATURE


- High collector current $I_{CM} = 1.5A$
- High gain band width product $f_T = 100MHz$ typ
- High collector dissipation $P_C = 900mW$
- Excellent linearity of DC forward current gain

APPLICATION

2 to 3.5W output low frequency amplify circuit of radio, cassette tape recorder, mini stereo.

OUTLINE DRAWING

Unit:mm

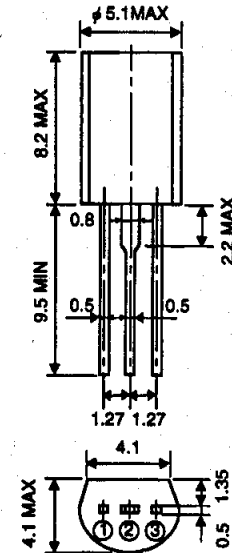

TERMINAL CONNECTOR

- ① : EMITTER
 - ② : COLLECTOR
 - ③ : BASE
- EIAJ : —
JEDEC : —

Note) The dimension without tolerance represent central value.

MAXIMUM RATINGS (Ta=25°C)

Symbol	Parameter	Rating	Unit
V _{CB0}	Collector to Base voltage	30	V
V _{EB0}	Emitter to Base voltage	4	V
V _{CE0}	Collector to Emitter voltage	25	V
I _{CM}	Peak Collector current	1.5	A
I _C	Collector current	1	A
P _C	Collector dissipation (Ta=25°C)	900	mW
T _J	Junction temperature	+150	°C
T _{stg}	Storage temperature	-55 to +150	°C

ELECTRICAL CHARACTERISTICS (Ta=25°C)


Symbol	Parameter	Test conditions	Limits			Unit
			Min	Typ	Max	
V _{(BR)CBO}	C to B break down voltage	I _C = 10 μA, I _E = 0	30			V
V _{(BR)EBO}	E to B break down voltage	I _E = 10 μA, I _C = 0	4			V
V _{(BR)CEO}	C to E break down voltage	I _C = 100 μA, R _{BE} = ∞	25			V
I _{CB0}	Collector cut off current	V _{CB} = 25V, I _E = 0			1	μA
I _{EB0}	Emitter cut off current	V _{EB} = 2V, I _C = 0			1	μA
h _{FE} *	DC forward current gain	V _{CE} = 1V, I _C = 500mA	55		300	—
V _{CE(sat)}	C to E saturation voltage	I _C = 500mA, I _B = 25mA			0.5	V
f _T	Gain band width product	V _{CE} = 6V, I _E = -10mA		100		MHz

* : It shows h_{FE} classification in right table.


Item	C	D	E
h _{FE}	55 to 110	90 to 180	150 to 300

TYPICAL CHARACTERISTICS

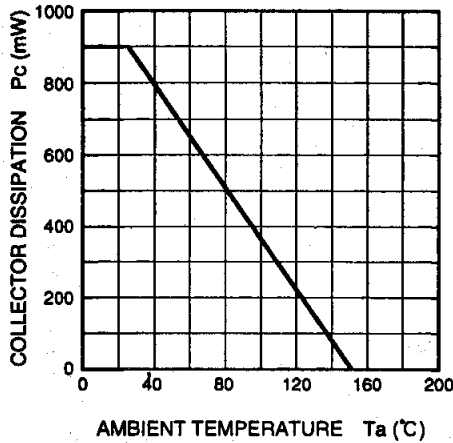
COLLECTOR DISSIPATION VS. AMBIENT TEMPERATURE




COMMON EMITTER OUTPUT

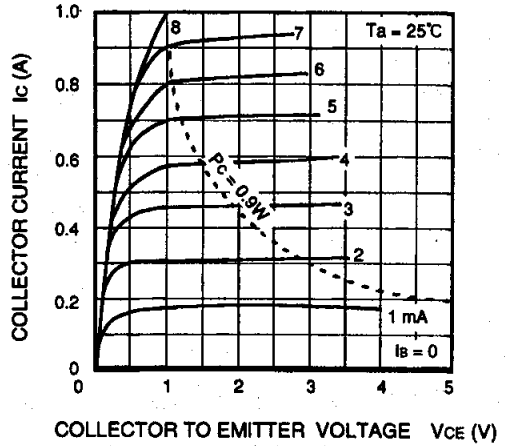


COMMON EMITTER TRANSFER

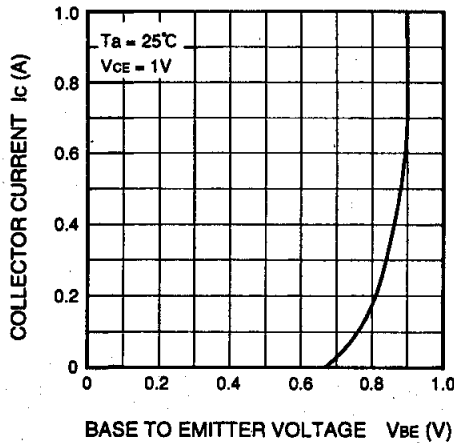

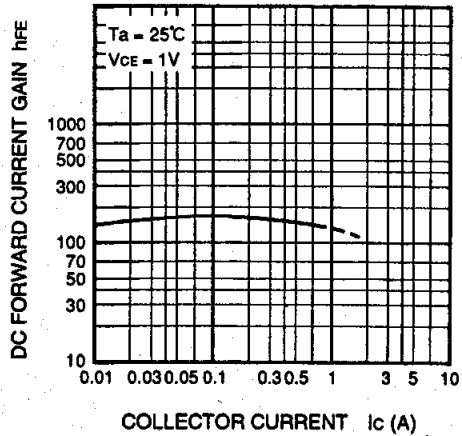DC FORWARD CURRENT GAIN VS. COLLECTOR CURRENT



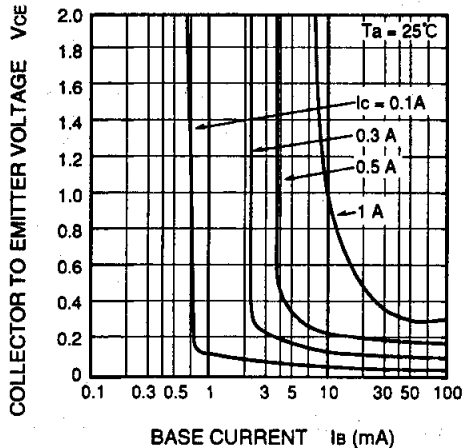COLLECTOR TO EMITTER SATURATION VOLTAGE VS. BASE CURRENT



 **ISAHAYA ELECTRONICS CORPORATION**

<http://www.idc-com.co.jp>
6-41, TSUKUBA, ISAHAYA, NAGASAKI, 854-0065, JAPAN

Keep safety in your circuit designs !

Isahaya Electronics Corporation puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage. Remember to give consideration to safety when making your circuit designs, with appropriate measures such as (i) placement of substitutive, auxiliary circuits, (ii) use of non-flammable material or (iii) prevention against any malfunction or mishap.

Notes regarding these materials

•These materials are intended as reference to assist out customers in the selection of the Isahaya semiconductor product best suited to the customer's application, they do not convey any license under any intellectual property rights, or any other rights, belonging to Isahaya Electronics Corporation or a third party.
•Isahaya Electronics Corporation assumes no responsibility for any damage, or infringement of any third-party rights, originating in the use of any product data, diagrams, charts or circuit application examples contained in the materials.
•All information contained in these materials, including product data, diagrams and charts, represent information on products at the time of publication of these materials, and are subject to change by Isahaya Electronics Corporation without notice due to product improvements or other reasons. It is therefore recommended that customers contact Isahaya Electronics Corporation or authorized Isahaya Semiconductor product distributor for the latest product information before purchasing a product listed herein.
•The prior written approval of Isahaya Electronics Corporation is necessary to reprint or reproduce in whole or in part these materials.
•If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination. Any diversion or reexport contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.
•Please contact Isahaya Electronics Corporation or an authorized Isahaya Semiconductor product distributor for further details on these materials or the products contained therein.
